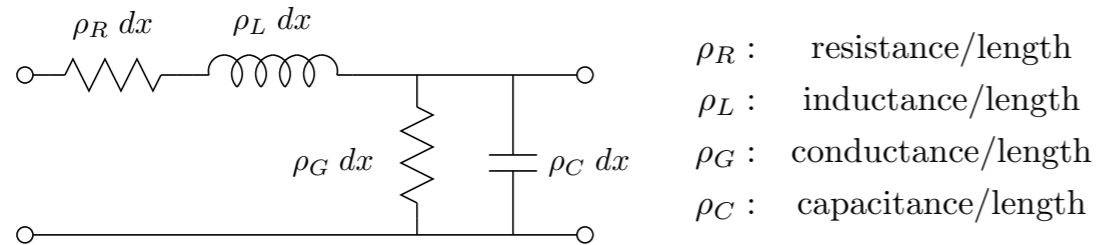


# Transmission Lines

## Transmission Line Equivalent Circuit



## Coupled 1st Order Differential Equations

$$\frac{\partial V(x)}{\partial x} = -(\rho_R + j\omega\rho_L)$$

$$\frac{\partial I(x)}{\partial x} = -(\rho_G + j\omega\rho_C)$$

## Uncoupled 2nd Order Differential Equations

$$\frac{\partial^2 V(x)}{\partial x^2} = \gamma^2 V(x)$$

$$\frac{\partial^2 I(x)}{\partial x^2} = \gamma^2 I(x)$$

$$\gamma = \sqrt{(\rho_R + j\omega\rho_L)(\rho_G + j\omega\rho_C)}$$

## Differential Equation Solutions

$$V(x) = V_{(+)}e^{-\gamma x} + V_{(-)}e^{+\gamma x}$$

$$I(x) = \frac{1}{Z_0} (V_{(+)}e^{-\gamma x} + V_{(-)}e^{+\gamma x})$$

$V_{(+)}$ ,  $V_{(-)}$  positive and negative propagating waves


## Wave propagation velocity

$$v = \frac{1}{\sqrt{\epsilon_{\text{eff}}\mu_{\text{eff}}}}$$

## Open Circuit Impedance

general	low $\omega$ limit	high $\omega$ limit
$Z = \sqrt{\frac{\rho_R + j\omega\rho_L}{\rho_G + j\omega\rho_C}}$	$Z_{\text{DC}} = \sqrt{\frac{\rho_R}{\rho_G}}$	$Z_0 = \sqrt{\frac{\rho_L}{\rho_C}}$

## Closed Equivalent Circuit

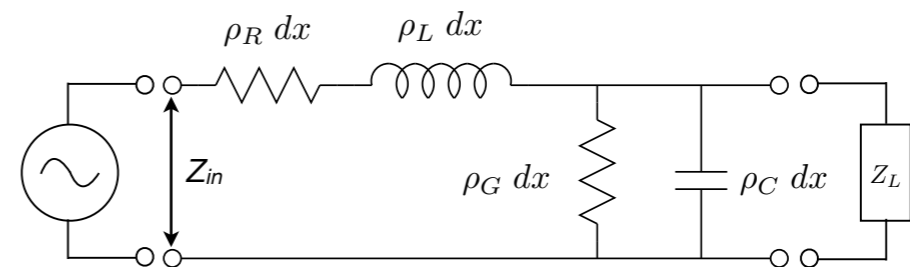

## Closed Circuit Input Impedance

$$Z_{\text{in}}(\ell) = Z_0 \frac{Z_L + jZ_0 \tanh(\gamma L)}{Z_0 + jZ_L \tanh(\gamma L)}$$

## Max Power Transmission (not max efficiency)

$$Z_{\text{in}} = Z_{\text{in}}^*$$


$$Z_L = Z_0$$

## Signal Reflection Coefficient at Load

$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0}$$

# Logic and Triggering


## Discrimination (1 bit ADC)

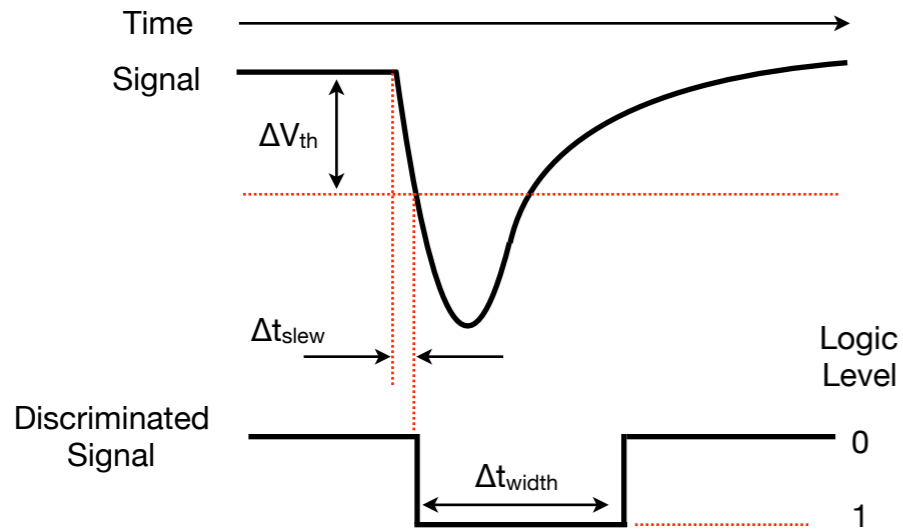

Width may be fixed or "time over threshold"


## Logic Gate Behavior

### AND (Coincidence)






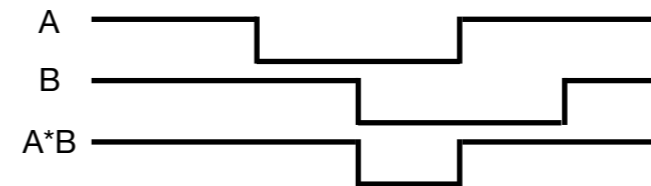


Width may be coincidence duration or fixed


### OR (Fan-In)

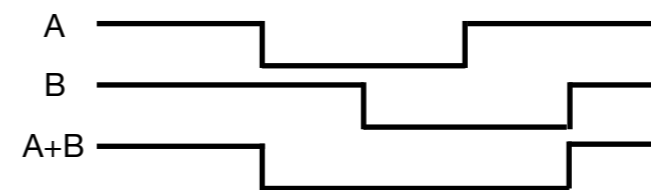

## Logic Gate Symbols

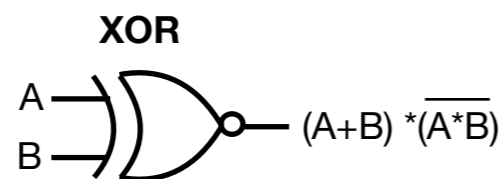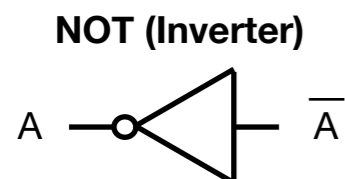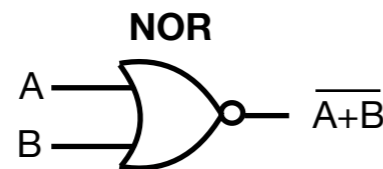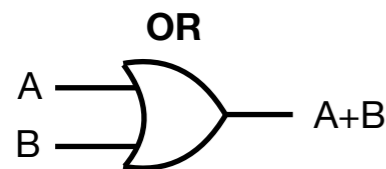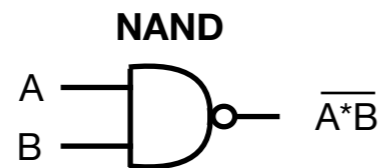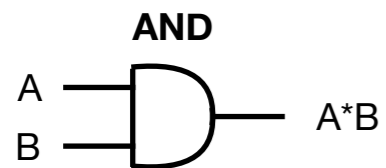

## Simple Efficiency Measurement

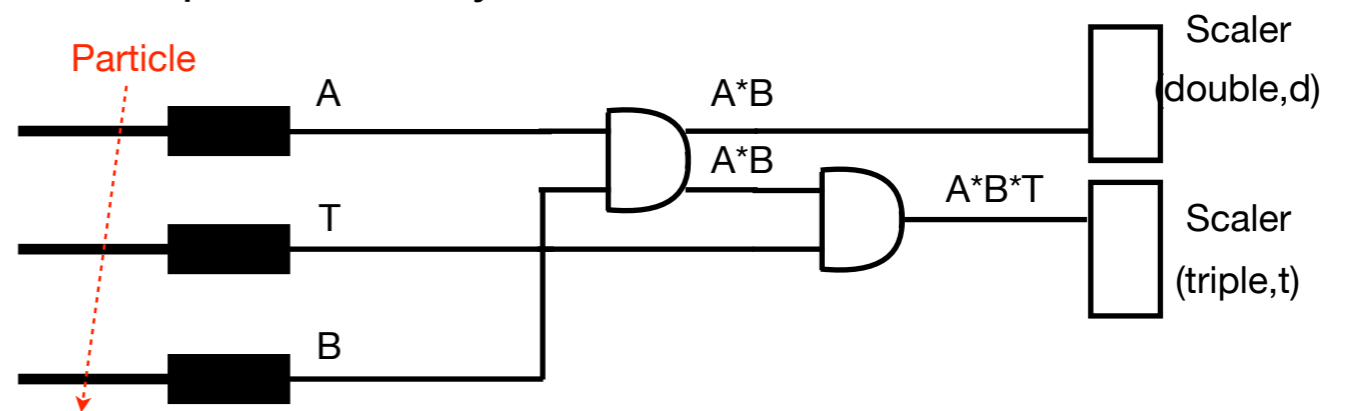

## Efficiency and its uncertainty

$$\epsilon = \frac{N_t}{N_d}$$

$$\sigma_\epsilon = \sqrt{\frac{\epsilon(1-\epsilon)}{N_d}}$$

Gates may have any number of inputs and outputs



