

# LArASIC - FE ASIC for DUNE LAr TPC

Dr. Venkata Narasimha Manyam


*Instrumentation Division, Brookhaven National Laboratory*



# Outline


- LArASIC Introduction
- Changes Between Recent LArASIC Versions
- LArASIC P3 Simulations and Identified Issues
- LArASIC P4 Development
- LArASIC P4 Simulations
- Summary and Future Work
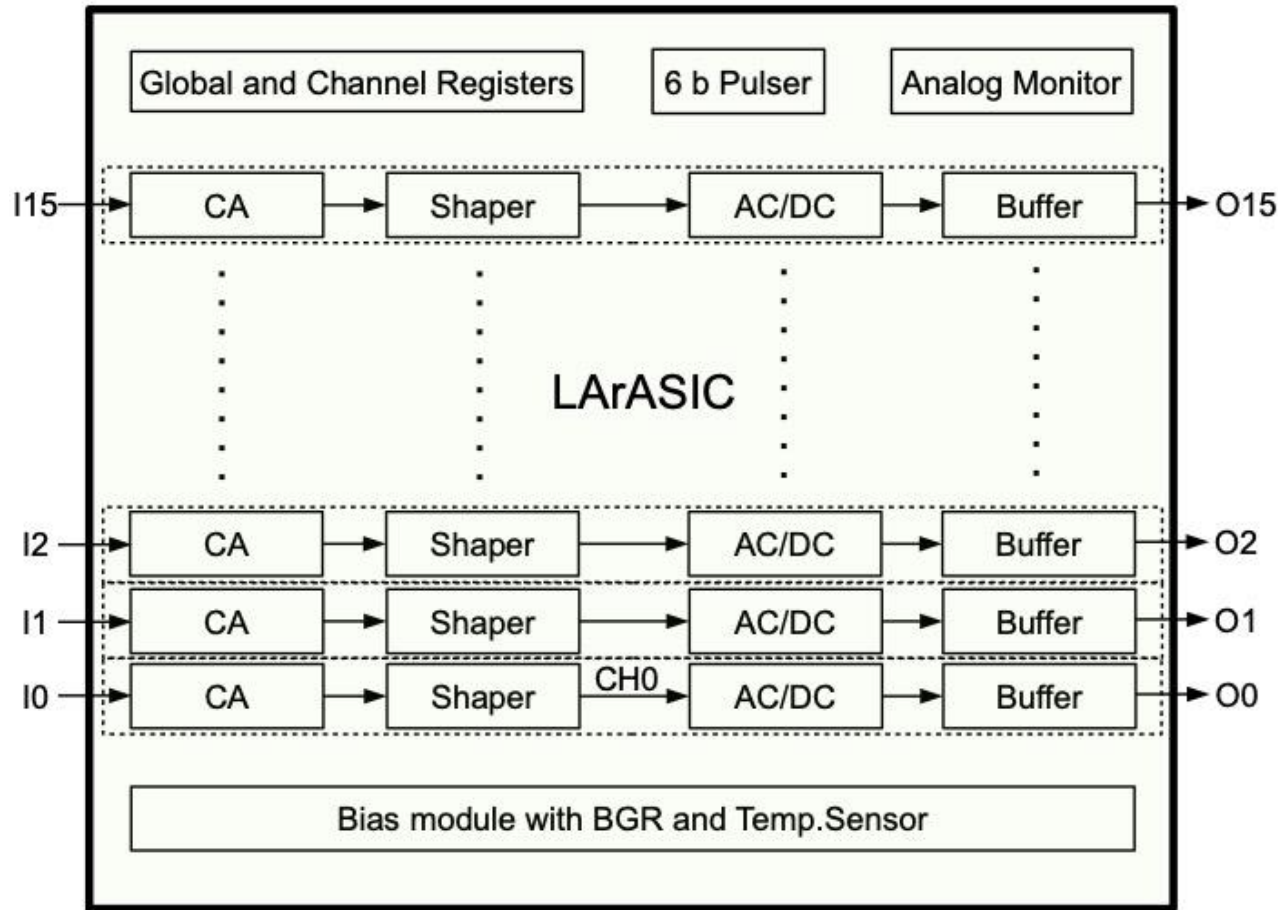
# LArASIC – Simplified block diagram & functionality




- 16 channels
- Two-stage charge amplifier, high-order filter (5<sup>th</sup>)
- Adjustable Reset Quiescent Current (RQI/leakage) settings (100 pA, 500 pA, 1nA, 5 nA)
- Adjustable gain: 4.7, 7.8, 14, 25 mV/fC (Max. charge 55, 100, 180, 300 fC)
- Adjustable filter time constant (peaking time 0.5, 1, 2, 3  $\mu$ s)
- Selectable collection/non-collection mode (baseline 200, 900 mV)
- Selectable DC/AC coupling (100 $\mu$ s HPF time-const.)
- Rail-to-rail analog signal processing with single-ended buffer
- Bandgap referenced (BGR) biasing circuits
- Temperature sensor ( $\sim 3$ mV/ $^{\circ}$ C)
- Integrated 6-bit pulse generator
- 144 configuration registers, SPI interface
- 5.5 mW/channel (input MOSFET 3.9 mW)
- $\sim 16,000$  MOSFETs
- Designed for room (300K) and cryogenic (77K) operation
- Technology CMOS 0.18  $\mu$ m, 1.8 V, 6M, MIM, SBRES

# Previous FE ASIC layout

 

Successful deployment with excellent performance at MicroBooNE and ProtoDUNE
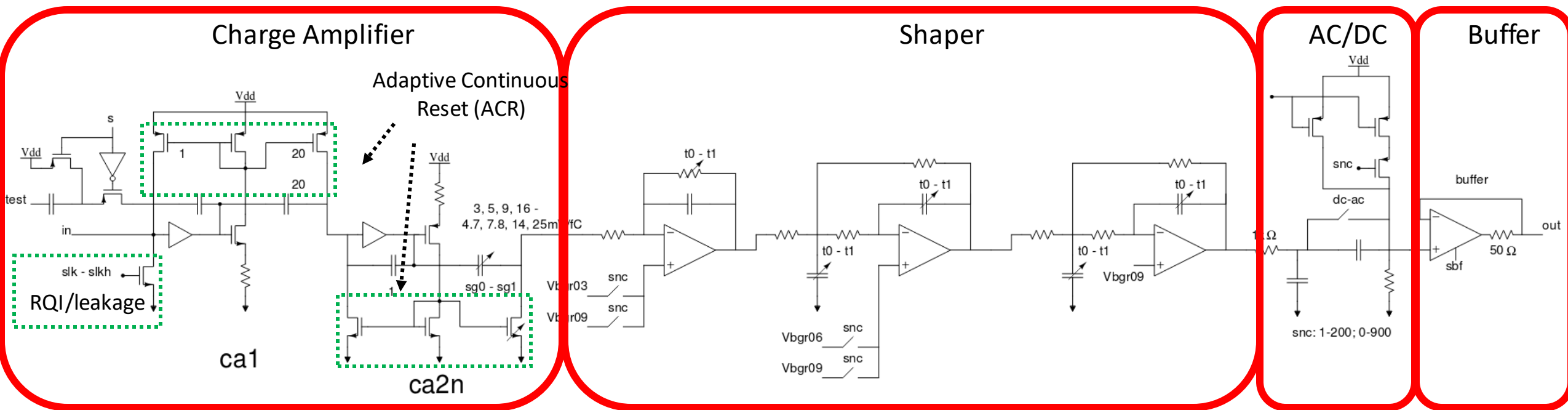
# LArASIC Channel – Simplified block diagram



# Changes between recent versions of the FE ASIC

## P1 (V6)

- 6-bit pulse generator added
- SLKH, i.e., high (10x) Reset-loop Quiescent Current (RQI) added to compensate for saturation effects (aka “Chirping”)
- BGR fix didn’t work → 7% chips don’t start in cold
- RQI subtraction added in CA2 to correct for BL DC for 5nA RQI → CA2 Adaptive Continuous Reset (ACR) non-functional → needs 1GOhm at input
- Transistor sizing similar to V5
- Imperfect PZ cancellation → return to baseline issues

## P2 (V7)

- PA-SH changed to correct return to baseline issue
- Removed RQI subtraction in CA2
- Changed W and L in the ACR of CA1 and CA2
  - {W,L} in ACR CA2, P2 = {8\*W, 8\*L} ACR CA2, P1
- Inter-channel BL variation (geometric dependence) for 200 mV BL option observed due to packaging stress
- Ledge observed only in cold during shower event (after P3 tape-out)
- BGR issue of 7% chips in cold still present

## P3 (V8)

- Geometric dependence for 200 mV baseline mitigated by replacing current biasing with voltage in shaper 1<sup>st</sup> and 2<sup>nd</sup> stages → changes CA2 bias vol.
- Ledge behavior still present in cold
- BGR issue of 7% chips in cold still present

# Outline of Identified problems and simulation methodology

- Identified problems

- Bandgap Voltage Reference (BGR) fails in 7% of the chips
- Ledge effect during shower event



Only in Cold operation

- Simulation procedure



- Model files from foundry used
  - “cmno18\_asp\_v1d2.scs” in BSIM4 (V4.5)
  - Extrapolated for LN and LAr temperatures, outside of guaranteed range
  - Mismatch models only for MOSFETs
- Perform different analysis needed such as DC, AC, stability (STB), noise , transient (with or/and without noise) in nominal, process corners (SS, FF, SF and FS) and Monte Carlo with process variation (PV) and mismatch (MM)
- Schematic level simulations have been shown later

# BGR Problem in P3



 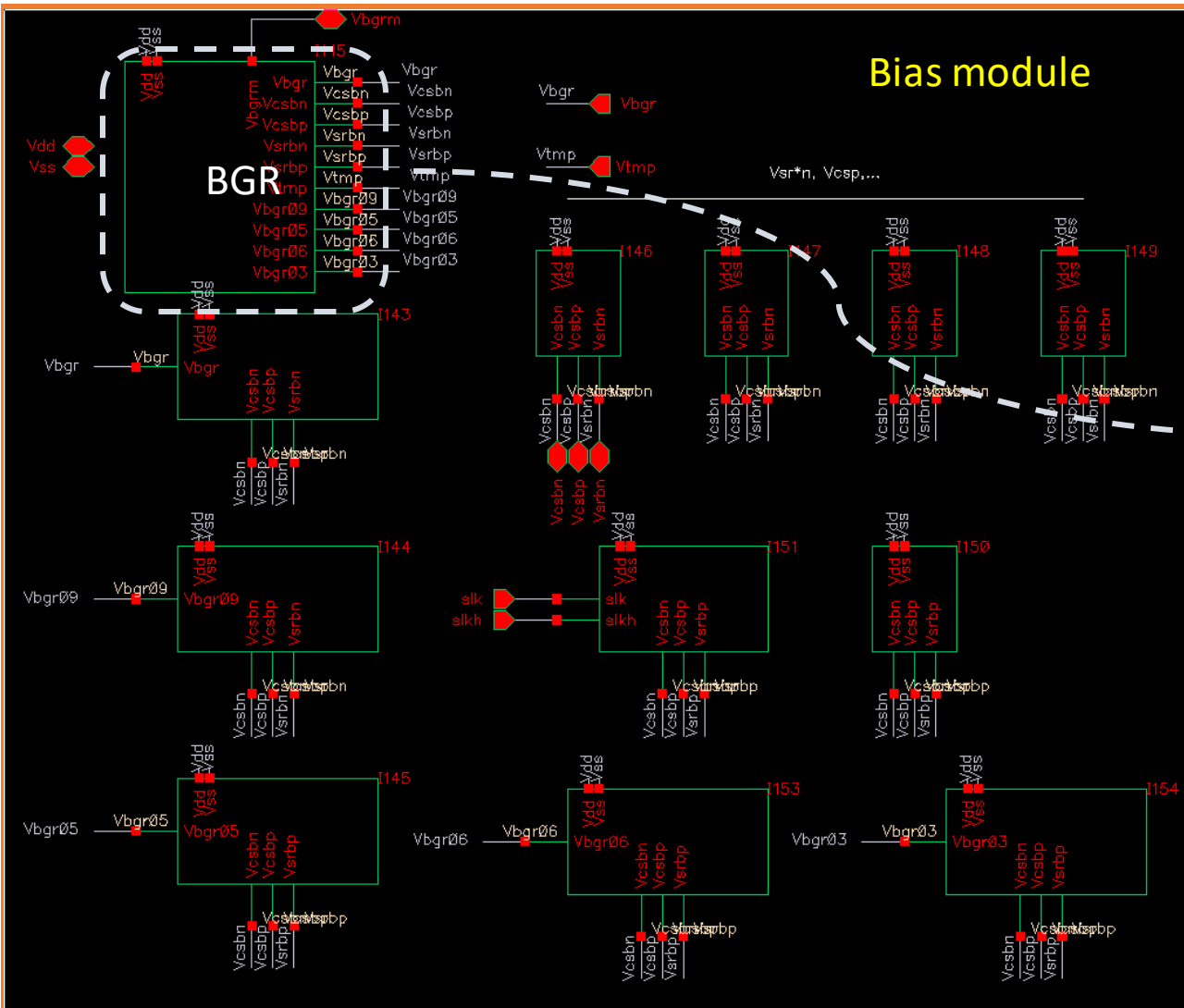
# Bias module based on Bandgap Voltage Reference (BGR)

- Still 7% of the P3 chips doesn't start only in cold → They are currently screened-off



# P3 BGR simulations


Name	Vis	mcparamset
VBGR	<input type="checkbox"/>	6
VBGR	<input type="checkbox"/>	7
VBGR	<input type="checkbox"/>	8
VBGR	<input type="checkbox"/>	9
VBGR	<input type="checkbox"/>	10
VBGR	<input type="checkbox"/>	11
VBGR	<input type="checkbox"/>	12
VBGR	<input type="checkbox"/>	13
VBGR	<input type="checkbox"/>	14
VBGR	<input type="checkbox"/>	15
VBGR	<input type="checkbox"/>	16
VBGR	<input type="checkbox"/>	17
VBGR	<input type="checkbox"/>	18
VBGR	<input type="checkbox"/>	19
VBGR	<input type="checkbox"/>	20
VBGR	<input type="checkbox"/>	21
VBGR	<input type="checkbox"/>	22
VBGR	<input type="checkbox"/>	23
VBGR	<input type="checkbox"/>	24
VBGR	<input type="checkbox"/>	25
VBGR	<input type="checkbox"/>	26
VBGR	<input type="checkbox"/>	27
VBGR	<input type="checkbox"/>	28
VBGR	<input type="checkbox"/>	29
VBGR	<input type="checkbox"/>	30
VBGR	<input type="checkbox"/>	31
VBGR	<input type="checkbox"/>	32
VBGR	<input type="checkbox"/>	33
VBGR	<input type="checkbox"/>	34
VBGR	<input type="checkbox"/>	35
VBGR	<input type="checkbox"/>	36
VBGR	<input type="checkbox"/>	37
VBGR	<input type="checkbox"/>	38
VBGR	<input type="checkbox"/>	39
VBGR	<input type="checkbox"/>	40
VBGR	<input type="checkbox"/>	41
VBGR	<input type="checkbox"/>	42
VBGR	<input type="checkbox"/>	43

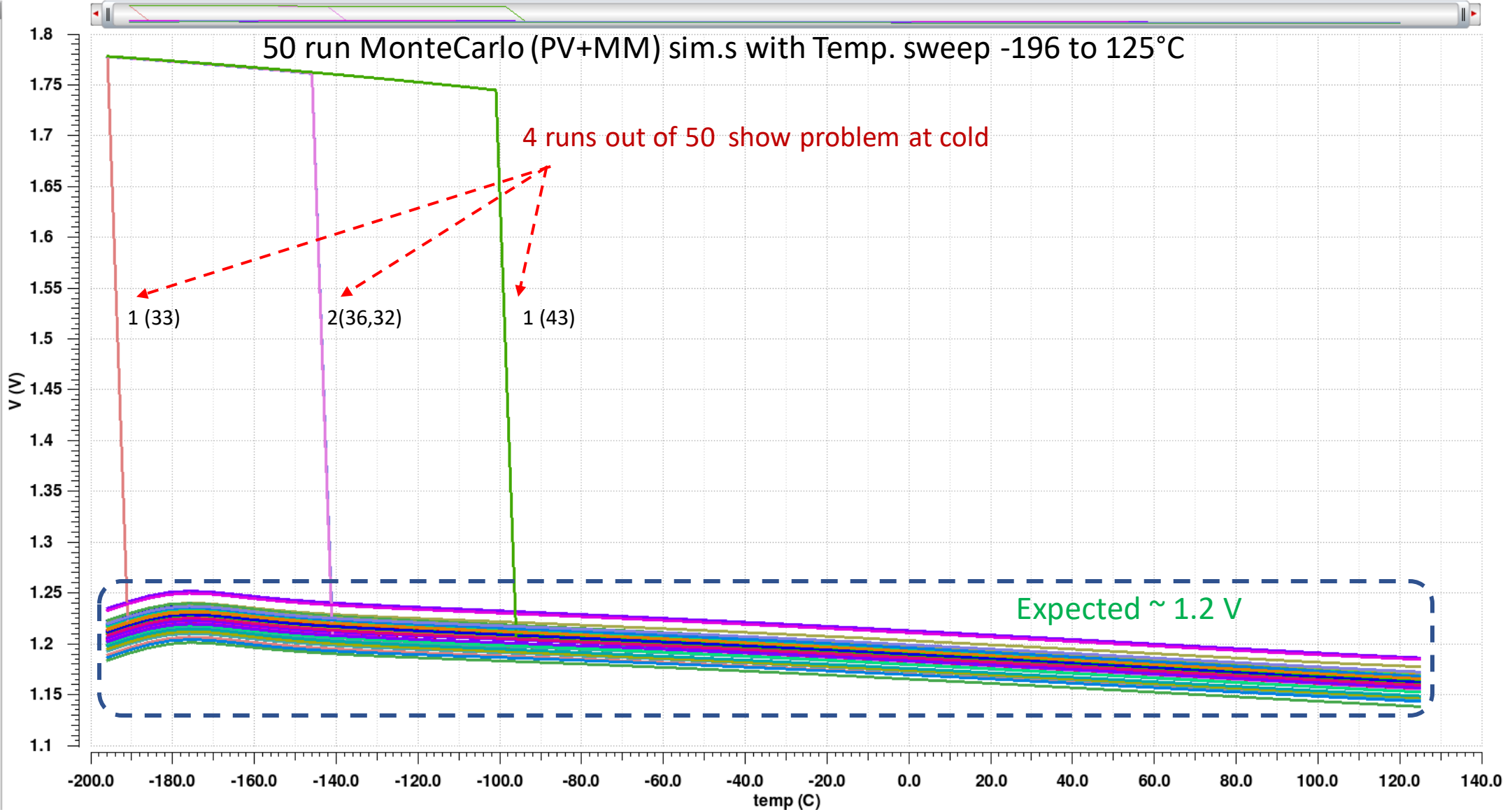

# Start-up sim.s of P3 BGR

Wed Jan 8 11:57:47

Name	Vis	Corner	mcparrn
VT(/Vbgr <sup>r</sup> )			
VT(/Vbgr <sup>r</sup> )		MC_n...m186	50
VT(/Vbgr <sup>r</sup> )		MC_n...m186	49
VT(/Vbgr <sup>r</sup> )		MC_n...m186	48
VT(/Vbgr <sup>r</sup> )		MC_n...m186	47
VT(/Vbgr <sup>r</sup> )		MC_n...m186	46
VT(/Vbgr <sup>r</sup> )		MC_n...m186	45
VT(/Vbgr <sup>r</sup> )		MC_n...m186	44
VT(/Vbgr <sup>r</sup> )		MC_n...m186	43
VT(/Vbgr <sup>r</sup> )		MC_n...m186	42
VT(/Vbgr <sup>r</sup> )		MC_n...m186	41
VT(/Vbgr <sup>r</sup> )		MC_n...m186	40
VT(/Vbgr <sup>r</sup> )		MC_n...m186	39
VT(/Vbgr <sup>r</sup> )		MC_n...m186	38
VT(/Vbgr <sup>r</sup> )		MC_n...m186	37
VT(/Vbgr <sup>r</sup> )		MC_n...m186	36
VT(/Vbgr <sup>r</sup> )		MC_n...m186	35
VT(/Vbgr <sup>r</sup> )		MC_n...m186	34
VT(/Vbgr <sup>r</sup> )		MC_n...m186	33
VT(/Vbgr <sup>r</sup> )		MC_n...m186	32
VT(/Vbgr <sup>r</sup> )		MC_n...m186	31
VT(/Vbgr <sup>r</sup> )		MC_n...m186	30
VT(/Vbgr <sup>r</sup> )		MC_n...m186	29
VT(/Vbgr <sup>r</sup> )		MC_n...m186	28
VT(/Vbgr <sup>r</sup> )		MC_n...m186	27
VT(/Vbgr <sup>r</sup> )		MC_n...m186	26
VT(/Vbgr <sup>r</sup> )		MC_n...m186	25
VT(/Vbgr <sup>r</sup> )		MC_n...m186	24
VT(/Vbgr <sup>r</sup> )		MC_n...m186	23
VT(/Vbgr <sup>r</sup> )		MC_n...m186	22
VT(/Vbgr <sup>r</sup> )		MC_n...m186	21
VT(/Vbgr <sup>r</sup> )		MC_n...m186	20
VT(/Vbgr <sup>r</sup> )		MC_n...m186	19
VT(/Vbgr <sup>r</sup> )		MC_n...m186	18
VT(/Vbgr <sup>r</sup> )		MC_n...m186	17
VT(/Vbgr <sup>r</sup> )		MC_n...m186	16
VT(/Vbgr <sup>r</sup> )		MC_n...m186	15
VT(/Vbgr <sup>r</sup> )		MC_n...m186	14

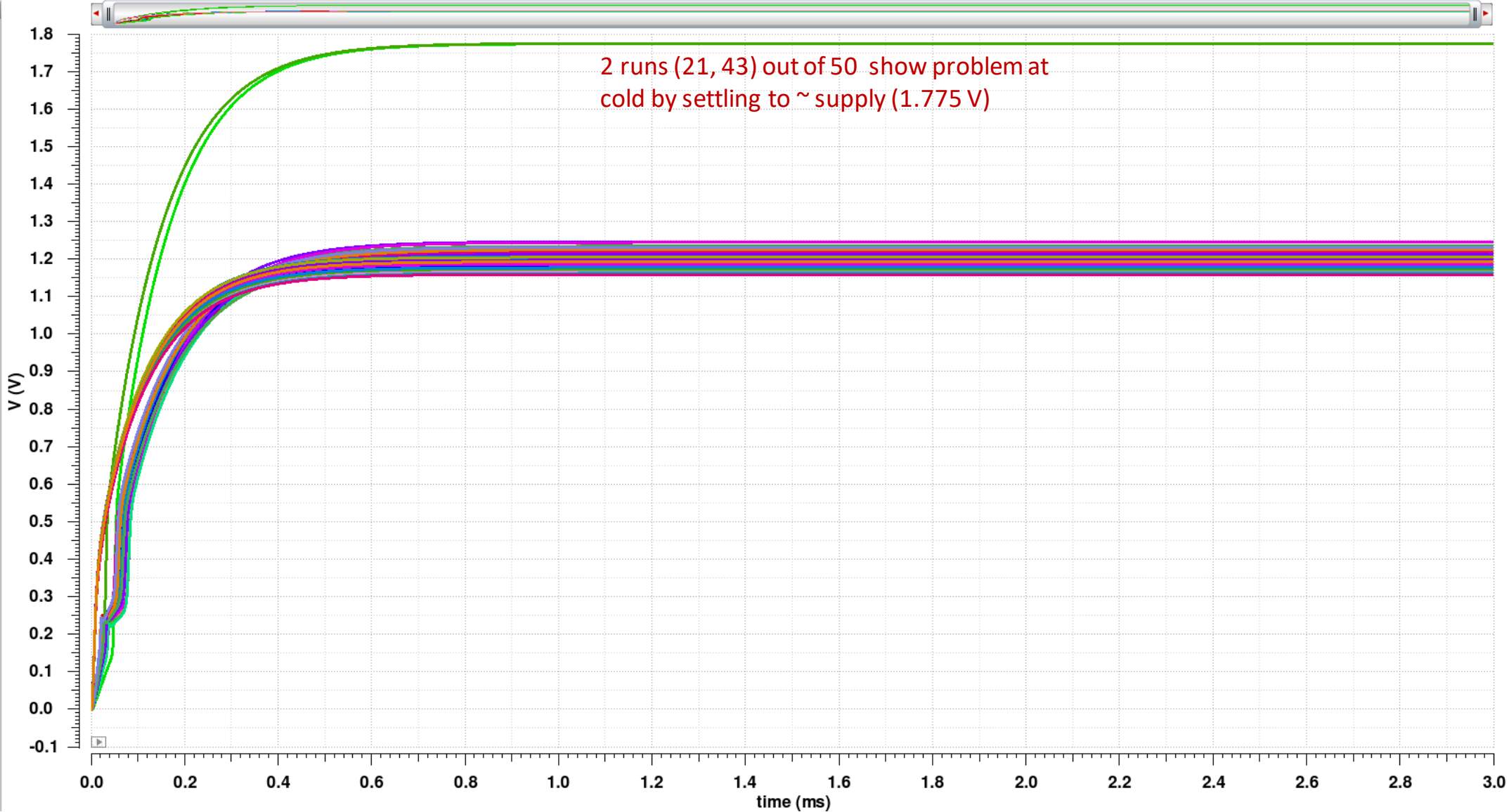

1 $\mu$ s supply ramping; 50 run MC (PV+MM) at LAr and RT

# Ledge Effect in P3

# Ledge effect in LArASIC P3

- Only during cold operation and mostly with shower charge (e.g.  $> 100$  fC for 14 mV/fC setting) for 200 mV baseline setting, LArASIC P2 and P3 outputs of some of the channels saturate and produce ledge characteristic after a delay

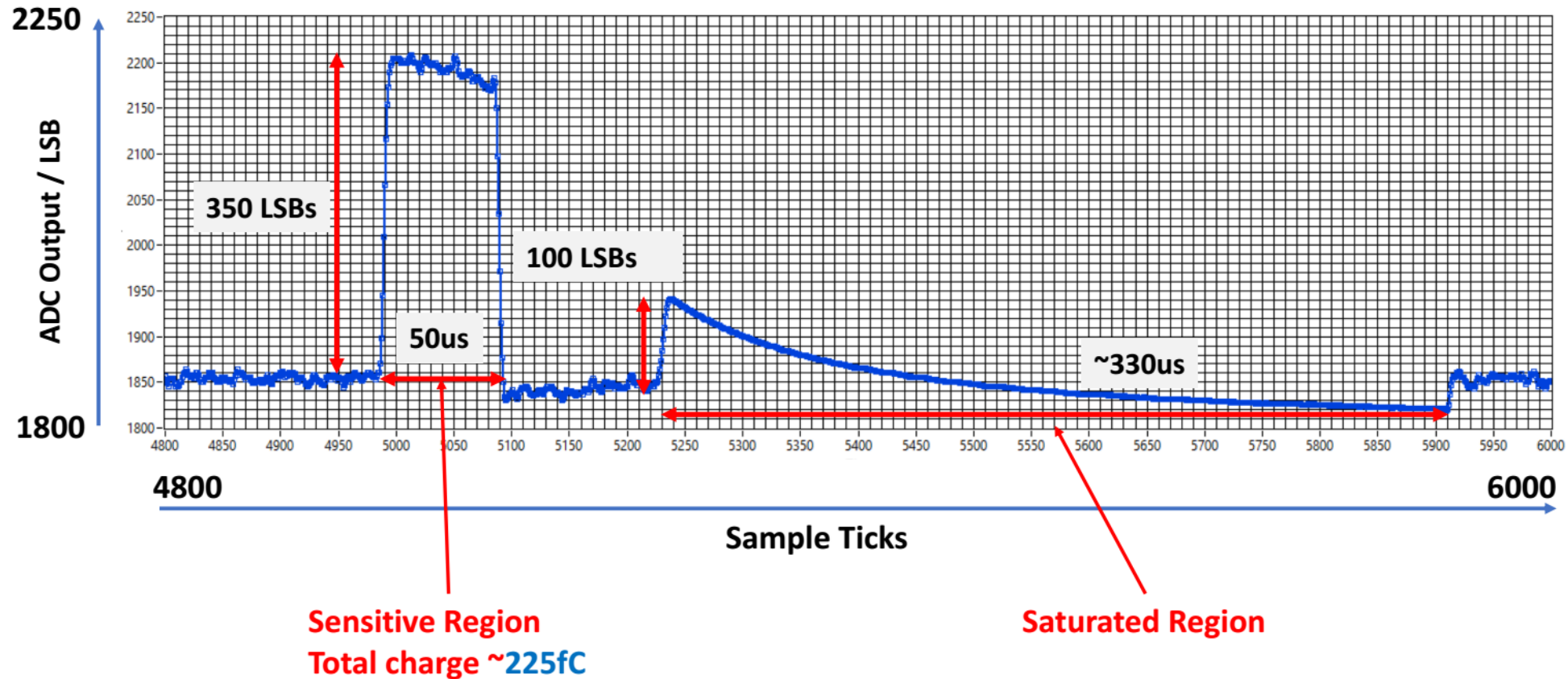



Image from: Study of the “Ledge” effect in protoDUNE readout, Hucheng Chen, et al.

# Simulation of shower event at LN : 500 fC input for 50 $\mu$ s

Ledge effect only observed with new models (BSIM4) and not with old (BSIM3)


vOut\_NBL  
 vOut\_NBL  
 vOut\_NBL  
 TT\_new\_m196  
 TT\_m196

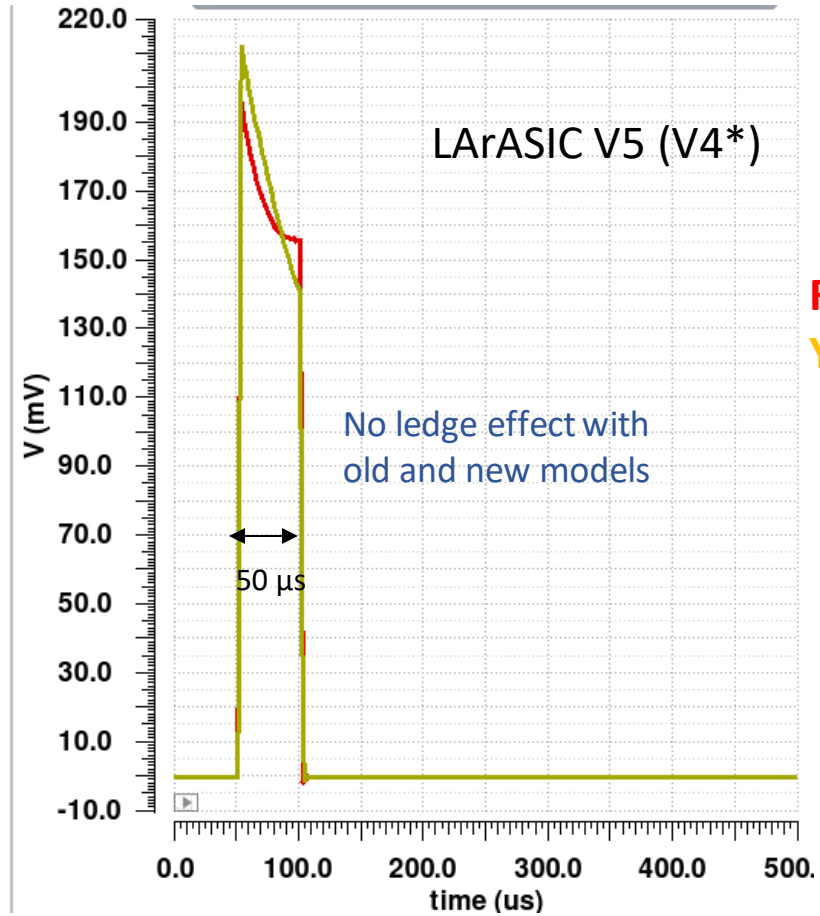tPeak = 1  $\mu$ s  
 Leakage = 500 pA  
 BL = 200 mV  
 Gain = 14 mv/fC  
 Cdet = 150 pF



Red: old model  
 Yellow: new model

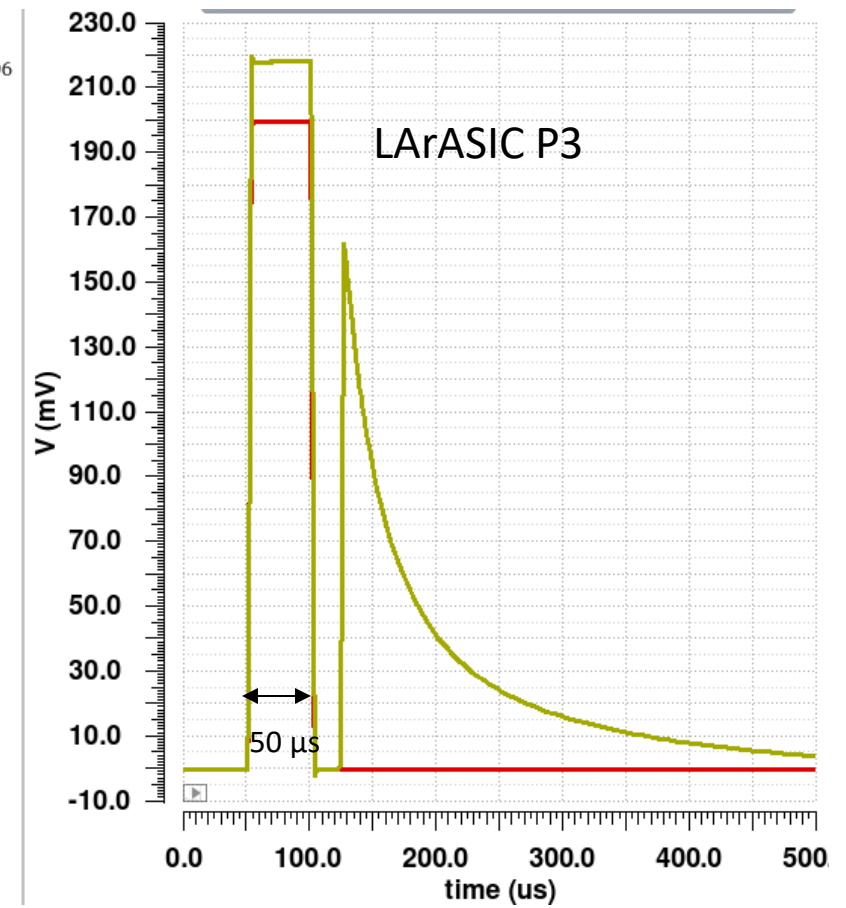vOut\_NBL  
 vOut\_NBL  
 vOut\_NBL  
 TT\_new\_m196  
 TT\_m196




TT\_m196  $\rightarrow$  rf018.scs is BSIM3 (V3.24)  $\sim$ 17k lines  
 TT\_new\_m196  $\rightarrow$  cmno18\_asp\_v1d2.scs is BSIM4 (V4.5)  $\sim$ 38k lines

} 180 nm TSMC tech. model files

# Origin of ledge effect

- Adaptive Continuous Reset(ACR) network in the ca2n resized from V5(V4\*)/V6(P1) moving to V7(P2)/V8(P3) to improve pole-zero cancellation (baseline restoration)
- Width and Length of the transistors in ACR increased by 8 times in P3 compared to V5, increased gate cap. by ~64 times, making the loop unstable, causing ledge

Ledge effect origin fully understood

 



Both W and L increased by 8 times

# Other Performance Metrics of P3


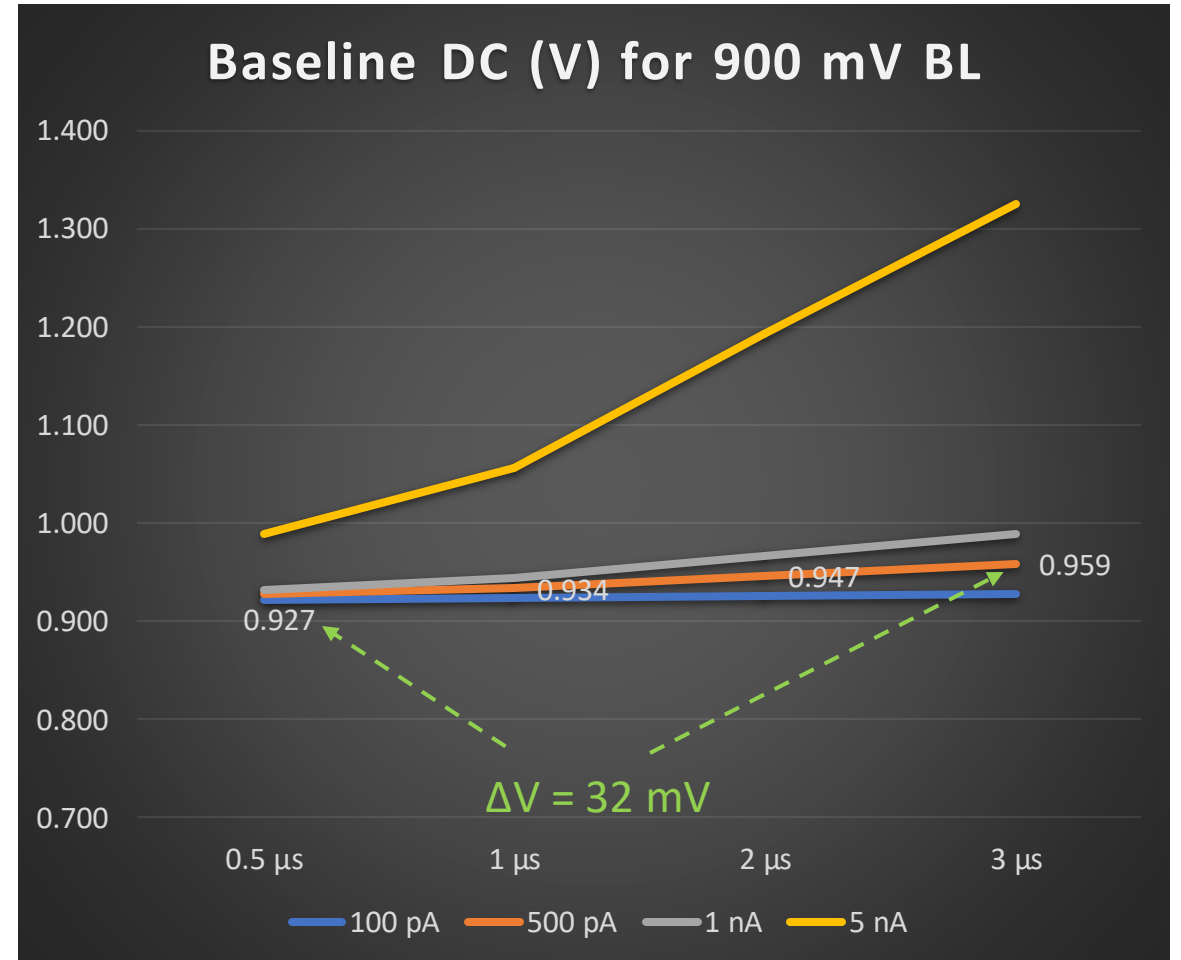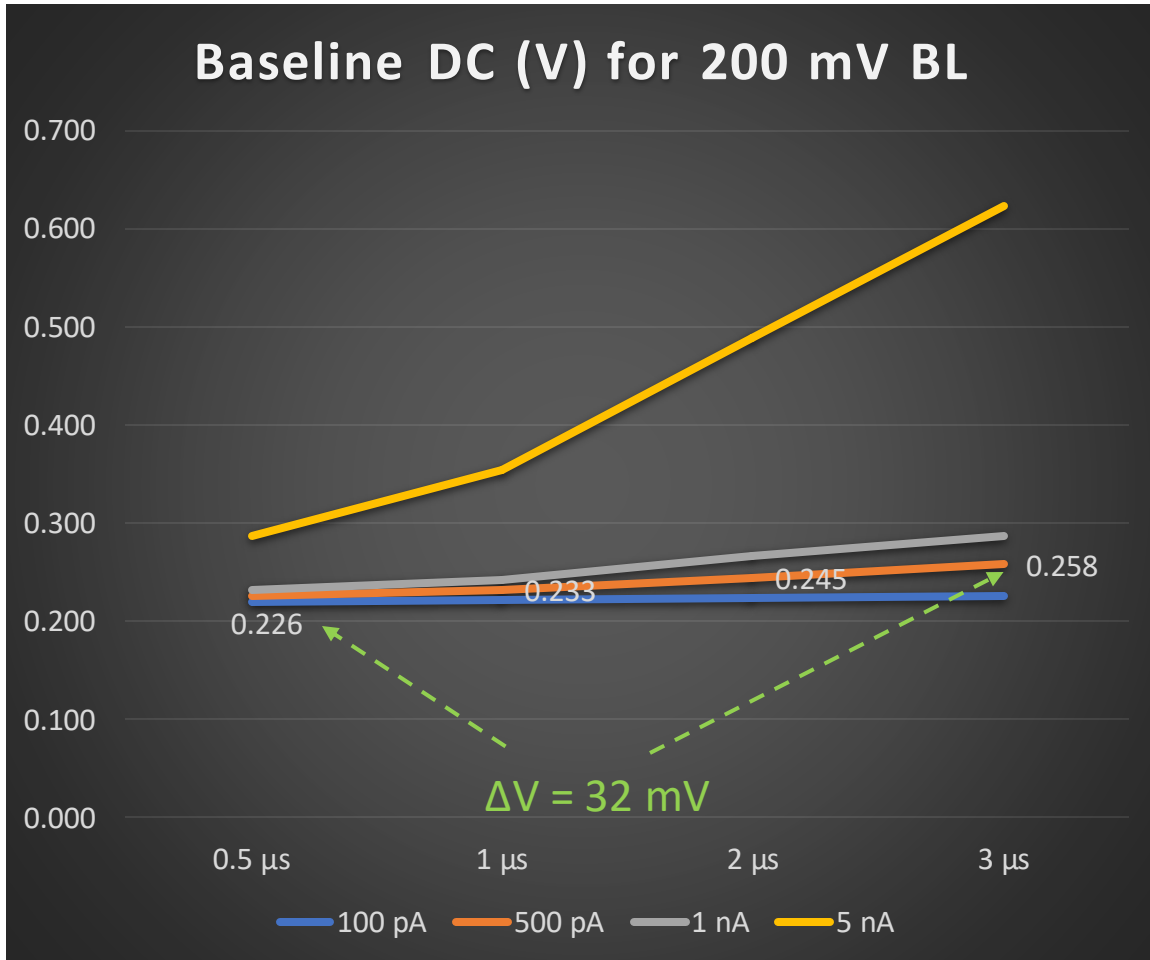
# Simulations of P3 channel baseline DC shift for different settings

\* Setting: BL = 200/900 mV, Gain = 14 mV/fC, Cdet = 150 pF





RQI (leakage) setting of 500 pA mostly used and 5 nA is not needed  
Baseline shift reduces signal swings

# P3 ASIC baseline DC variation in LN – Measurement of 171 chips, 2736 channels

Setting: BL = 200/900 mV, Gain = 14 mV/fC, T<sub>p</sub> = 2 us, DC, Buffer on, 500pA.

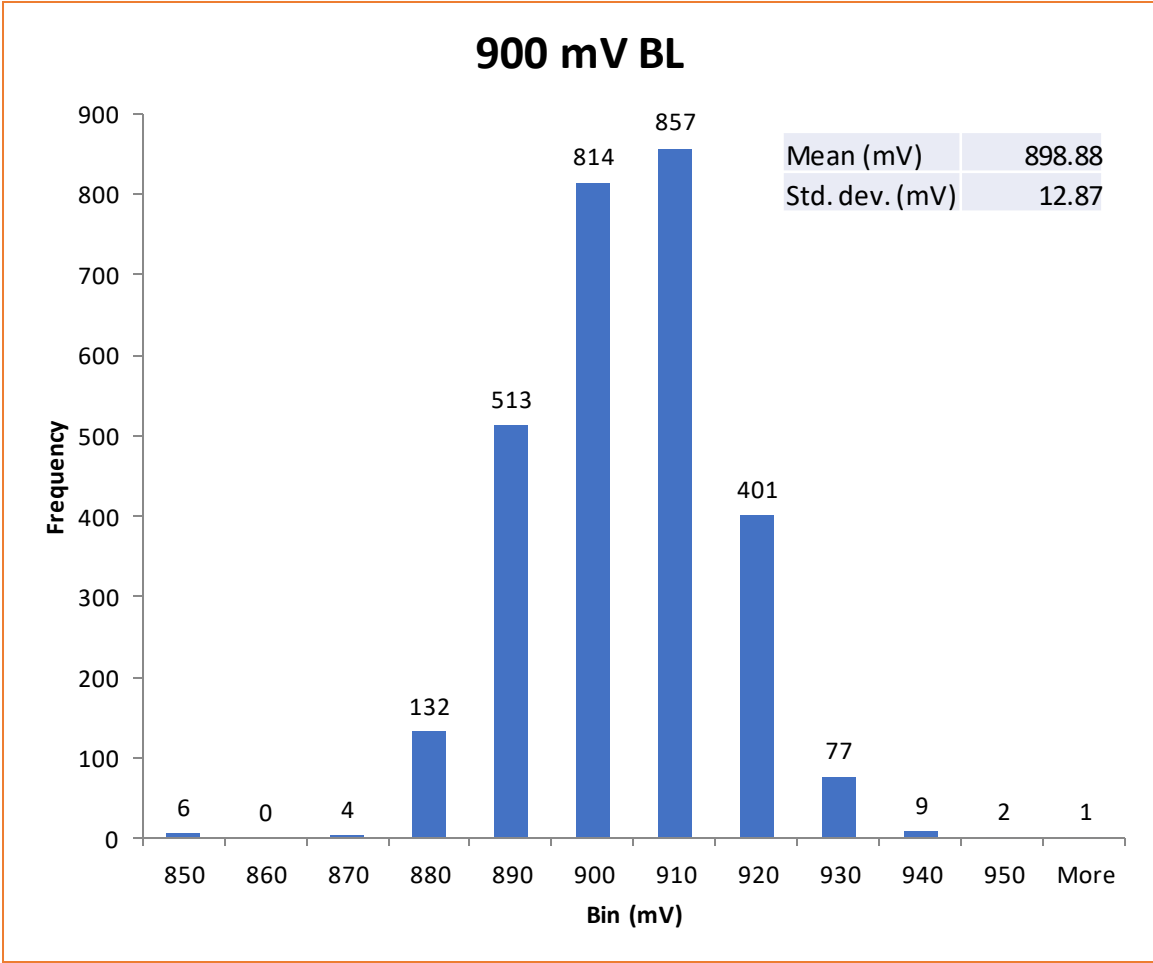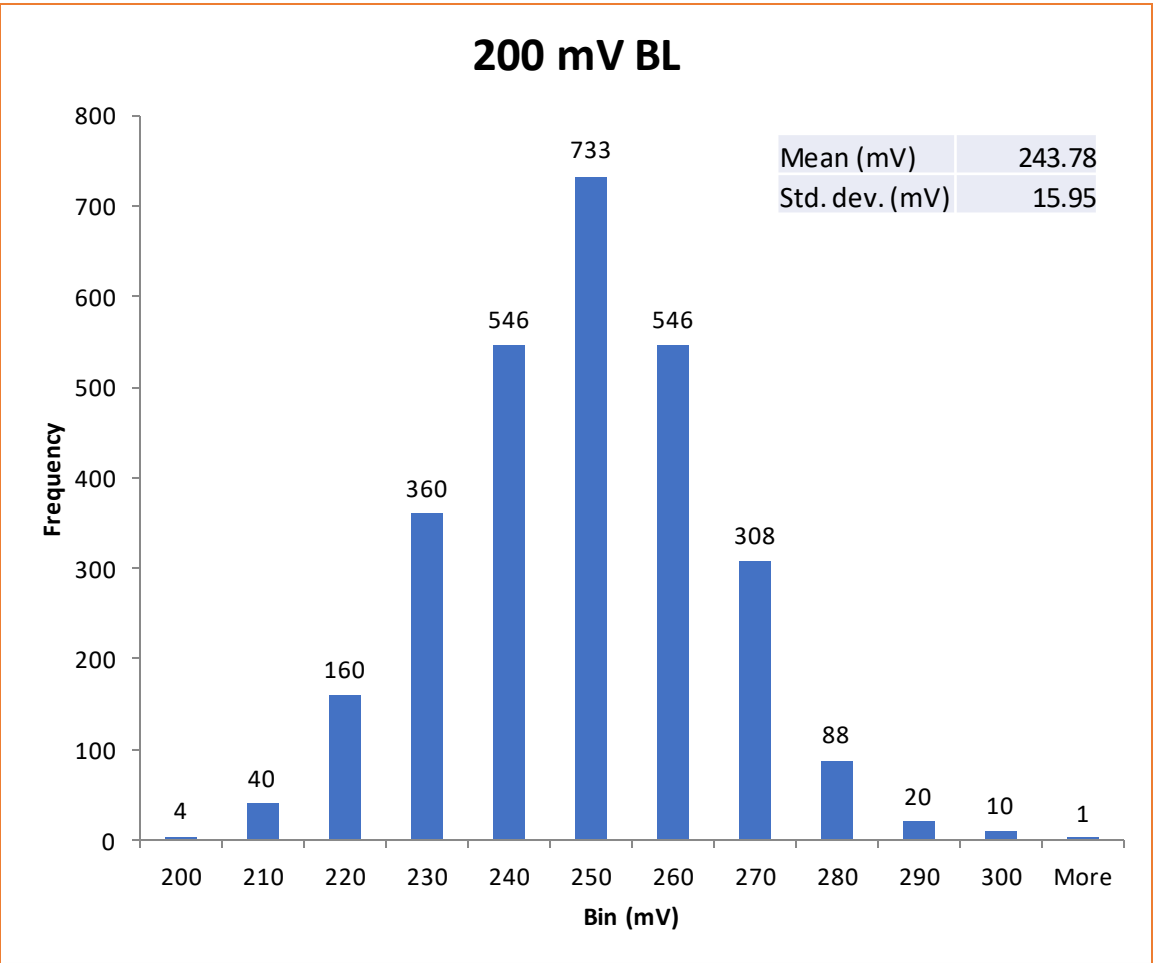1.6% had unresponsive channels and 4.79% did not respond after a power cycle in LN





# P3 FE ASIC baseline DC variation in LN – MC simulations

100 run MC simulations (PV+MM) at schematic level

Setting: BL = 200/900 mV, Gain = 14 mV/fC,  $T_p = 2 \mu s$ , DC coupling, Buffer not used, 500pA,  $C_{det} = 150 \text{ pF}$

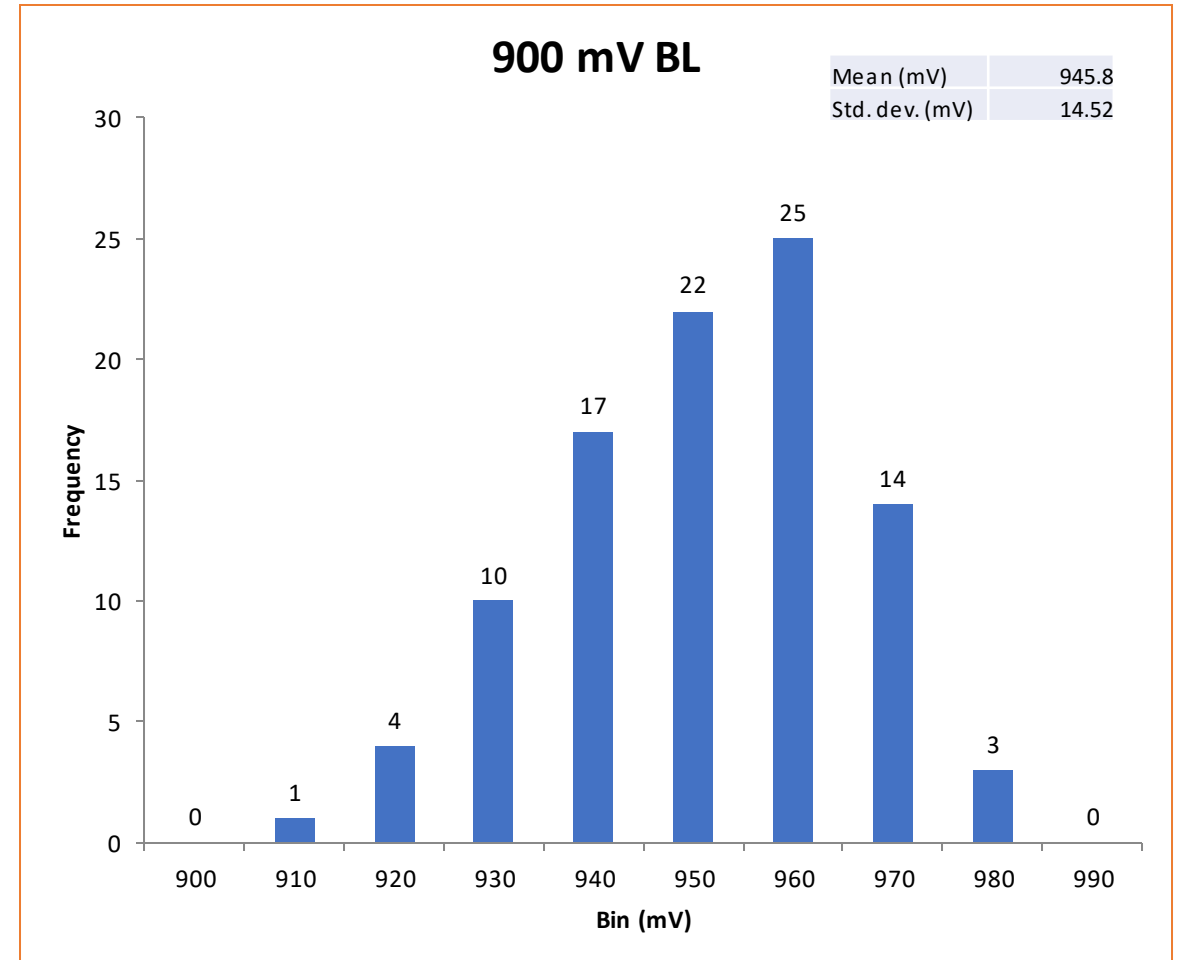
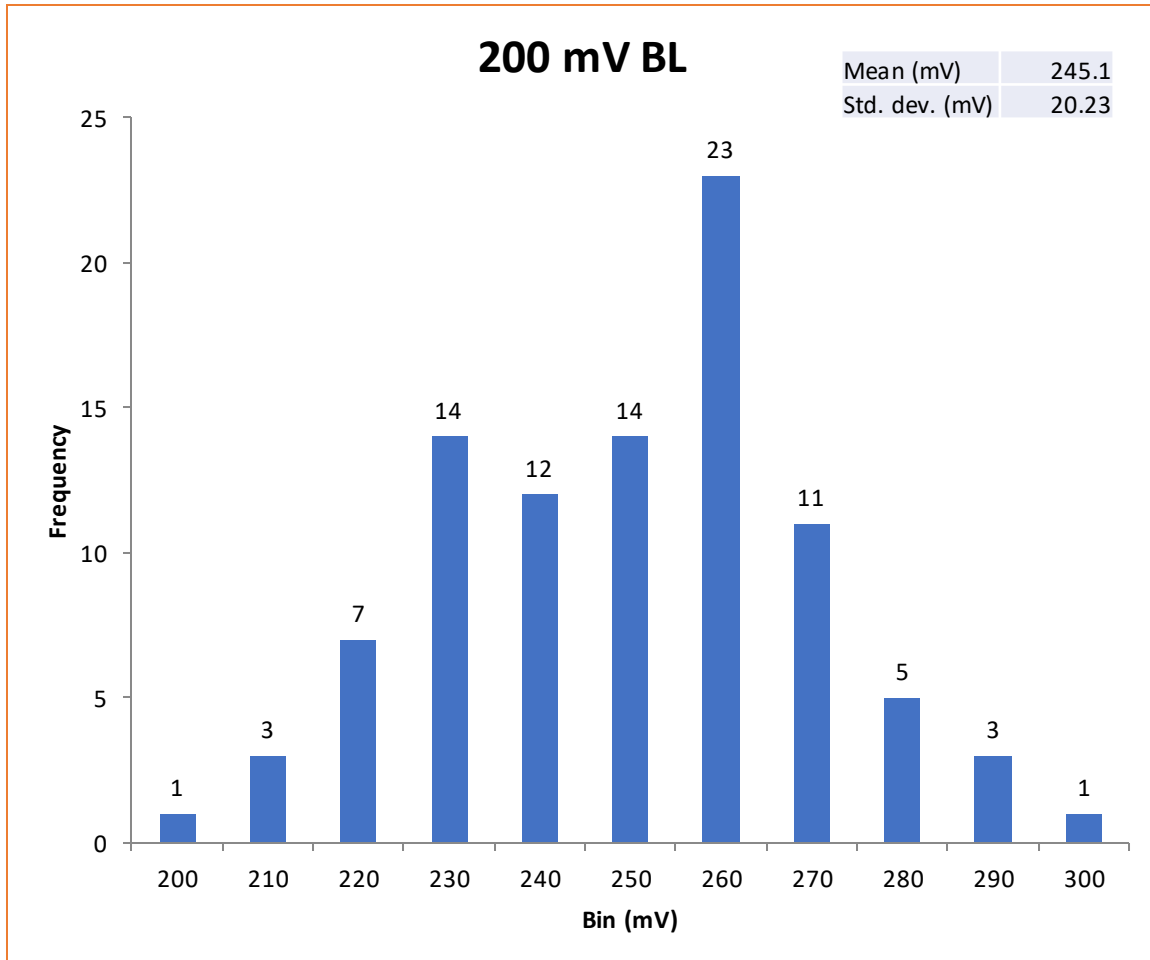
Bandgap reference voltage problem (1.78 V instead of 1.2 V) in 6% (200 mV BL) and 4% (900 mV BL) simulation runs



Close to measurements
 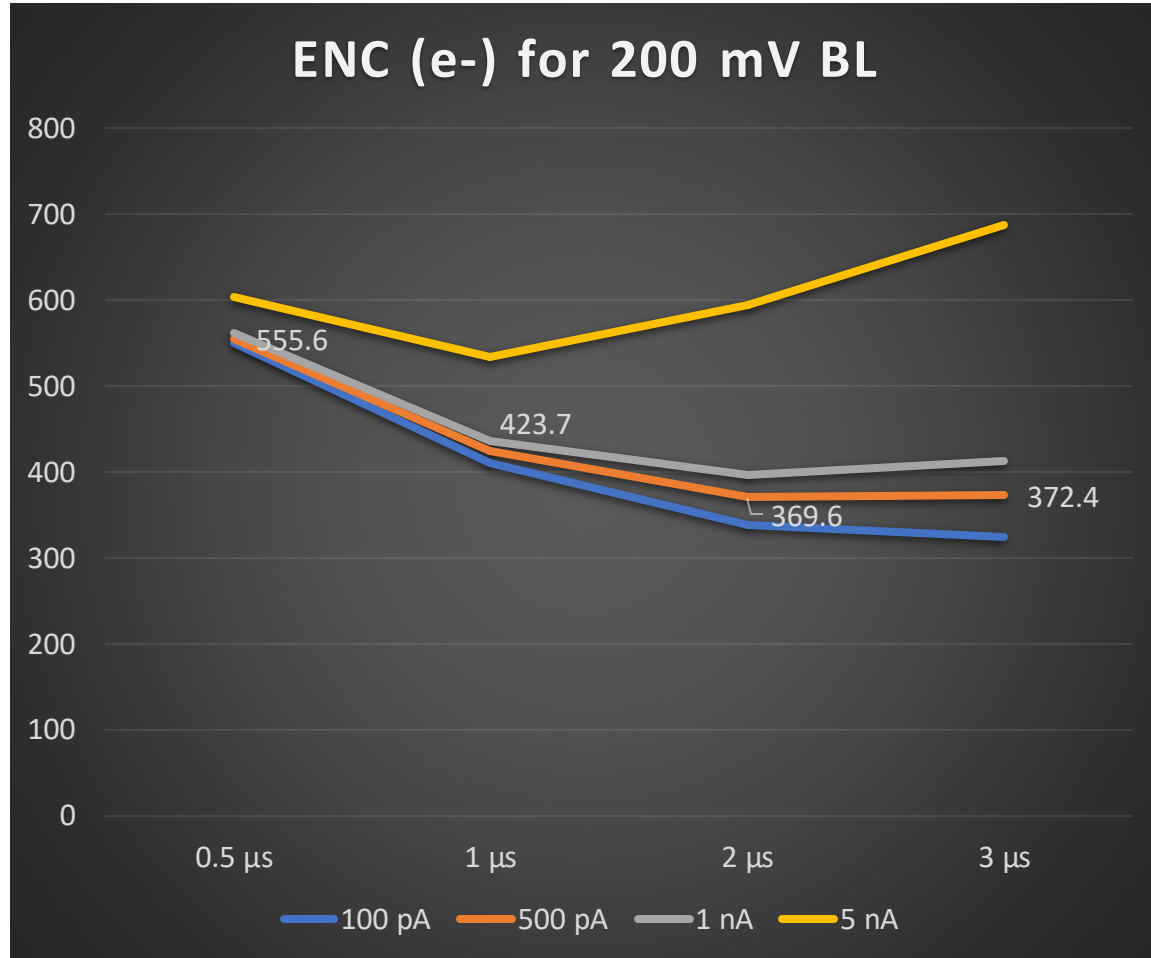
# Simulations of P3 channel ENC


Setting: BL = 200/900 mV, Gain = 14 mV/fC, Cdet = 150 pF




# P3 Simulation results – Linearity

Setting: BL = 200 mV, Gain = 14 mV/fC,  $T_p = 2 \mu s$ , 500pA, Cdet = 150 pF

## Output voltage vs Input charge

 


## Residual Plot

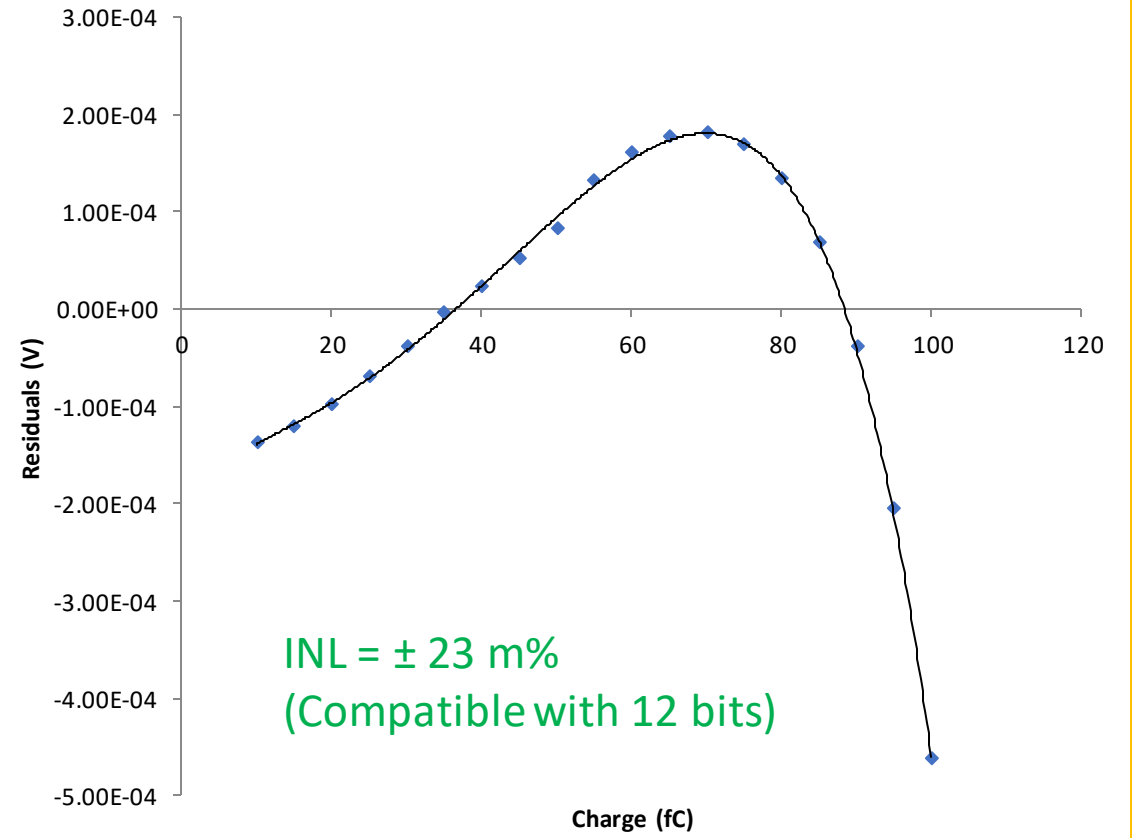


# Single-ended output buffer linearity

## Output voltage vs Input voltage

 

## Residual Plot

 

INL =  $\pm 14 \mu\%$  (Typical)

# LArASIC P4 Development

- Towards a robust design

## Required Improvements for New FE ASIC (P4)

- Required
  - Address bandgap voltage reference failures happening in ~7% of the chips at cold
  - Ledge effect mitigation during shower events up to 500 fC input charge
  - Implement single ended to differential buffer matching with ADC spec.s
- Additional
  - Decreasing baseline shift for different settings




# BGR Problem Mitigation in P4


# Mitigation of Bandgap Reference problem with schematic modifications for P4

In all the previous versions of BGR, bias of BGR was derived from BGR → Problem


We decoupled it

 
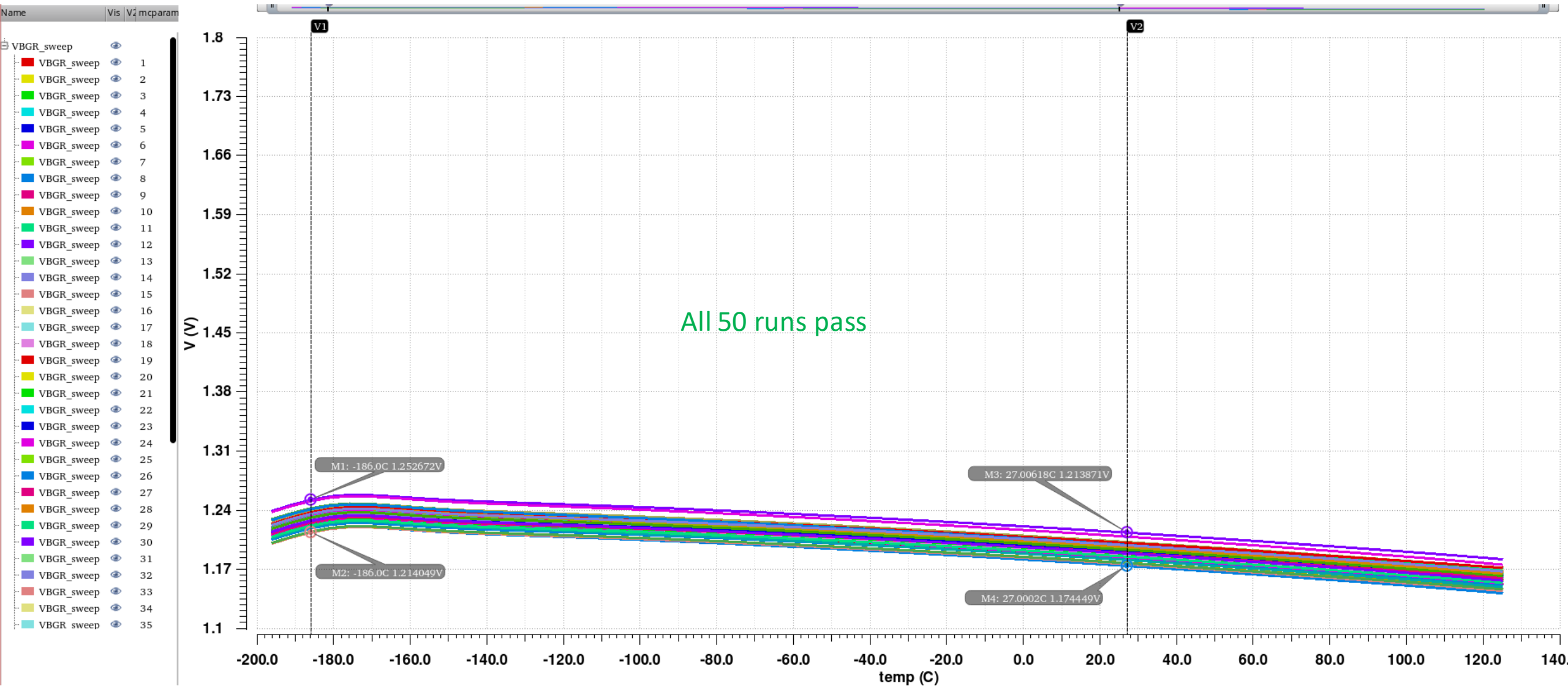
# 50 run MC (PV+MM) sim.s with Temp. sweep -196 to 125°C of proposed BGR



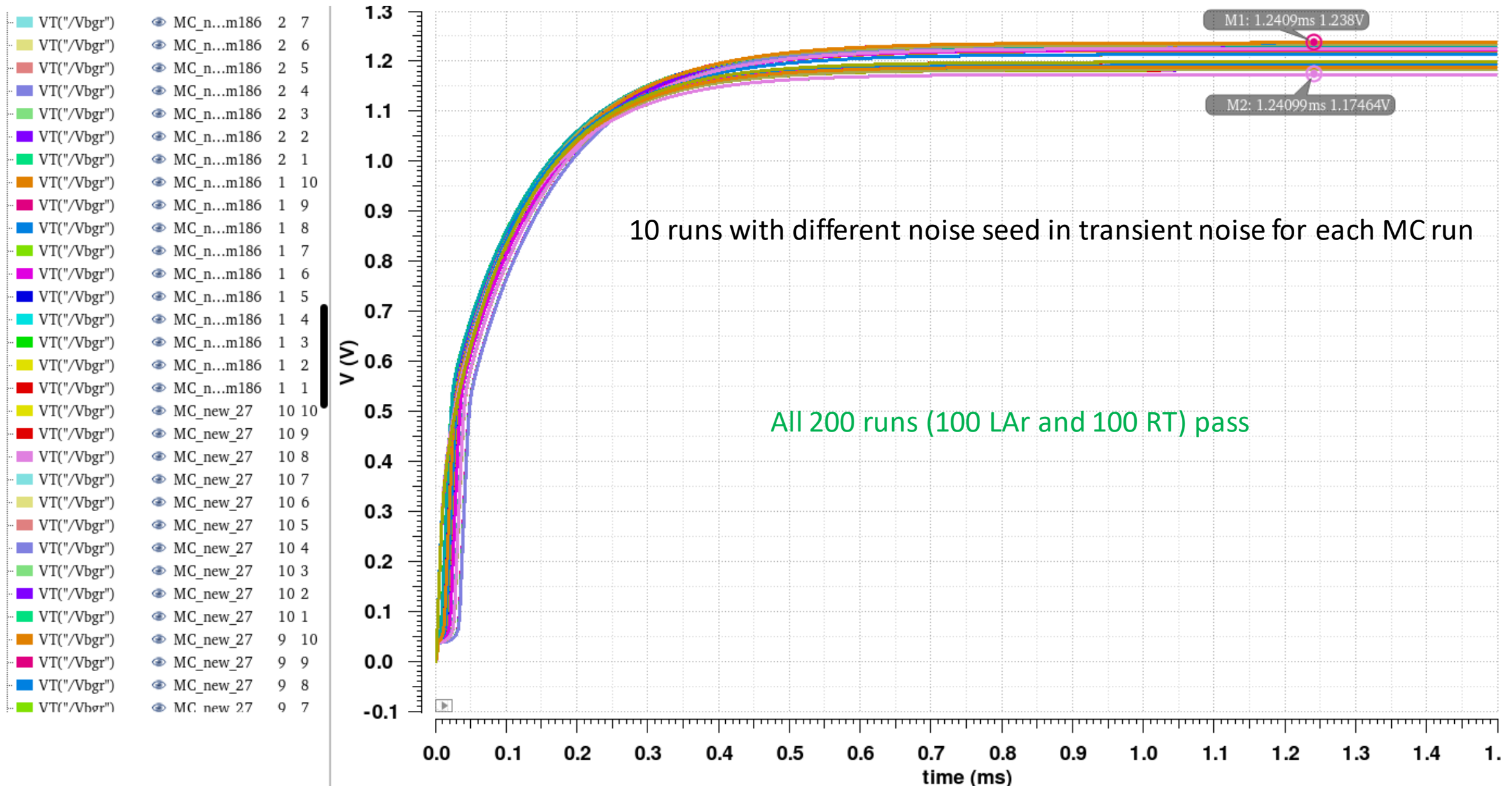
# Start-up sim.s of proposed BGR with $1\mu\text{s}$ supply ramping; 10 run MC (PV+MM) at LAr and RT



# Ledge Effect Mitigation in P4

 
# Proposed mitigation of Ledge Effect

- After multiple simulations the optimal resizing factor was chosen to be 3x instead of 8x
  - Capacitance increases by factor 9, not 64
  - Mitigates ledge effect
  - Pole-zero cancellation similar to P3




Both W and L increased by 3 times instead of 8
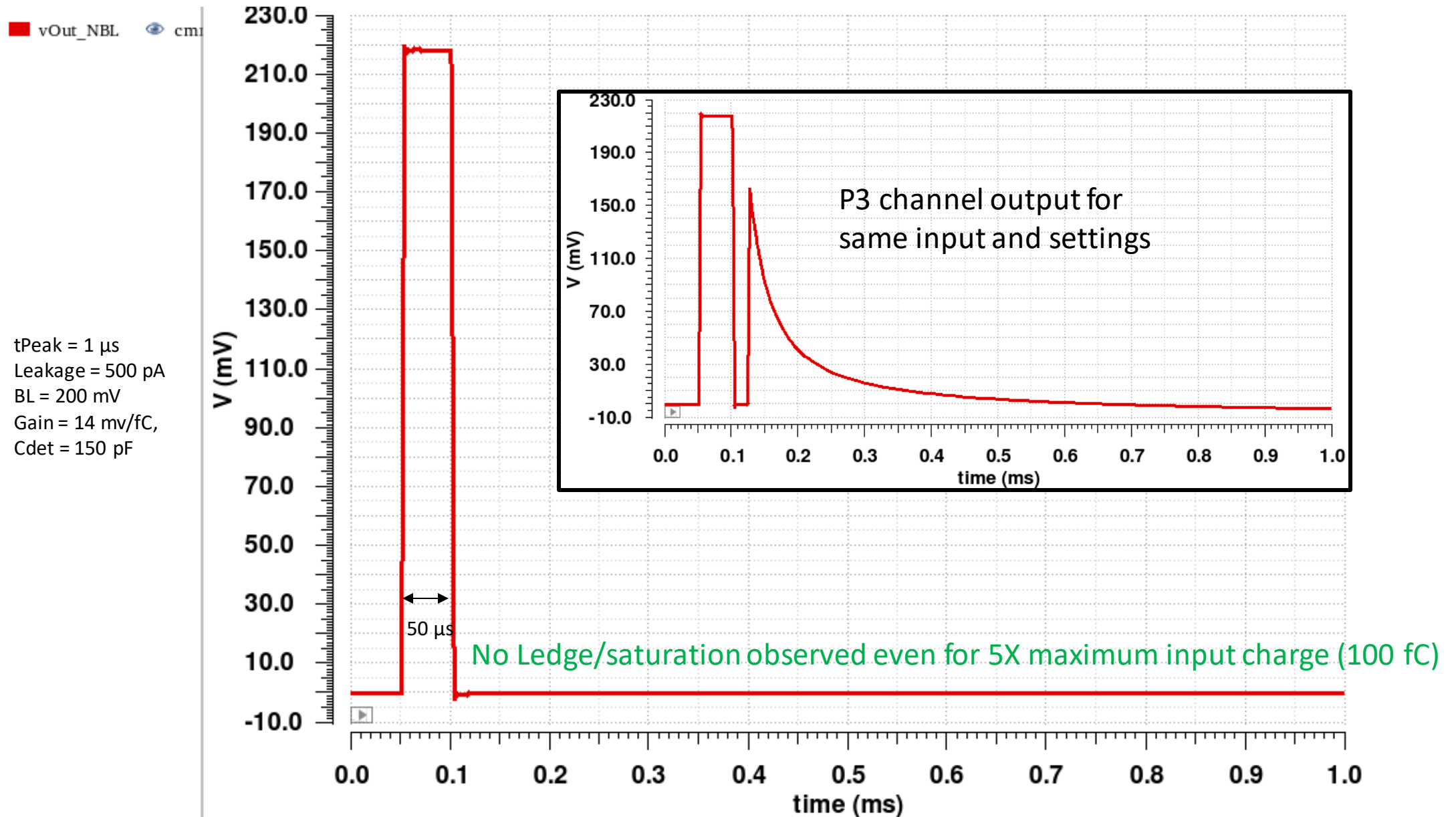
# Simulations of shower event at LN for P4 : 500 fC input for 50 $\mu$ s


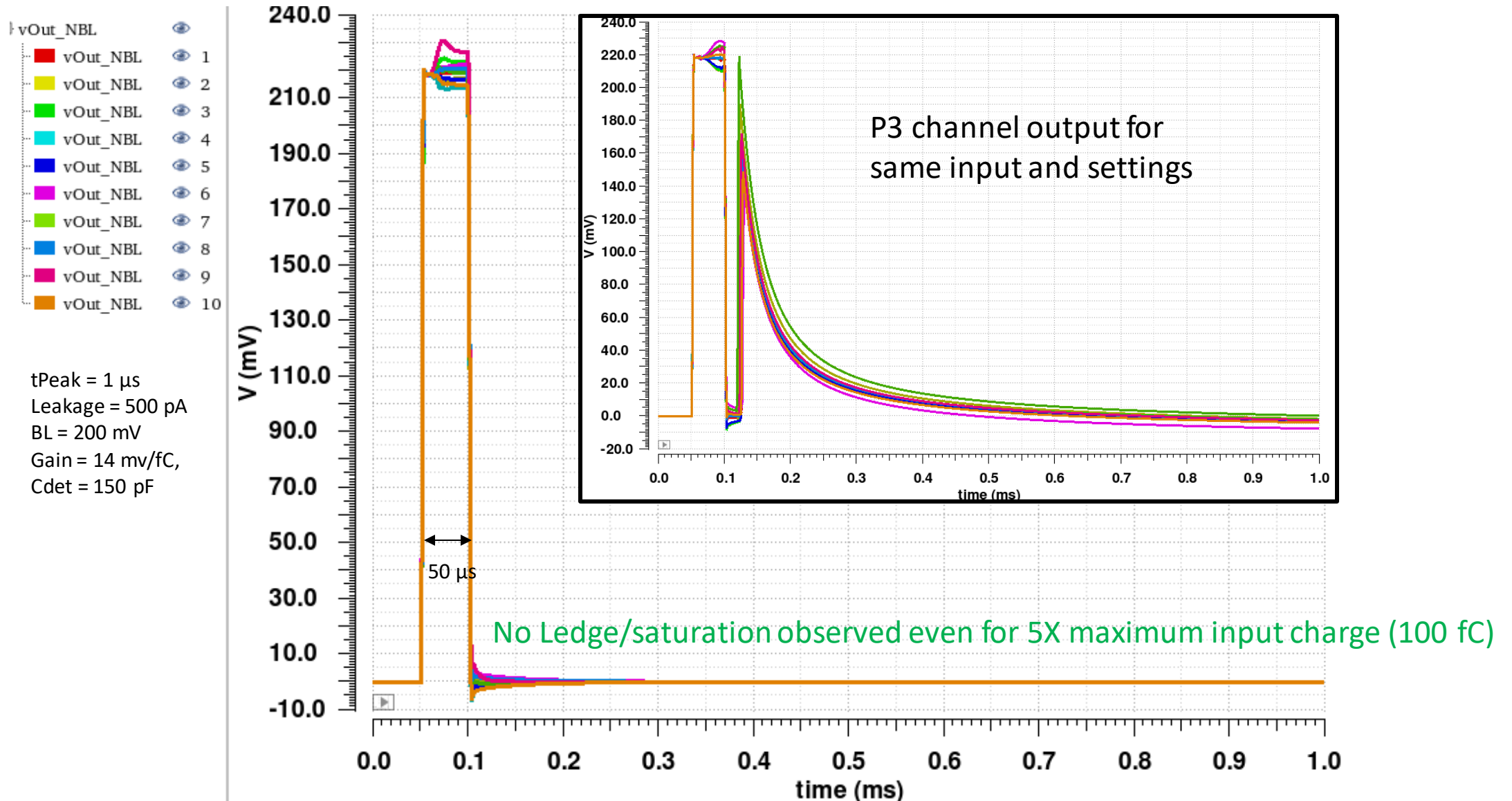
# Monte-Carlo simulation of shower event at LN for P4 : 500 fC input for 50 $\mu$ s


10 run with process and mismatch at schematic level





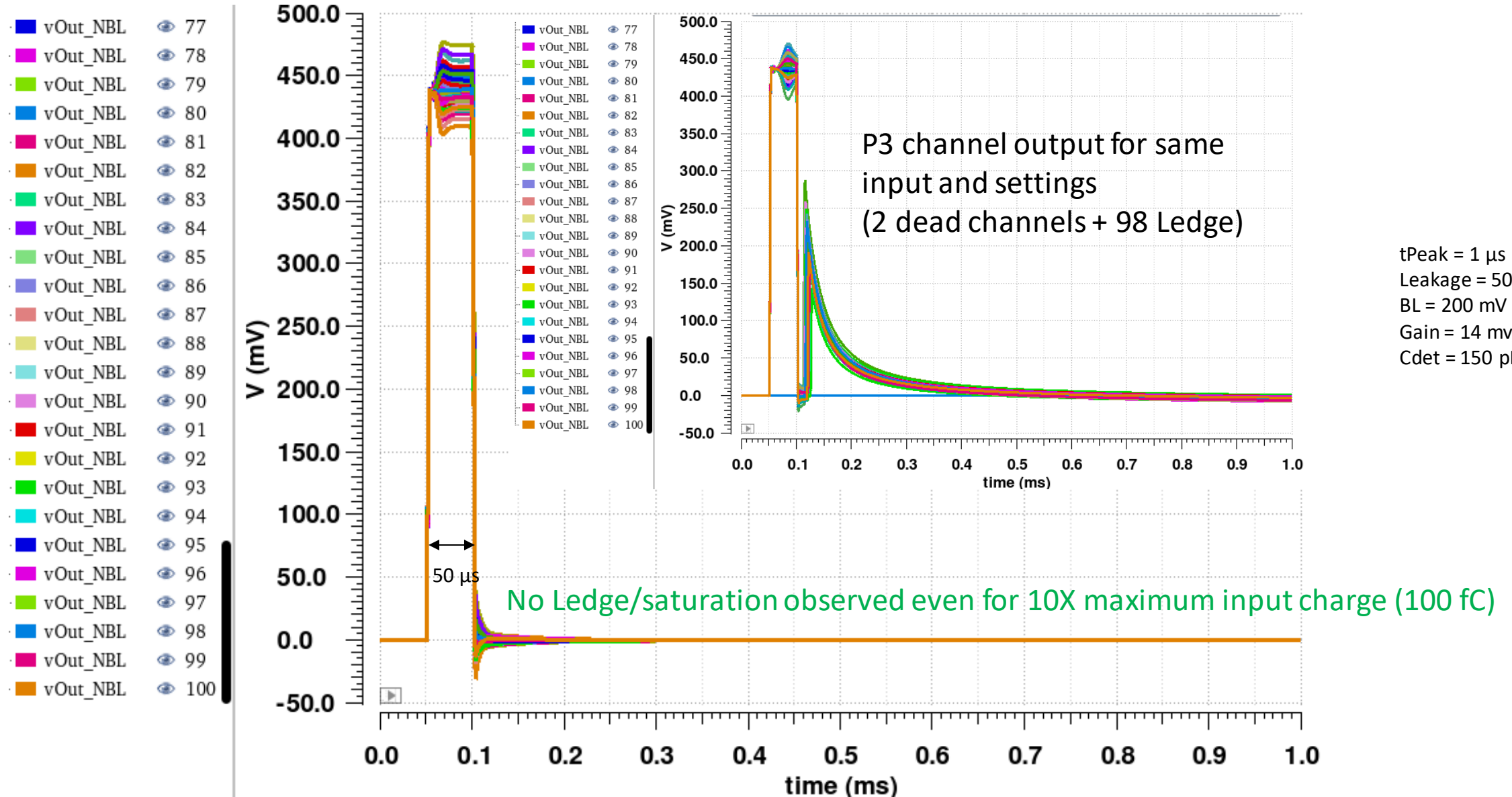
# Monte-Carlo simulation of shower event at LN for P4 : 1 pC input for 50 $\mu$ s

100 run with process and mismatch at schematic level



# Baseline DC Shift Improvement in P4
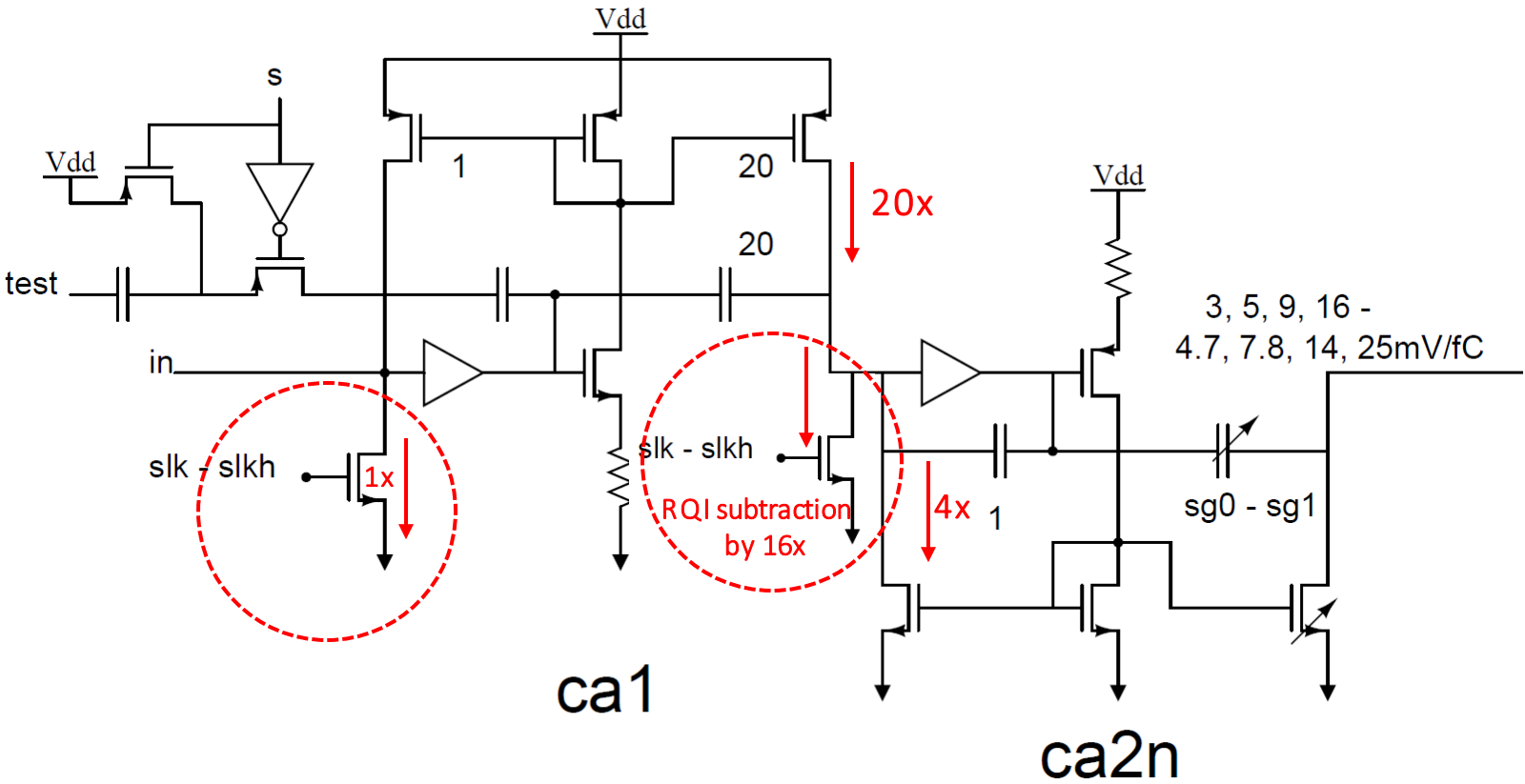
# Proposed mitigation of baseline shift for different settings





- RQI subtraction improves baseline shift
- A factor of 16x RQI is optimal

- Previously in P1, all the RQI was completely subtracted (20x) in P1, which incapacitates adaptive continuous reset loop (leakage). Hence necessitating 1 GΩ resistor at input to make the loop work.
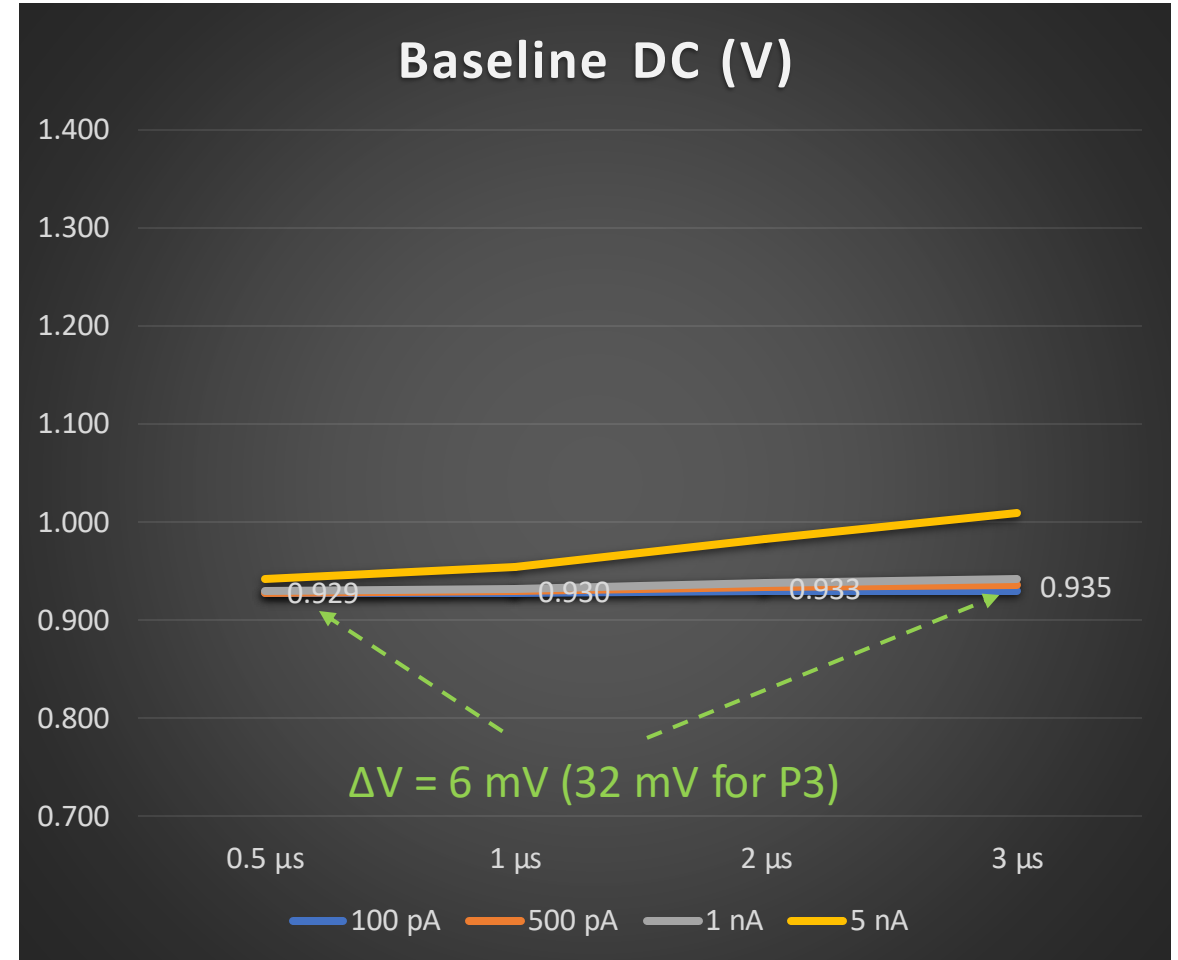 
# Baseline shift for different settings with Proposed modifications

Setting: BL = 200/900 mV, Gain = 14 mV/fC, Cdet = 150 pF



Baseline shift improved → Maximizes signal swings


# Other Performance Metrics of P4

# Proposed P4 FE ASIC Baseline DC Variation in LN – MC simulations


100 run MC simulations (PV+MM) at schematic level

Setting: BL = 200/900 mV, Gain = 14 mV/fC,  $T_p = 2 \mu s$ , DC, Buffer not used, 500pA

### 200 mV BL

 



### 900 mV BL

 

Slightly better than P3
  
# Simulated ENC of the proposed P4 channel

Setting: BL = 200/900 mV, Gain = 14 mV/fC, Cdet = 150 pF




ENC almost similar to P3


# Proposed P4 simulation results – Linearity

Setting: BL = 200 mV, Gain = 14 mV/fC, T<sub>p</sub> = 2 us, 500pA, C<sub>det</sub> = 150 pF
 
## Output voltage [mV] vs Input charge [fC]



## Residual Plot

 




# Single-ended to Differential Converter (SDC) buffer


- Two options

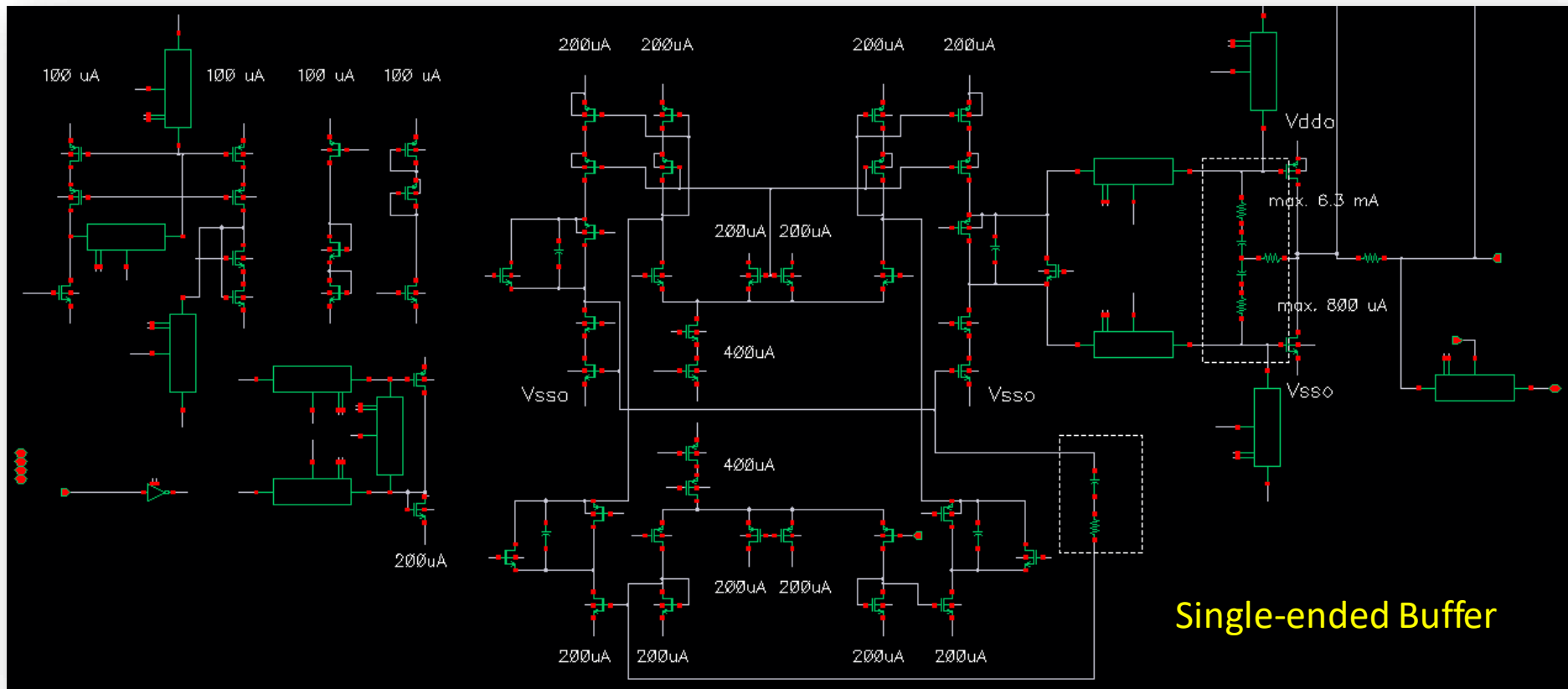1. Porting the SDC design present in cold ADC (65 nm)  $\rightarrow V_{dd} = 2.25\text{ V}$
2. Based on single-ended buffer core
  - Already present in 180 nm, highly linear and silicon-proven rail-to-rail operation
  - Need to modify for differential output and qualify with simulations
  - Addition of Common-Mode Feedback Circuit (CMFB)


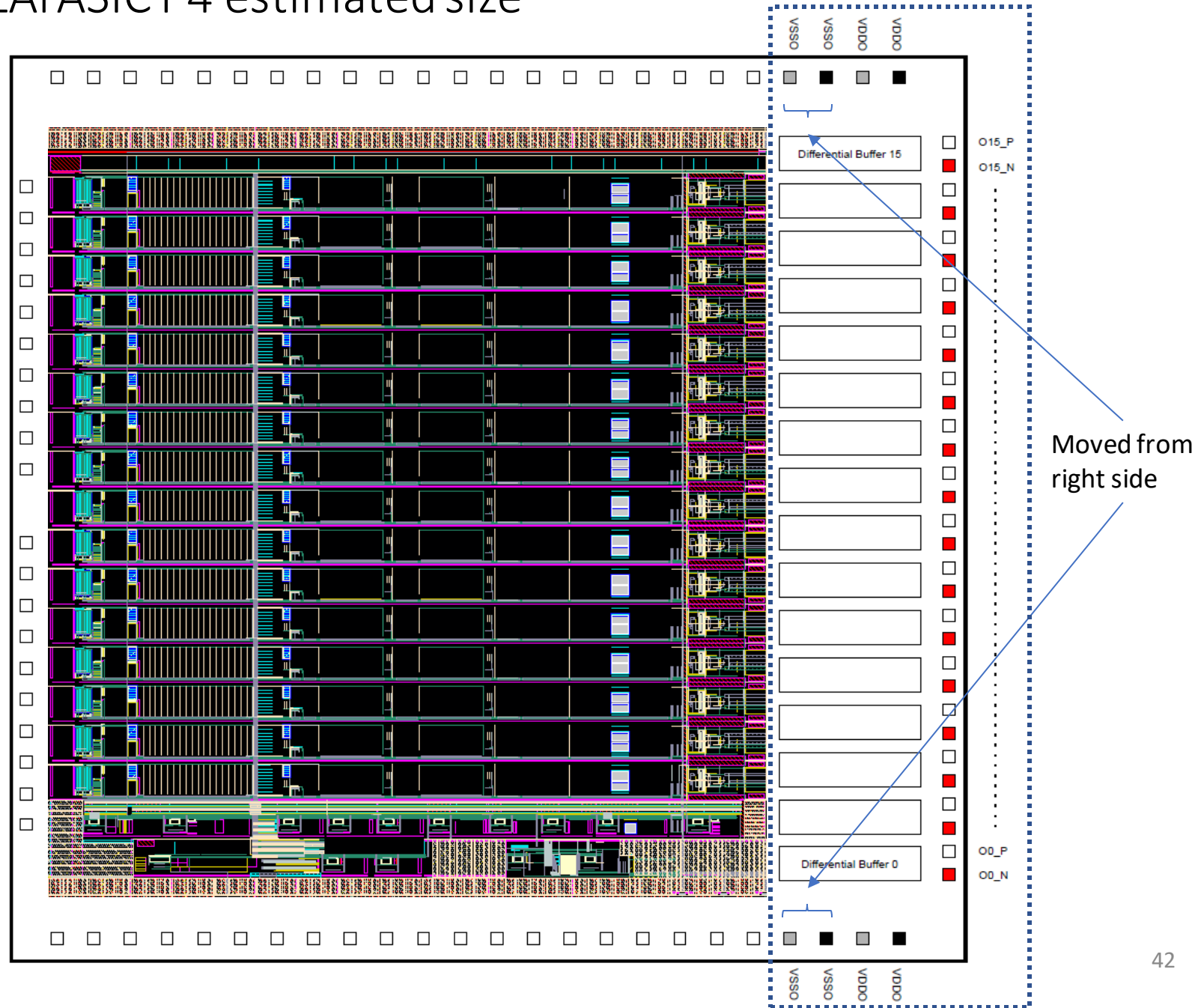
# LArASIC P4 estimated size

- Differential buffers will reuse single-ended buffer output and supply pads
- Need 16 more output, 2 Vddo and 2 Vssso pads.
  - Pad count 100 (from 80)
- Estimated layout size = 7 mm x 6.2 mm (from 6.0 mm x 5.7 mm)



## Summary and Future Work


- Discussed existing P3 LArASIC
- Simulations performed with foundry models
  - Unfortunately cold models don't exist
- Proposed P4 LArASIC with schematic modifications to mitigate
  - BGR problem – Done
  - Baseline DC shift variability – Done
  - Ledge effect – Done
- To start work on layout and post-layout verifications – **By end of March**
- Differential buffer – **By end of April**
- All layout Modifications, extracted simulations and tapeout – **End of June**

# Backup Slides

# P3 Simulation results – Linearity testing in time domain

Setting: BL = 200 mV, Gain = 14 mV/fC,  $T_p = 2 \mu\text{s}$ , 500pA, Cdet = 150 pF

I\_input

 

vOut\_NBL

