


# "Analog" Components of Digital System: Status and Plans

Gang Liu

University of Hawaii


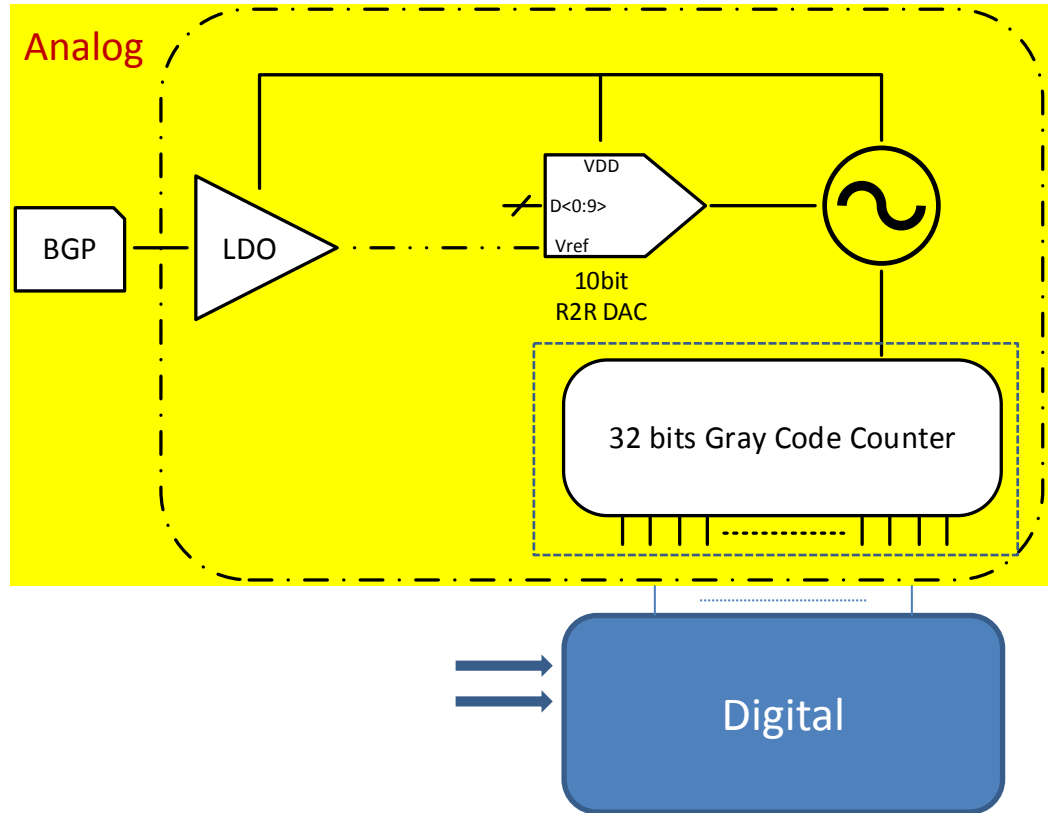
# Overview structure

- **Ring oscillator:**  
Tune range, Resolution, Power
  - **10-bit DAC:**  
Resolution, Power
  - **Bandgap & Regulator**  
Power
  - **Buffer and etc.**
- 
- **32-bit Gray code counter**



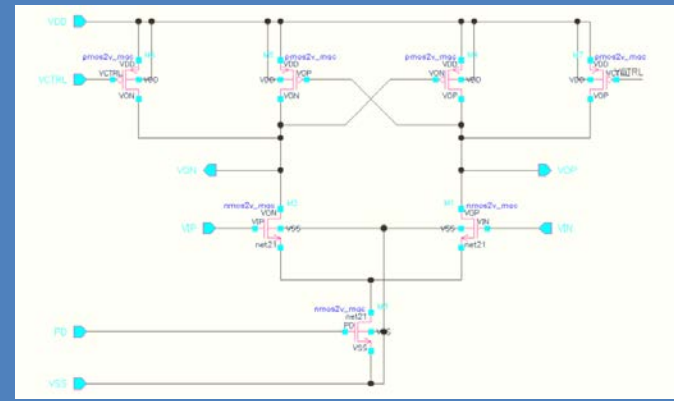
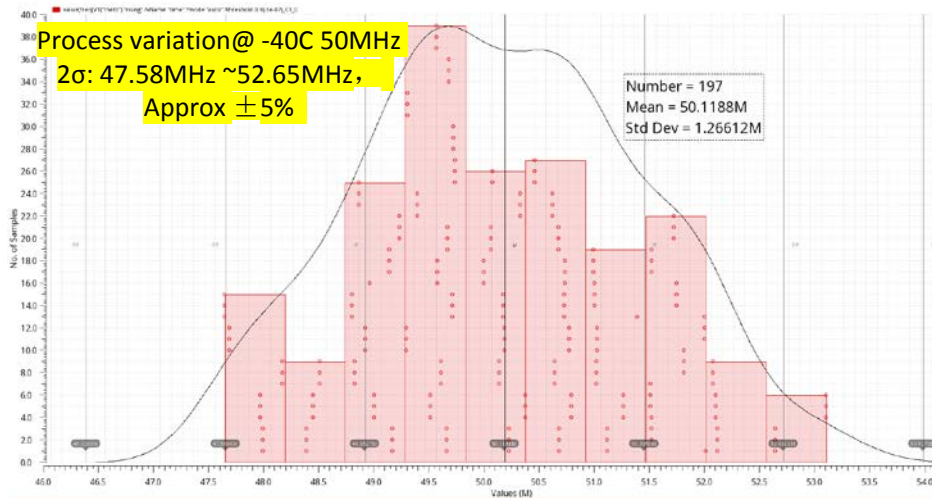
# Ring Oscillator

- Tune range: 50MHz ~ 100MHz
- Based on differential delay cell
- Power-down mode
- Power: 0.36mW @ 50MHz -40C




 
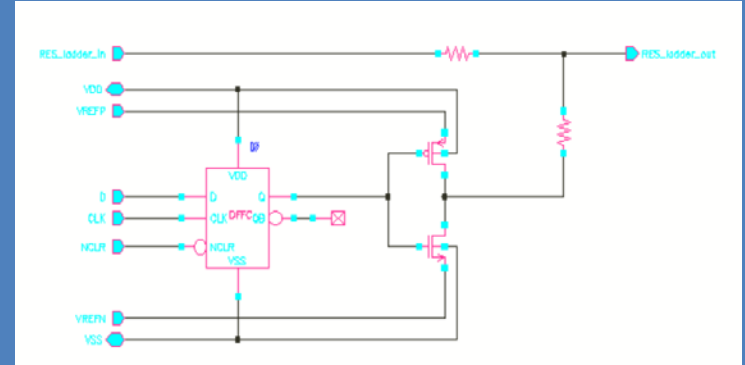
# 10-bit R2R DAC

- R2R structure
- Based on 1-bit DAC, cascade to 10 bit
- DNL=0.95LSB, INL=0.78LSB
- ENB>8 bit, considering the process variation
- Quiescent power: 0.22mW @ -40C


  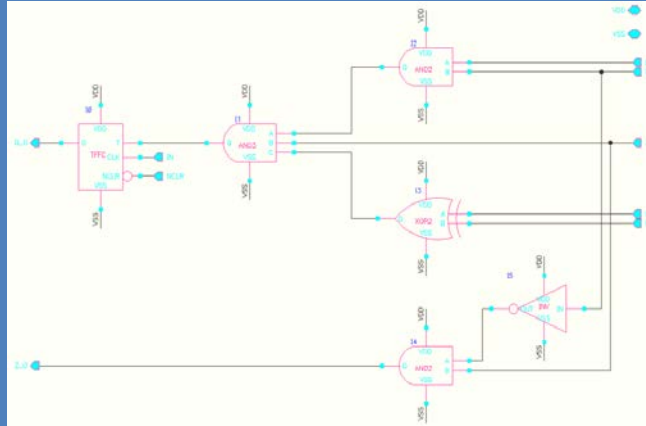
# 32-bit Gray Code Counter



- 1-bit GCC cell
- Cascaded to 32 bit
- Custom designed std cell
- Power:  $\sim 0.23\text{mW}$



# Bandgap

- First-order temperature compensation
- -40C to 55C temperature coefficient < 7ppm
- Power: 0.34mW @ -40C

- The regulator is in process.

  

# Status

Component	Schematic	Layout	power
Ring oscillator	Done	Done	0.36mW
GCC	Done	Done	~0.23mW
DAC	Done	Done	0.22mW
Bandgap	Done	Done	0.34mW
Regulator	In process	In process	TBT
			Total: 0.36+0.23+ 0.22+0.34+Reg =1.15mW+Reg per ASIC

# Future plan

- Finish the regulator design
- Cold model of the process ?
- Official Standard cell library ?
- Components to share, DAC, BGP ?



*Thank you !*