



# Signal Conditioning: Field Emission Probe sub-module

Bartosz Pękosławski & Paweł Marciniak





## About us

### Bartosz PEKOSŁAWSKI

Ph.D. Electrical Engineering

- Role:
  - HW (signal conditioning) designer
- Relevant Experience:
  - Projects on machine vibration monitoring – hardware engineer (2006 – 2011)
  - TULCOEMPA – hardware designer (2011 – 2015)
  - SPParTAN – hardware designer (2019 – 2022)
  - FOSREM – hardware designer (2021 – present)

### Paweł MARCINIAK

Ph.D. Electrical Engineering

- Role:
  - HW (signal conditioning) designer
- Relevant Experience:
  - INNOREH – software designer (2017 – 2021)
  - SPParTAN – firmware designer (2019 – 2022)
  - ITER – hardware engineer (2021 – 2022)
  - FOSREM – hardware designer (2021 – present)





# Agenda

- The FEP module requirements
- The PoC version specification and scope
- The sub-module simulations and design details
- Implementation
- Test results discussion
- Full scale design plans
- Summary



# The FEP module requirements

- 1 FEP per cavity/coupler
- transimpedance amplifier used
- bias up to 45 V
- read back up to 10 mA
- trip levels set under software control
- 2 MSPS waveform capture
- $< 10 \mu\text{A}$  resolution
- $< 1 \mu\text{s}$  RFPI response time





# The PoC version specification and scope

Two FEP channels

Bias voltage adjustable via SPI up to 45 V

Management Block:


- I<sup>2</sup>C communication with Raspberry PI
- Current measurement
- Temperature and humidity measurements





# The sub-module design details

## Conceptual diagram

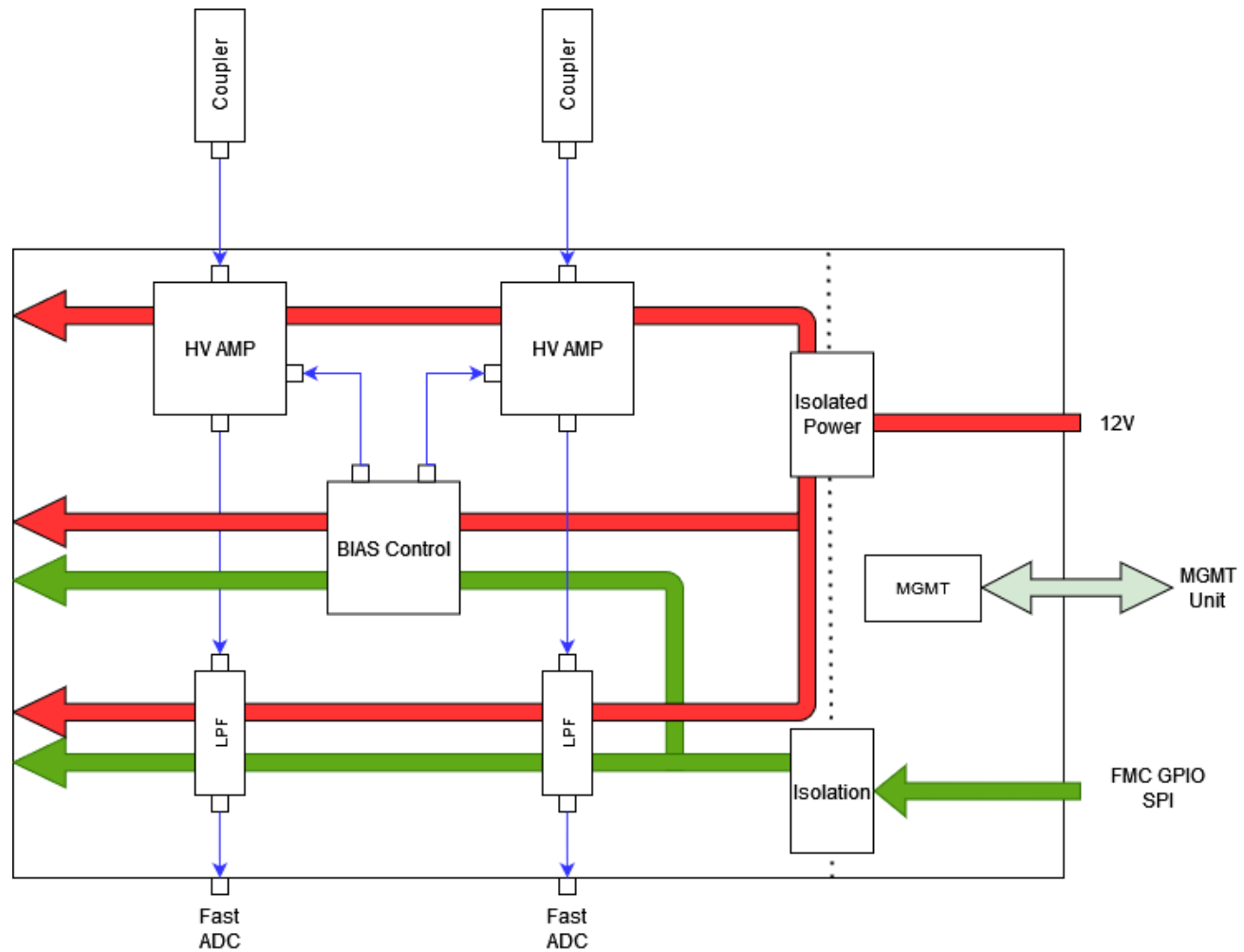






# The sub-module design details

## System Connectors Block

- Power Connector (12 V)

 


- MGMT Connector (I<sup>2</sup>C) and sensors



- Output Signal Connectors (MMCX)



- FMC GPIO Connector (SPI)

 

- Isolation of SPI signals based on MAX22245BAWA+ and MAX22246CAWA+ digital isolators (2 channels, 7 ns delay, up to 25 / 200 Mbps, 868 V<sub>RMS</sub> continuous / 5 kV<sub>RMS</sub> 60s / 12.8 kV<sub>RMS</sub> surge galvanic isolation)







# The sub-module design details

## Power Block

- 12V  $\rightarrow$  5V SMPC module Traco Power TRS 2-1211 (isolated, 9-18 V input, max. 2 W output power, 80% efficiency, 1.6 kV isolation)
- 12V  $\rightarrow$   $\pm$ 12 V SMPC module Traco Power TEN-3-1222N (isolated, 9-18 V input, max. 3 W output power, 84% efficiency, 1.6 kV isolation)
- EN 55032 class A external filters at the inputs for radiated and conducted emission
- LT3032 dual, low noise, positive and negative low dropout (300 mV) voltage linear regulator with 150 mA maximum output current ( $\pm$ 12 V  $\rightarrow$   $\pm$  11.8 V)
- Noninverting 12V  $\rightarrow$  48V SMPC based on LT8580 (0.2 – 1.5 MHz, UVLO, soft-start, 1 A/65 V switch, input voltage range 2.55 – 40 V)
- Inverting, dual inductor 12V  $\rightarrow$  –48 V SMPC based on LT8580





# The sub-module design details

## FEP Connectors Block

- SMA Connectors



Two SMAJ48A TVS diodes (56.1 V, 5.2 A) + 10 k $\Omega$  serial resistors at each input line

## Bias Control

- MCP48FEB24-20E quad, 12-bit resolution buffered voltage output Digital-to-Analog Converters (DAC), with volatile user memory
- MAX6138 bandgap voltage reference (4.096V),  
Operating Current Range: 60  $\mu$ A to 15 mA, 28  $\mu$ V<sub>RMS</sub> Output Noise (0.01 to 10 kHz)
- Noninverting voltage amplifier with 10 V/V gain based on LTC6090 OPAMP  
(max. 50 pA input bias current,  $\pm$ 4.75 to  $\pm$ 70 V supply voltage range, 12 MHz GBW, 21 V/ $\mu$ s slew rate, 3.5  $\mu$ V<sub>P-P</sub> Output Noise (0.1 to 10 Hz))




# The sub-module design details

## HV Amplifier

- Transimpedance amplifier with 470 V/A gain based on LTC6090 OPAMP (max. 50 pA input bias current,  $\pm 4.75$  to  $\pm 70$  V supply voltage range, 12 MHz GBW, 21 V/ $\mu$ s slew rate, 3.5  $\mu$ V<sub>P-P</sub> Output Noise (0.1 to 10 Hz))
- Inverting voltage amplifier with  $-1$  V/V gain based on LTC6090 OPAMP with  $\pm 48$  V supply voltage
 
## LPF Block


- Bessel LPF (Sallen-Key topology)
  - $G = 0.5$  V/V
  - $f_{-3dB} = 2.4$  MHz
  - $G(21.4 \text{ MHz}) = -40$  dB
  - Group delay = 90 ns
  - GBW required = 88.2 MHz
- LM6171BIM OPAMP (100 MHz Unity Gain Bandwidth , Input Voltage-Noise Density 12 nV/ $\sqrt$ Hz, Slew Rate of 3.6 kV/ $\mu$ s) with  $\pm 12$  V supply voltage and I/O clamp circuits




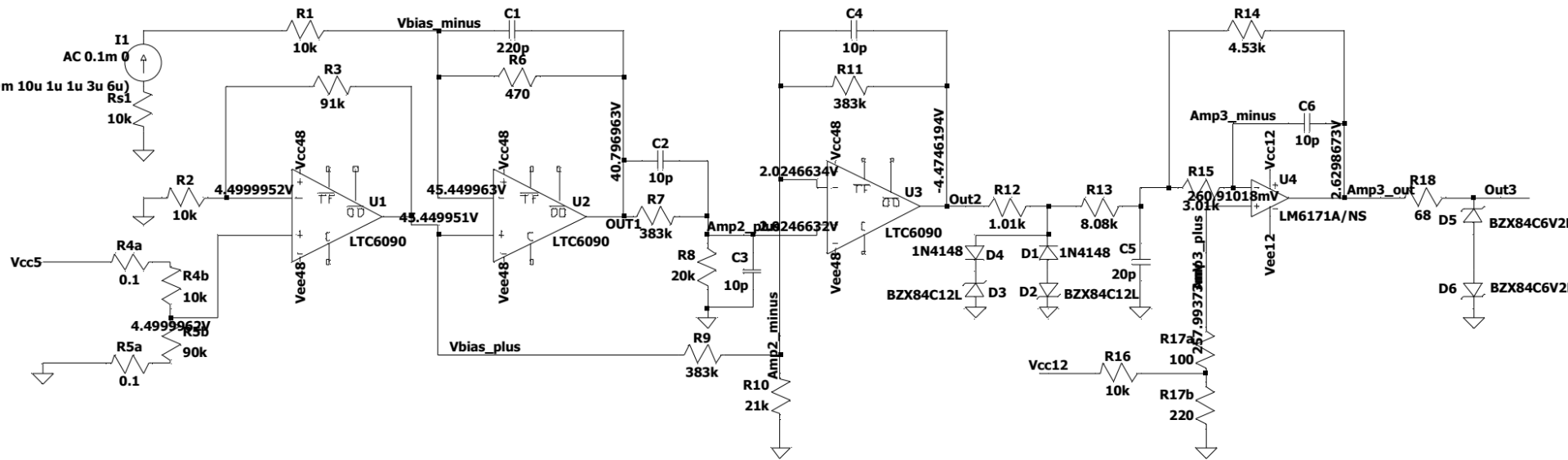
# The sub-module simulations and design details



- Signal conditioning path simulated in LTSpice – simulated circuit




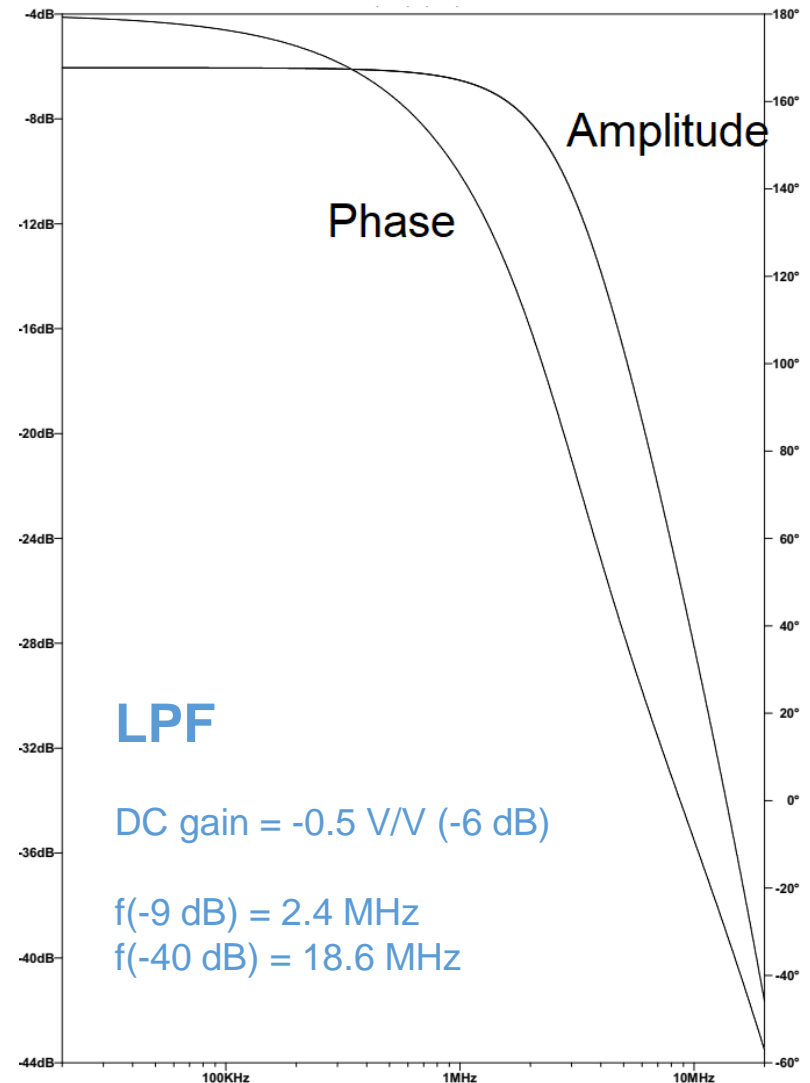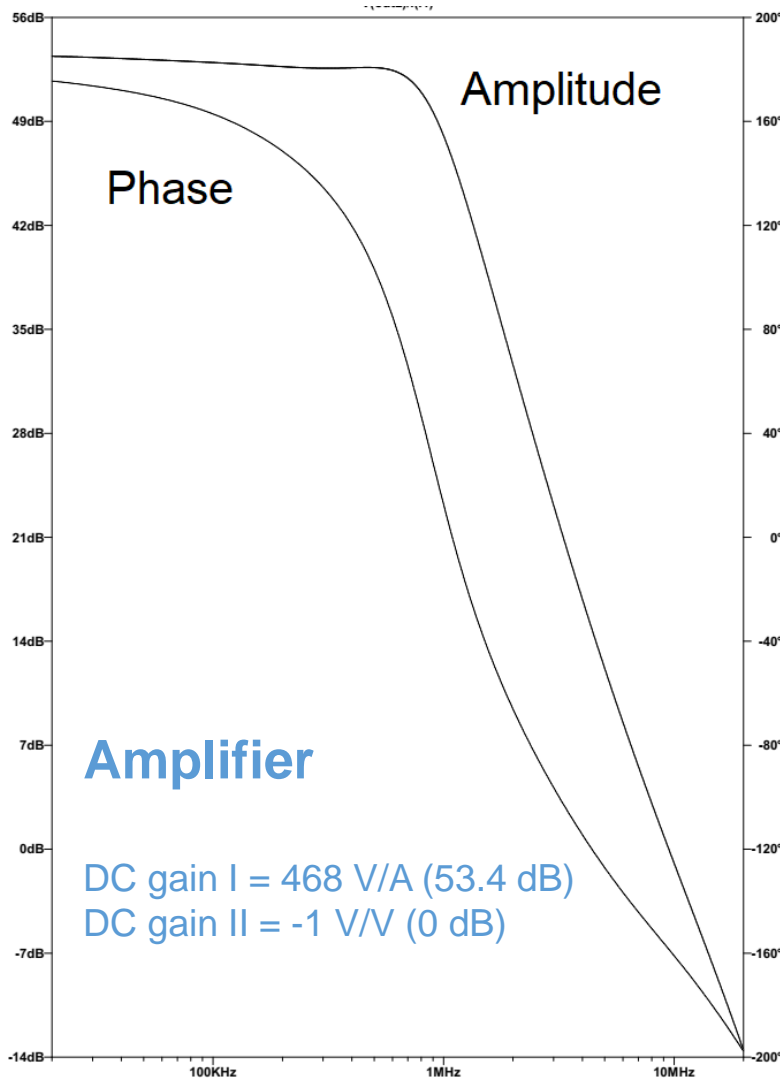
# The sub-module simulations and design details



- Signal conditioning path simulated in LTSpice – AC analysis




  
# The sub-module simulations and design details


- Signal conditioning path simulated in LTSpice – transient analysis




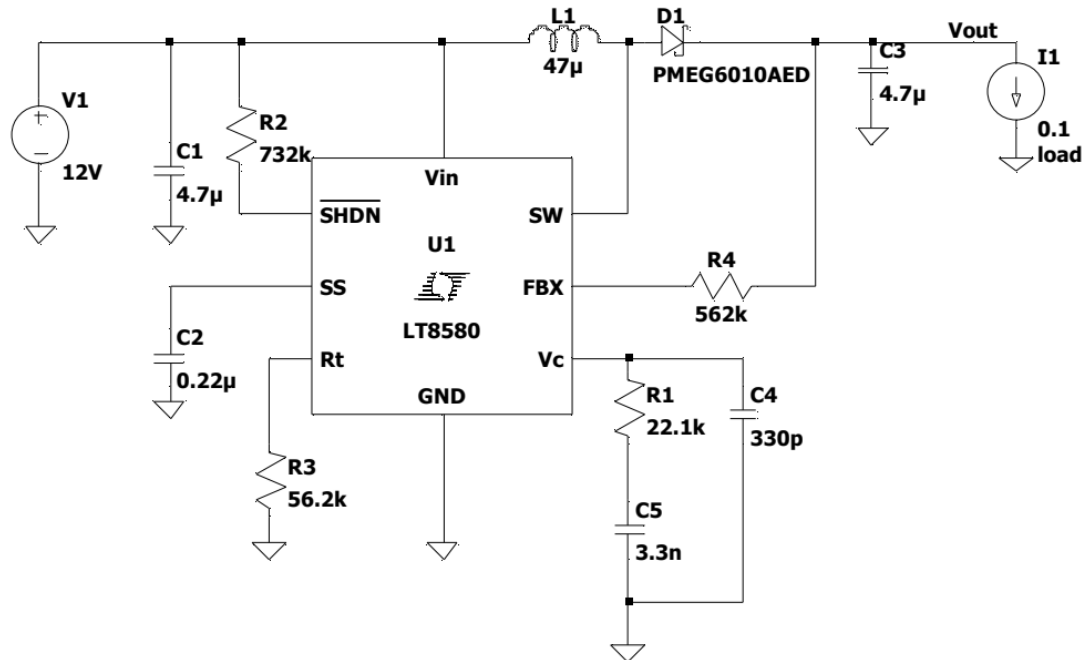
# The sub-module simulations and design details



- 12 V to +48 V SMPC simulated in LTSpice – simulated circuit




  
# The sub-module simulations and design details

- 12 V to 45 V SMPC simulated in LTSpice – simulation results







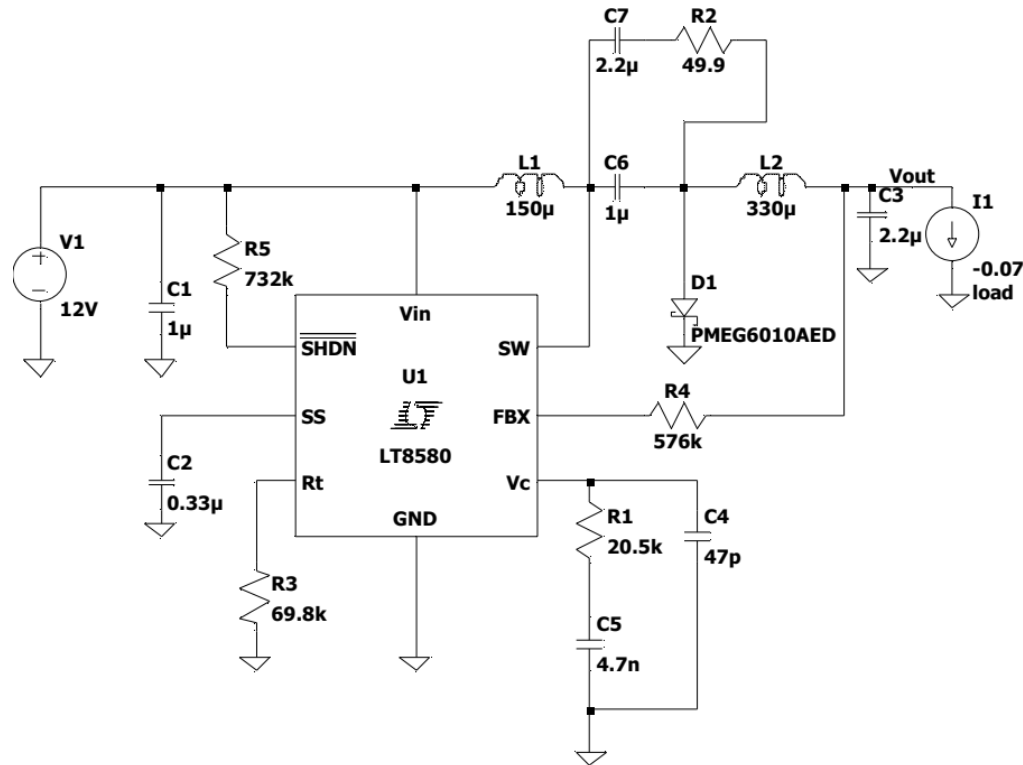
# The sub-module simulations and design details



- 12 V to -48 V SMPC simulated in LTSpice – simulated circuit




  
# The sub-module simulations and design details

- 12 V to -45 V SMPC simulated in LTSpice – simulation results









# Implementation

## 3D model

  







# Test results discussion

- Detection of soldering faults (partially manual soldering)
  - Short circuits
  - Damaged tracks
  - Missing or broken connections
- Operation of the power block and input bias (correctness of voltage levels)
- Output signal conditioning
- Delay between input and output signals
- I<sup>2</sup>C communication with temperature and supply current sensors





## Test results discussion

- **Detection of soldering faults, e.g. short circuits, damaged tracks, missing or broken connections**
  - Minor errors were detected on the basis of the vision analysis and corrected.
- **Operation of the power block (correct voltage levels)**
  - The power block works properly
  - Current consumptions are as expected (260 mA for 12 V voltage domain)
  - Output voltages are correct

Test point	Value [V]
5V SMPC output	4.986
±12V SMPC outputs	+11.98/-12.00
LDO outputs	+11.62/-11.84
±48V SMPC outputs	+47.81/-48.25
Reference voltage	4.087
DAC outputs CH1, CH2	2.490 / 2.494
Bias voltages (default) CH1, CH2	25.10 , 25.07







# Test results discussion

- **Correctness of output signal conditioning**
  - The correctness of the output signal for 6 input current signal amplitudes (100 kHz)

## HV Amplifier OUT (1 mA)

 

## LPF OUT (1 mA)

 






# Test results discussion

- **Correctness of output signal conditioning**
  - The correctness of the output signal for 6 input current signals (100 kHz)

HV Amplifier OUT (10  $\mu$ A)

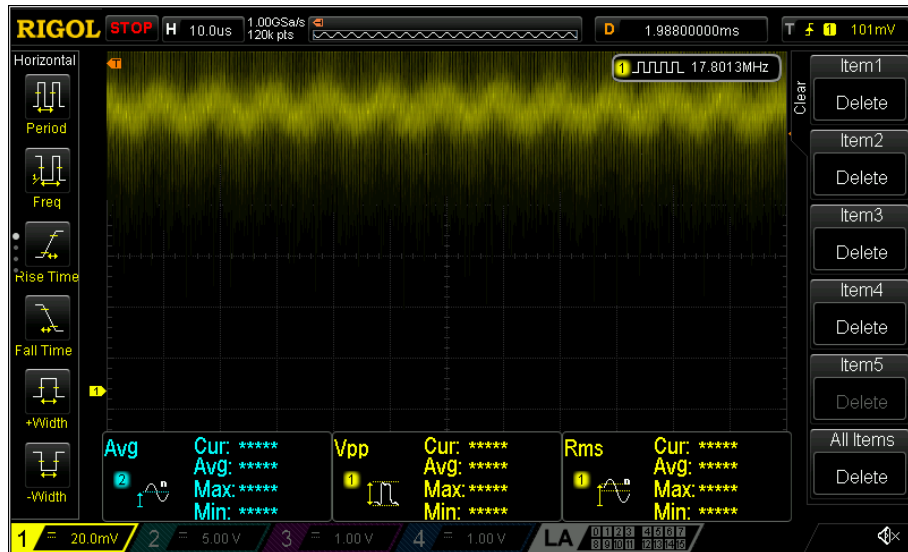

LPF OUT (10  $\mu$ A)






# Test results discussion

- Delay between input and output signals
  - The delay between input and output signals for 3 frequencies was measured:

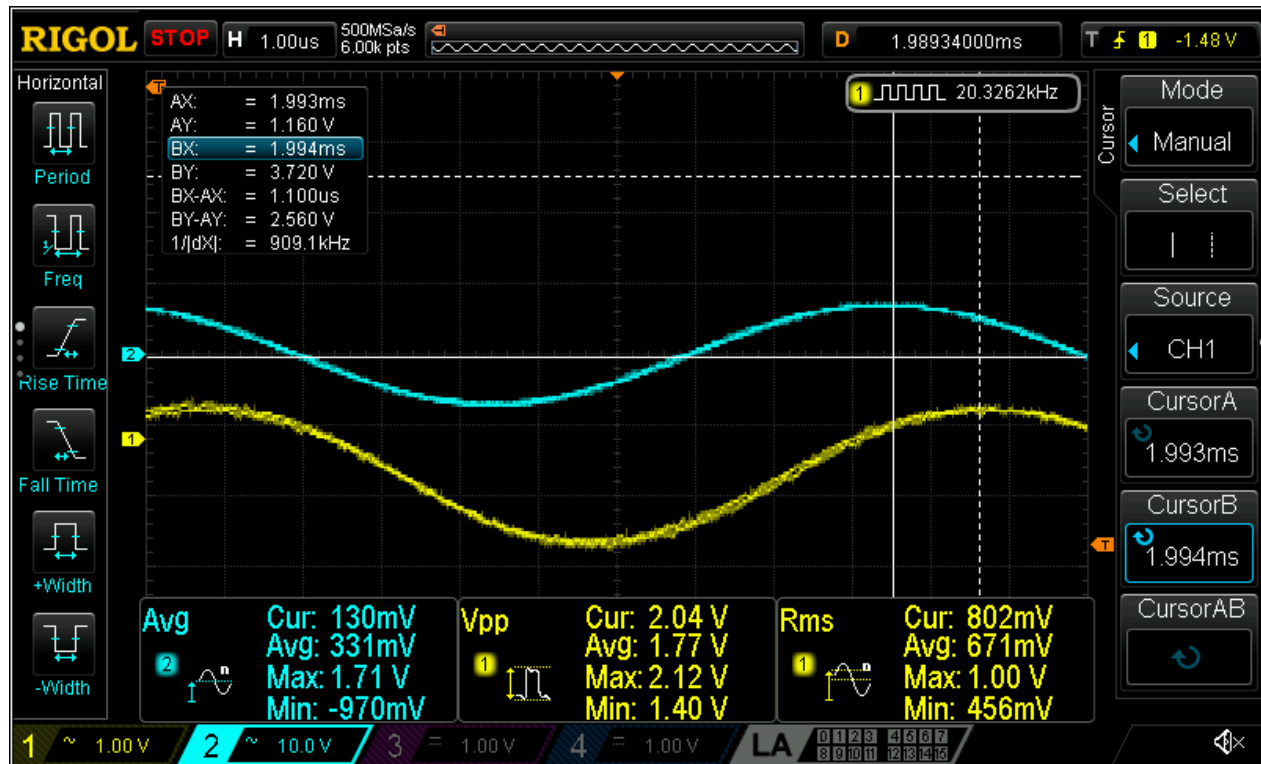**Delay = from 0.23  $\mu$ s (500 kHz) to 1.1  $\mu$ s (100 kHz)**





# Test results discussion

- **I<sup>2</sup>C communication with temperature and supply current sensors**
  - As part of the tests, the correctness of I<sup>2</sup>C communication with two sensors was checked:
    - STH31 - Connection with the temperature sensor was established and correct temperature was read.
    - INA219 – Connection with the sensor was established.



## Full scale design plans

- The presented solution can be partially adopted in the final design
- Minimization of the delay between input and output signals and noise reduction is needed in the final design
- 2 more channels are needed in the final design



- Changes in schematic diagrams (duplication of some blocks; replacement of HV OPAMPs; addition of EMI suppression filters)
- PCB project redesign



# Summary

- Requirements
  - 1 output signals per cavity => 4 output signals per module
  - Response time less then 1  $\mu$ s
- PoC, implementation and verification
  - PCB supporting 2 probes
  - 4-layer PCB
  - Correct operation of the power block and output signal conditioning
  - Delay between input and output is about 1.1  $\mu$ s for 100 kHz input signal
- Full scale design plans
  - PCB supporting 4 probes






Thank You





# The sub-module design details


## Power Block

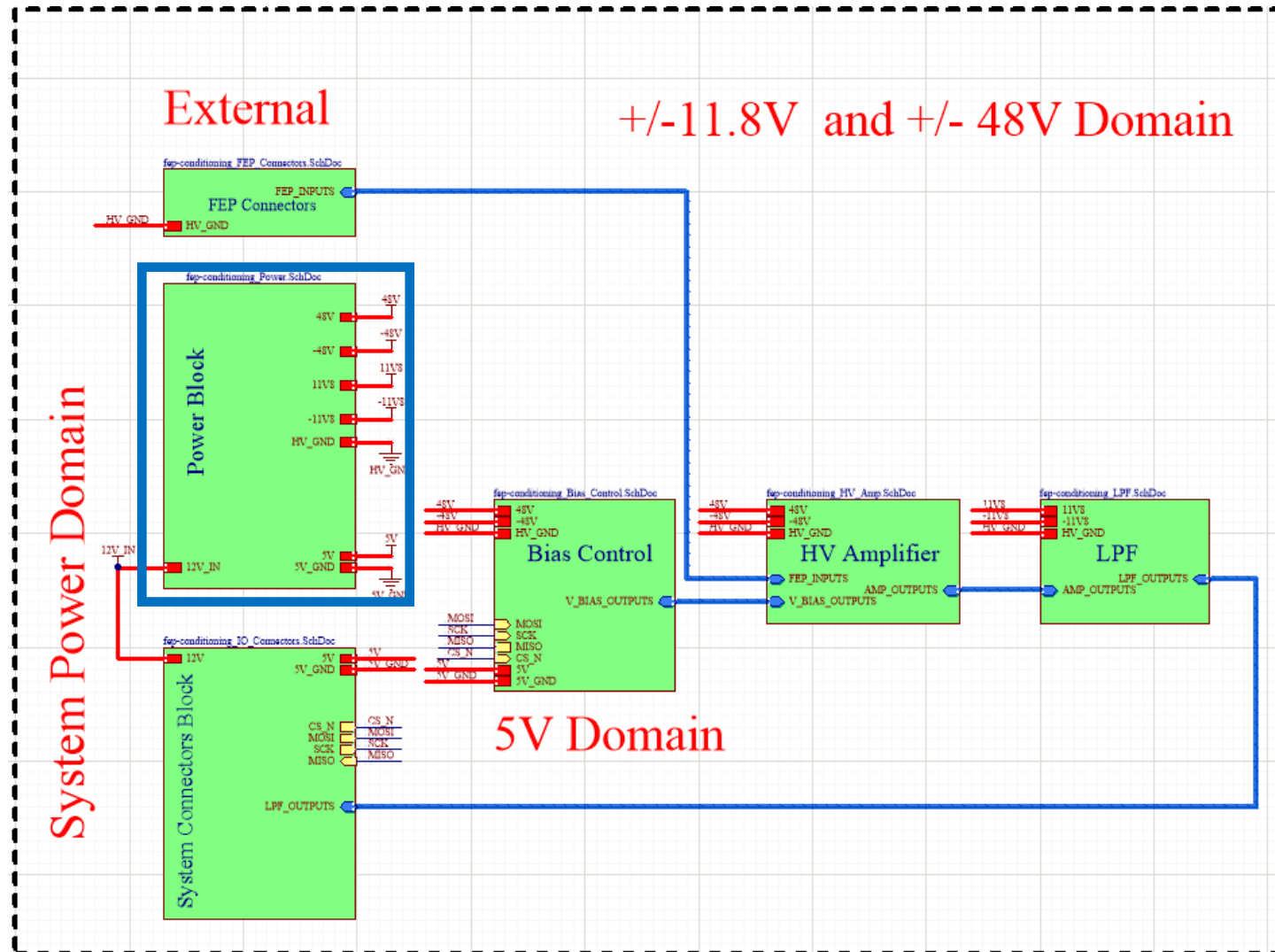



# The sub-module design details

## Power Block Schematic Diagram

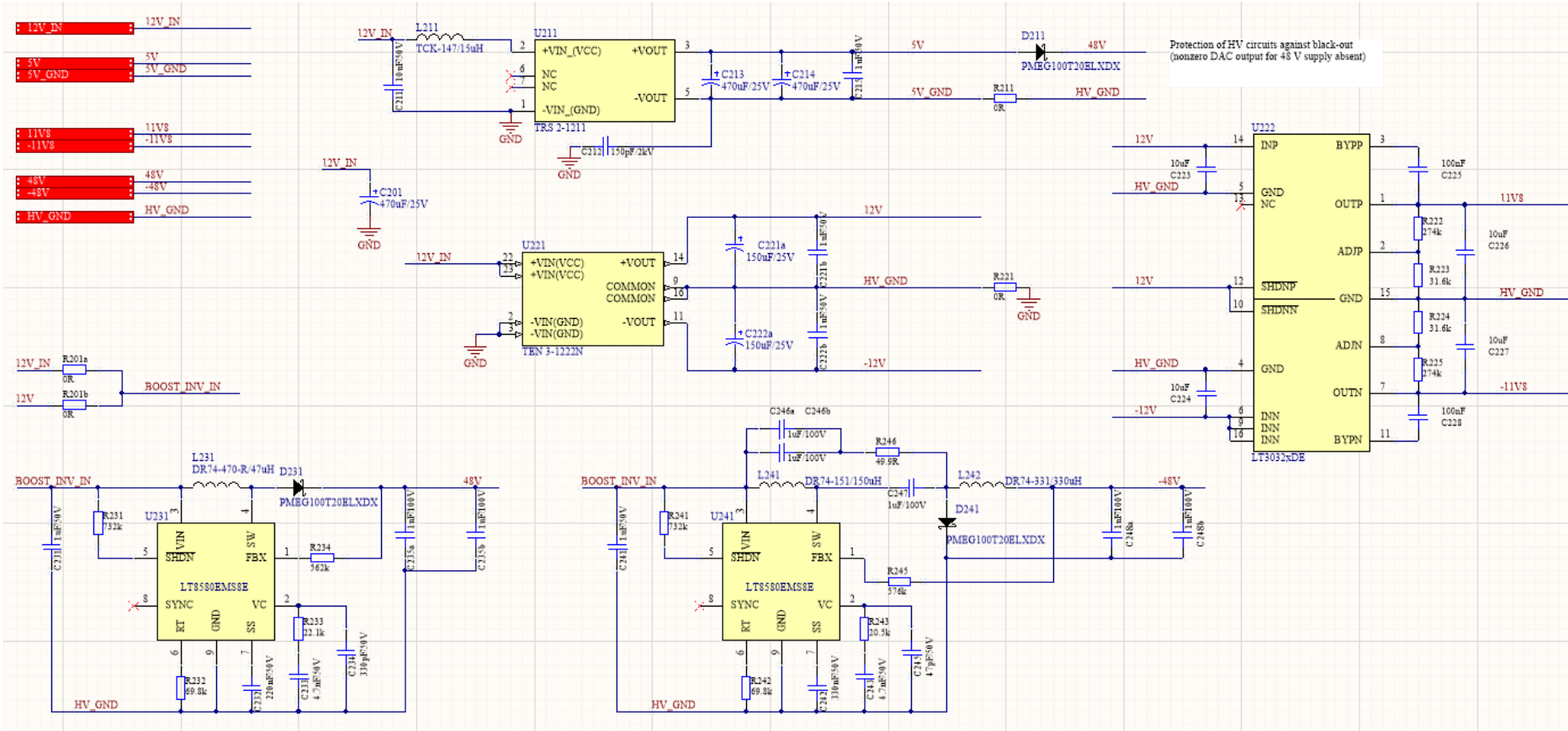






# The sub-module design details


## System Connectors Block

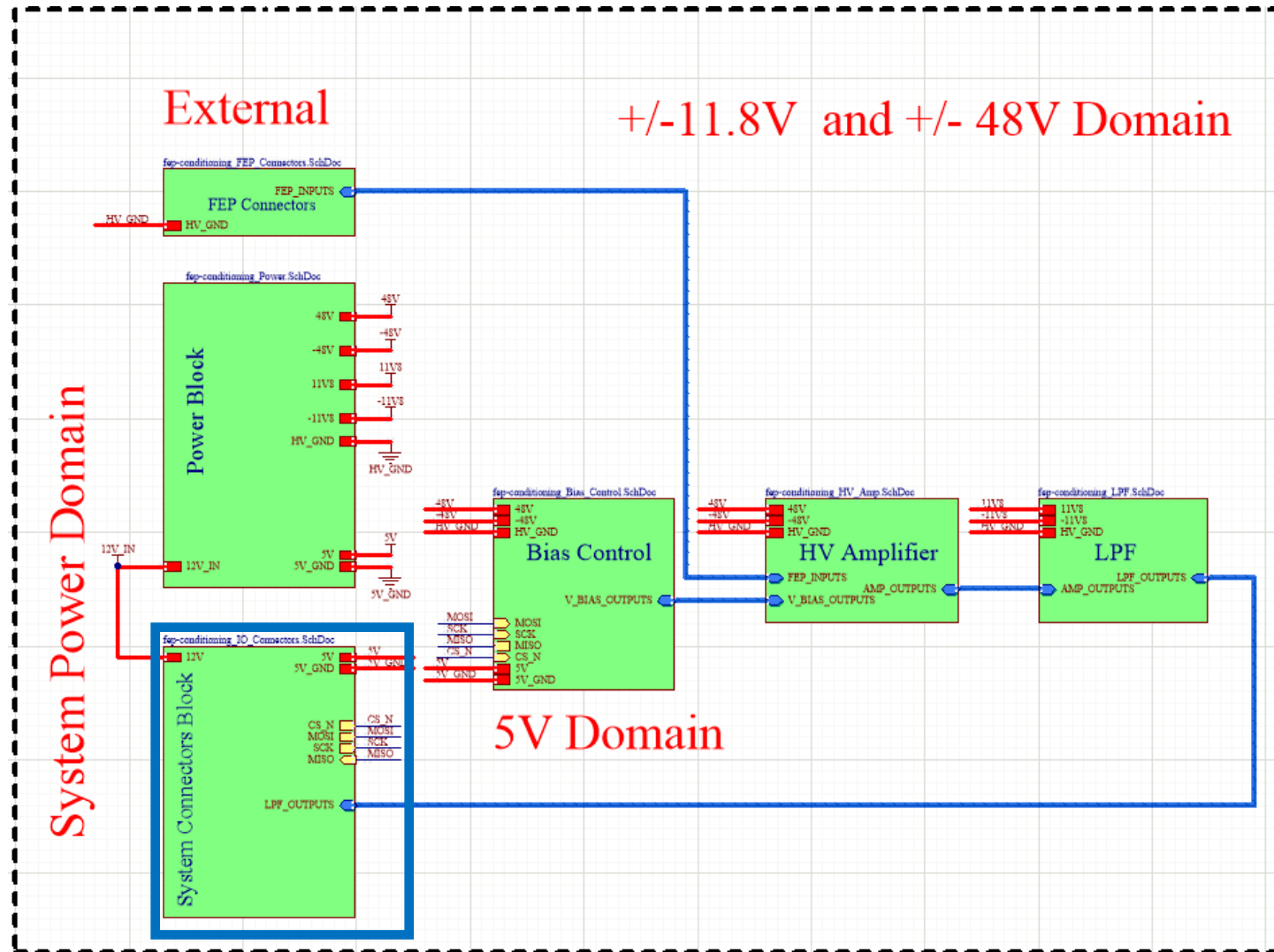



# The sub-module design details



## Management Sensors

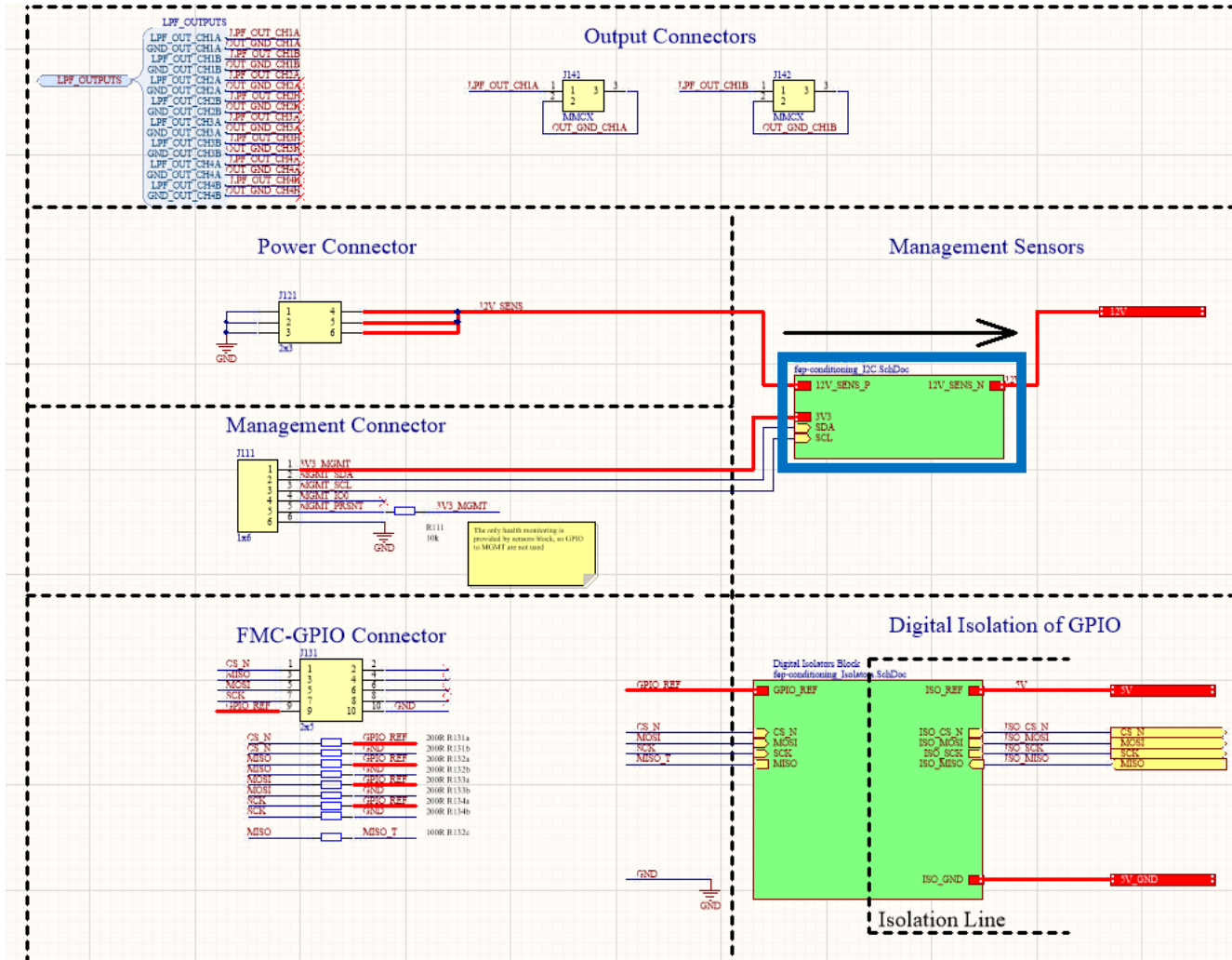



# The sub-module design details


## Management Sensors Block Diagram

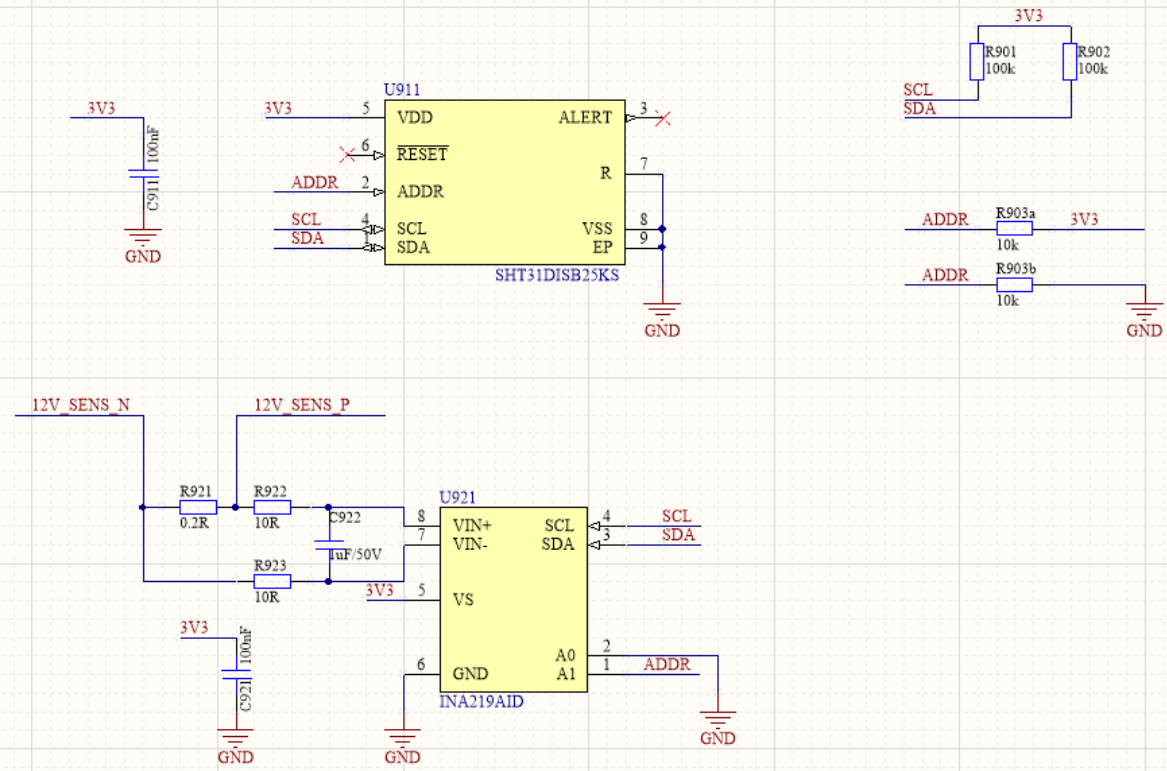 



# The sub-module design details


## Digital Isolation of GPIO

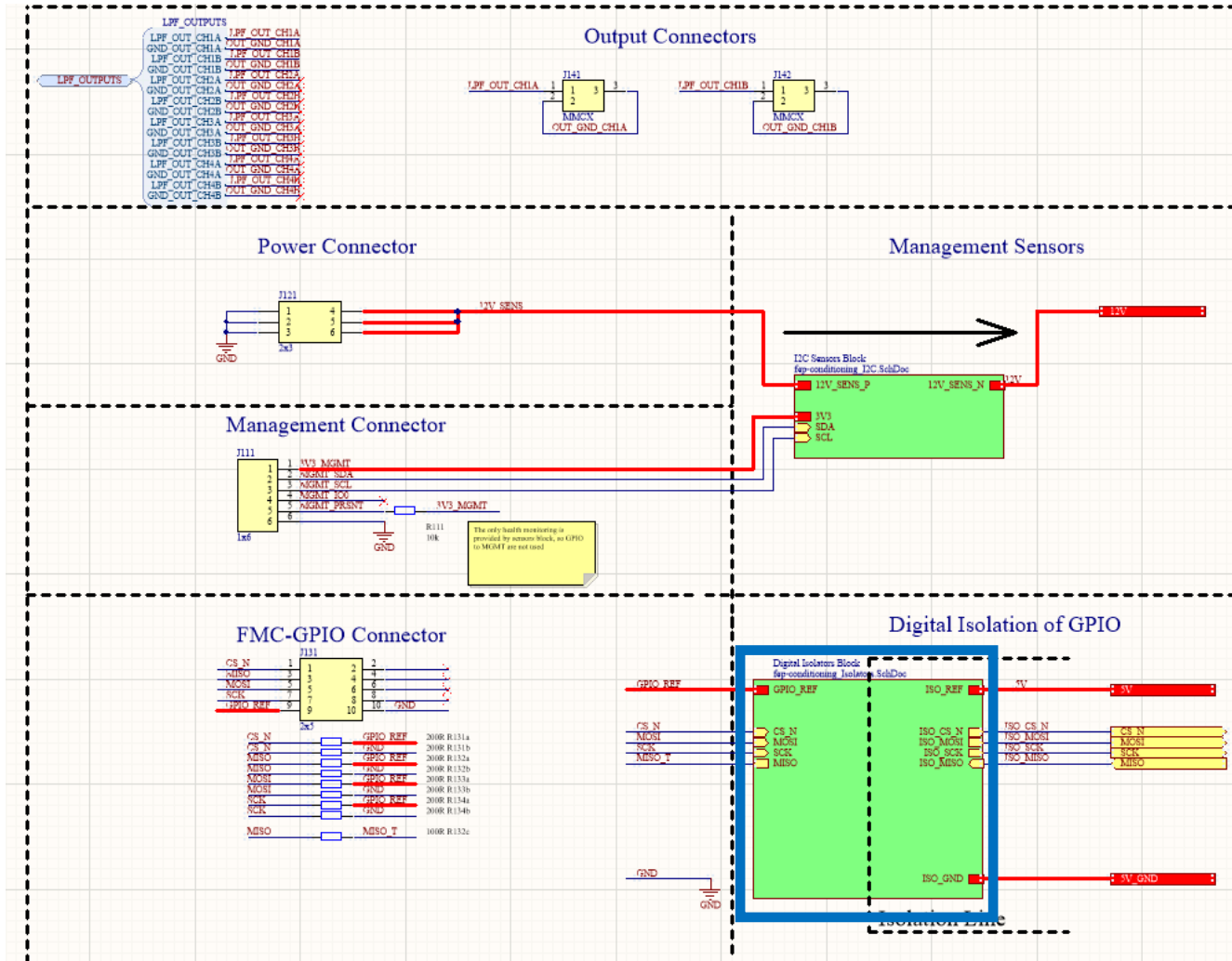



# The sub-module design details

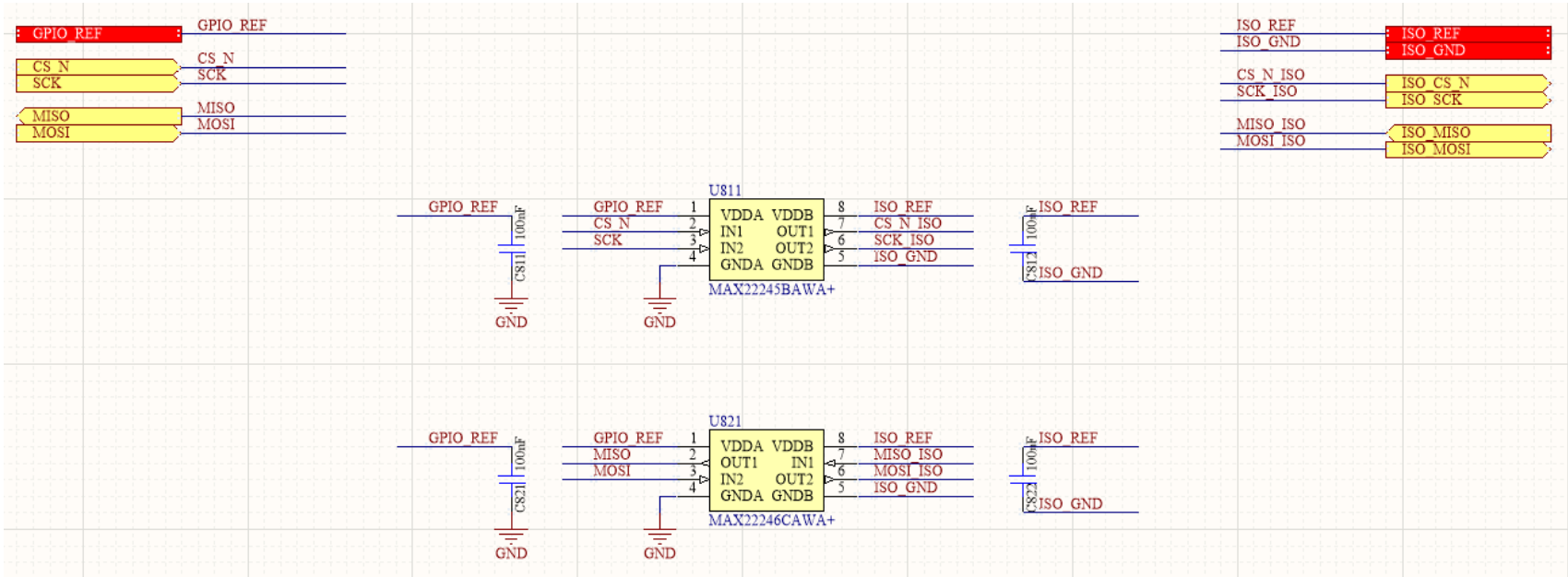
## Digital Isolation of GPIO Block Diagram





# The sub-module design details

## Bias Control

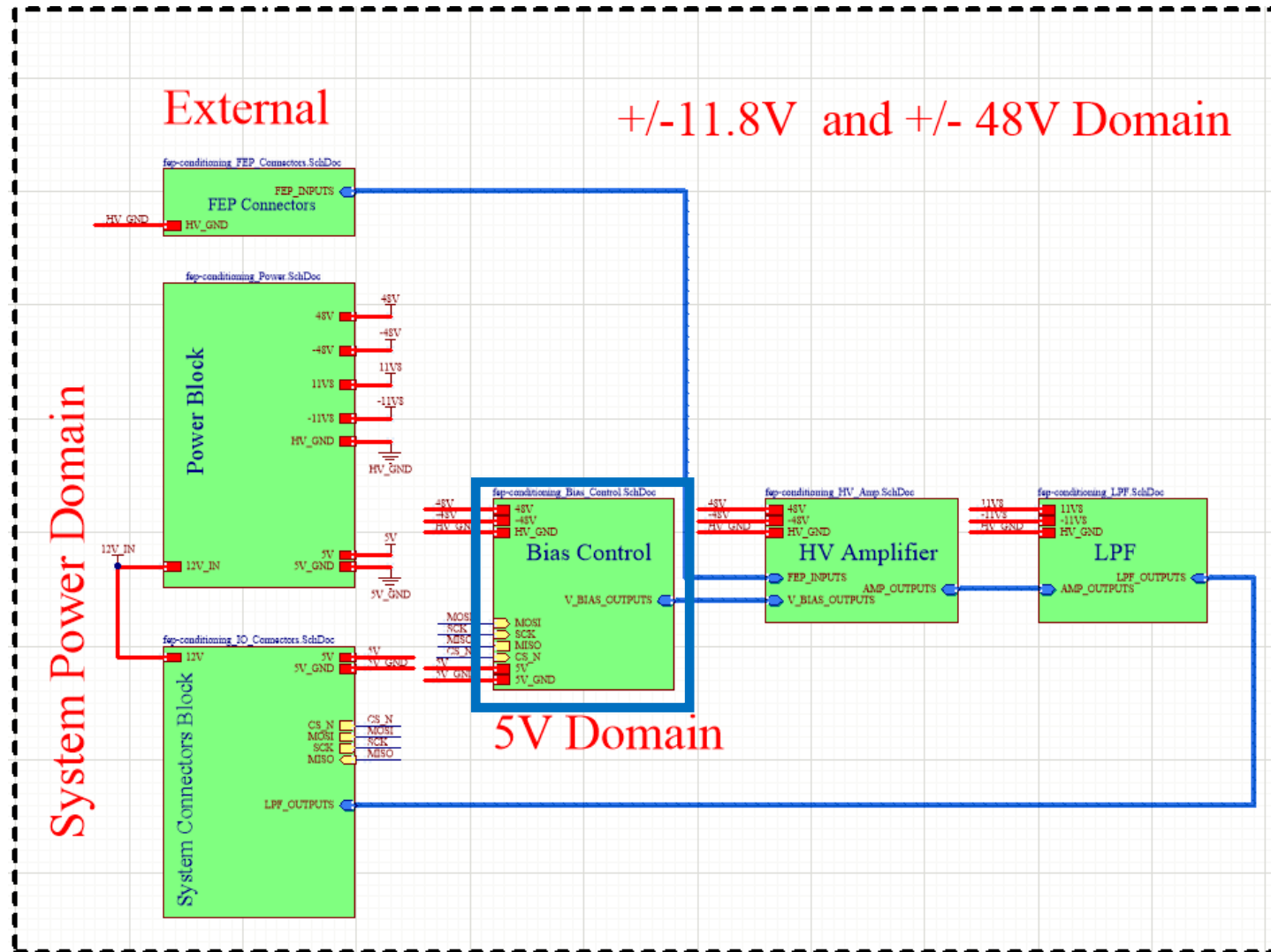








# The sub-module design details


## HV Amplifier

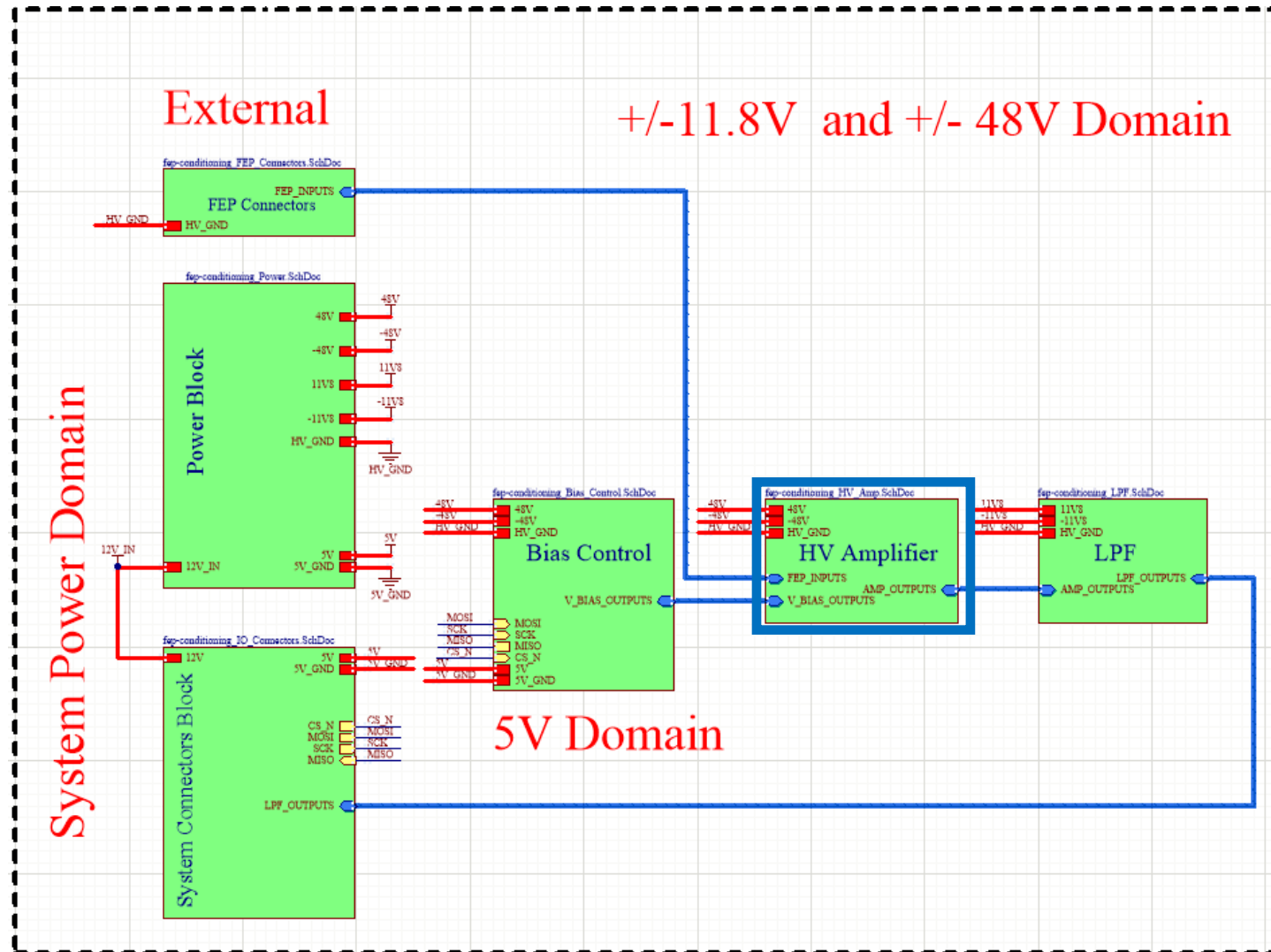



# The sub-module design details


## HV Amplifier Schematic Diagram

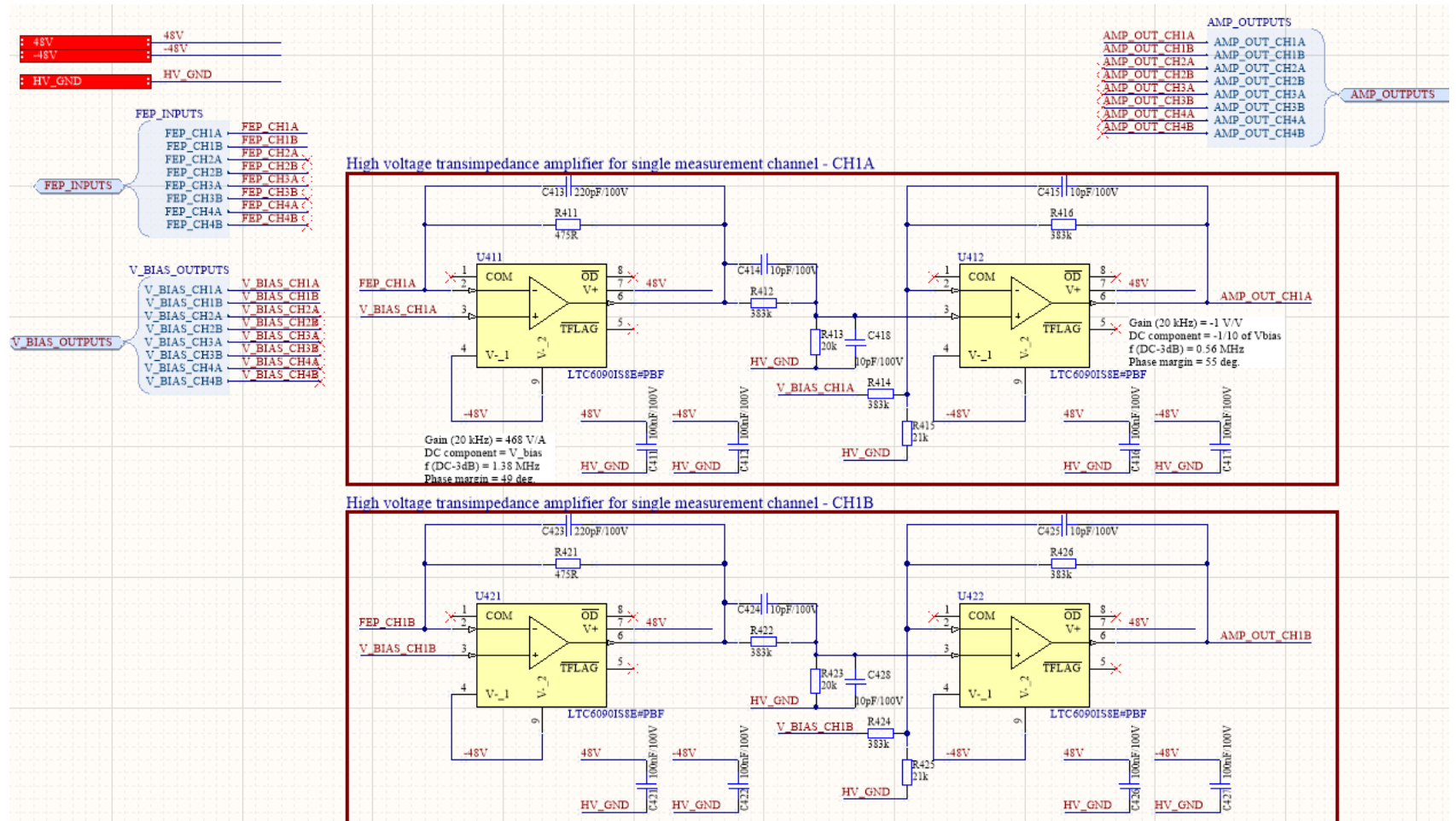



# The sub-module design details


## LPF Block

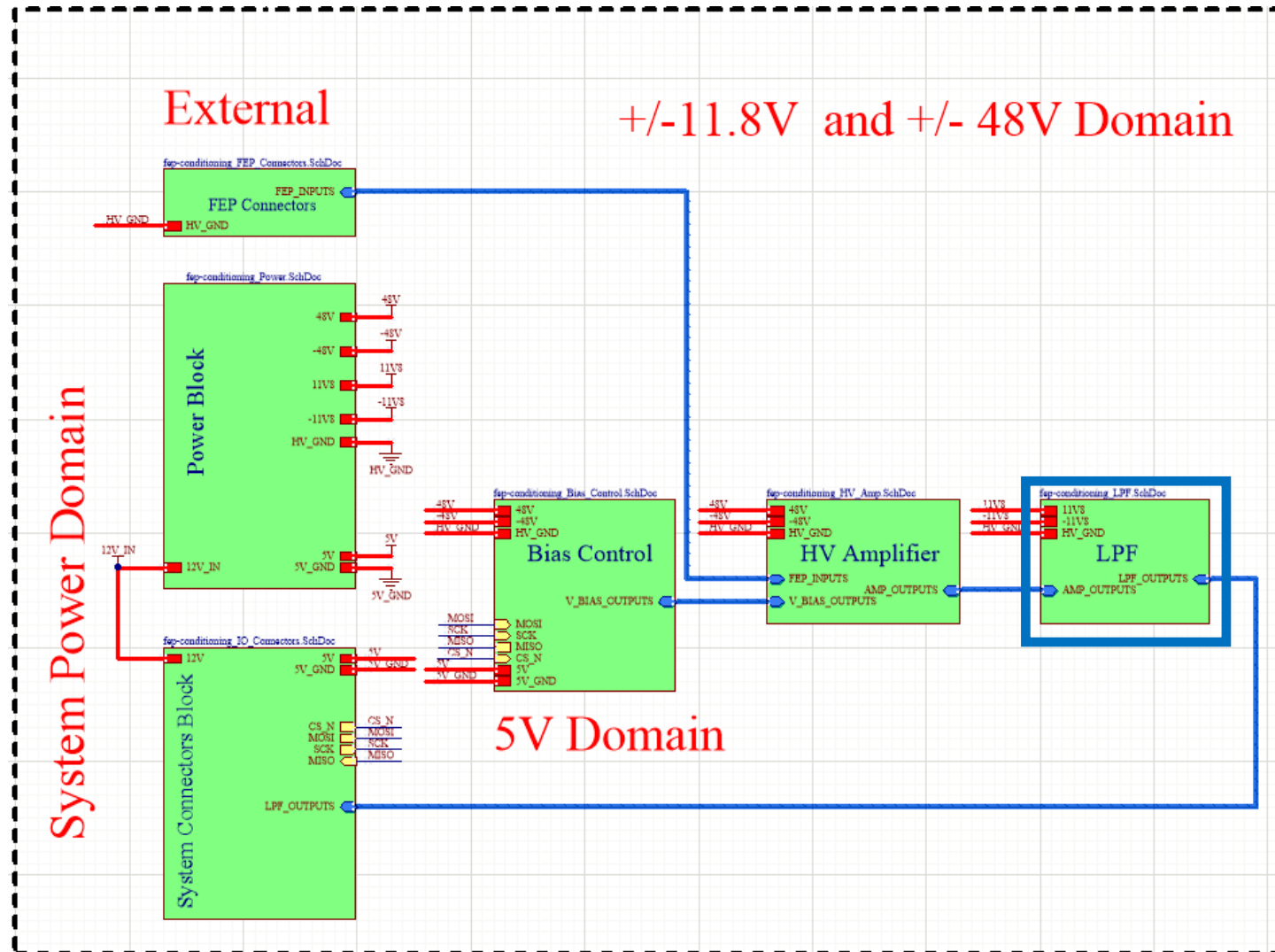



# The sub-module design details


## LPF Block Schematic Diagram

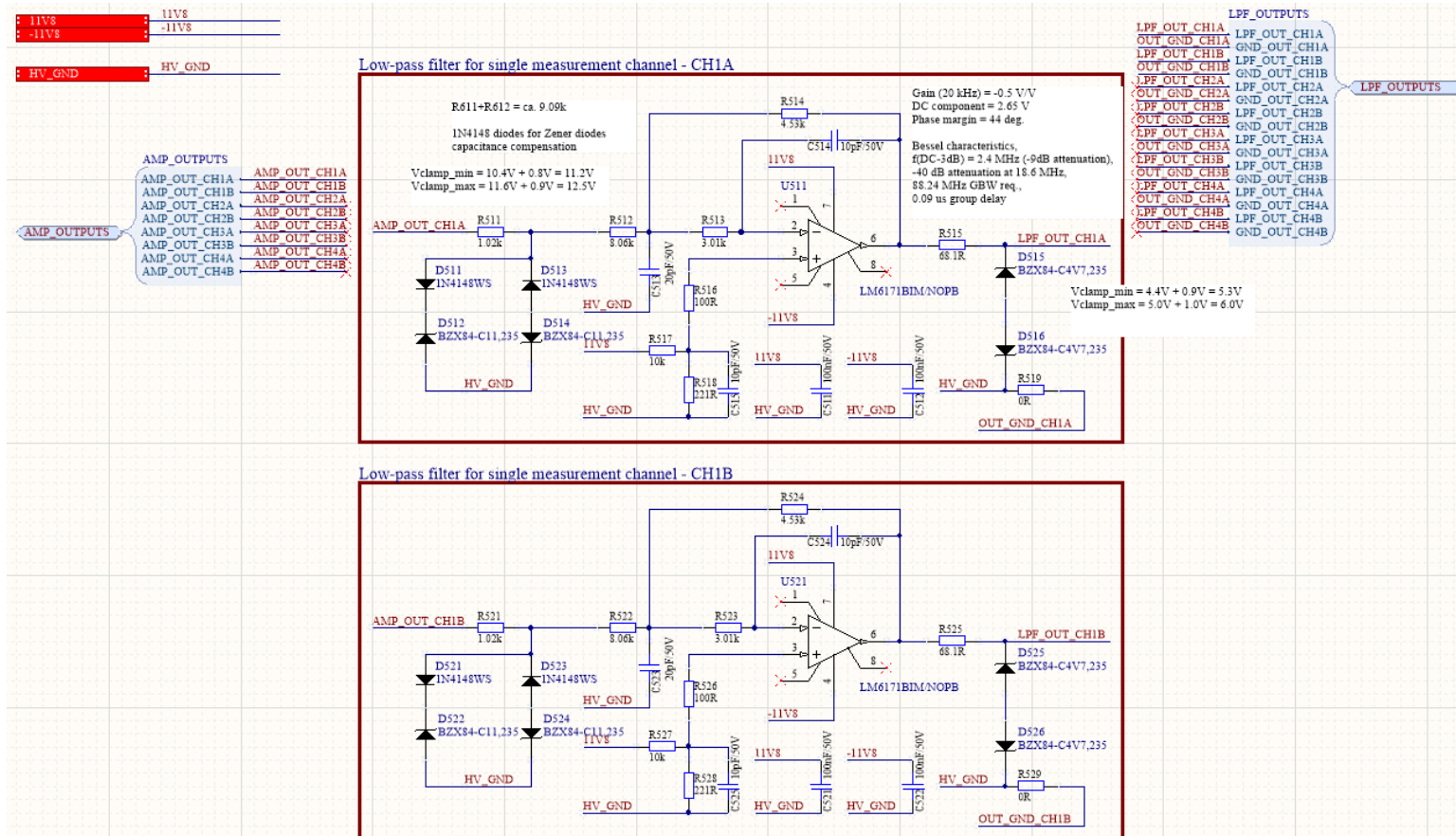



# The sub-module design details

## FEP Connectors

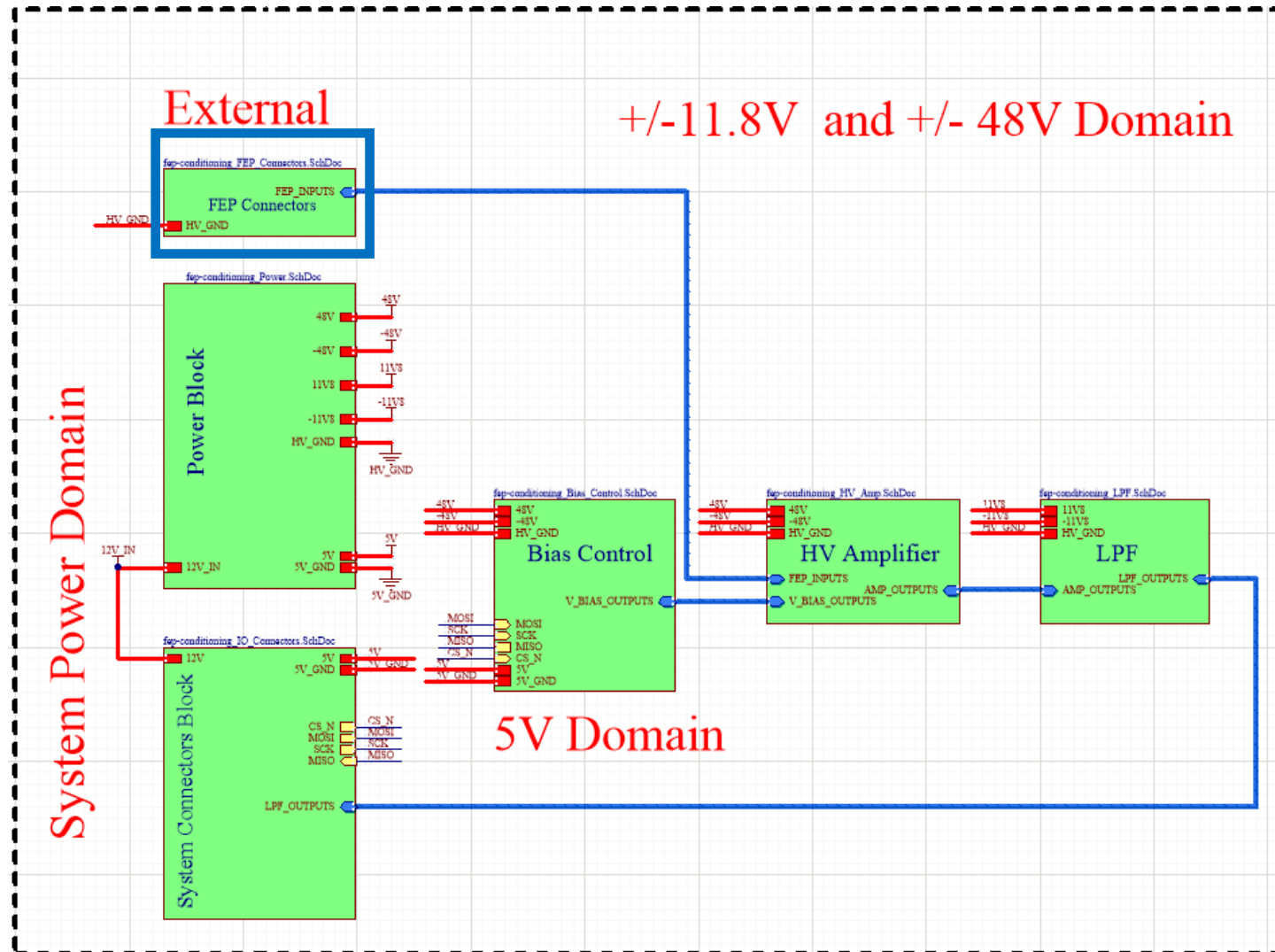



# The sub-module design details

## FEP Connectors Schematic Diagram

