

# SiPM front-end electronics in NEXT

- An approach based on gated integrators (NEXT-DEMO)
- An approach based on pulse stretching & sampling (NEXT-DBDM)
- A proposed front-end scheme and board for NEXT-100


# Review of NEXT-DEMO and NEXT-DBDM solutions

*Our proposal for NEXT-100 is based on the first results  
with these two developments*

# Review: NEXT-DEMO FE-SiPM read out (1/3)

NIM A, Vol. 695, 11th December 2012, Pages 229–232



Readout electronics for the SiPM tracking plane in the NEXT-1 prototype

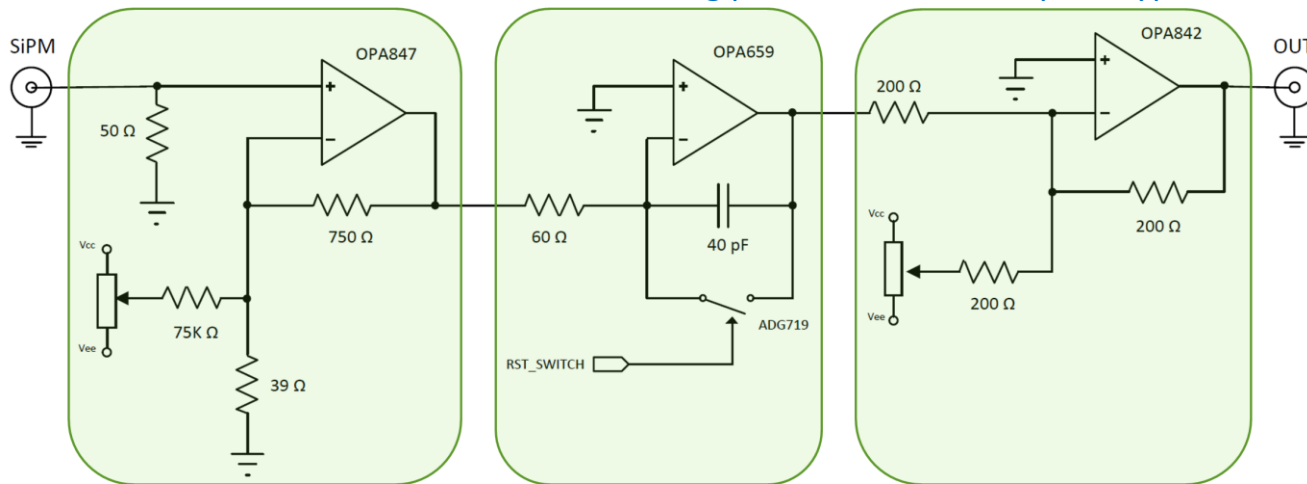


Stage 1: transimpedance amplifier + offset correction

Stage 2: gated integrator

Stage 3: inverter + offset correction

  
 
# Review: NEXT-DEMO FE-SiPM read out (2/3)



RD51 SRS readout/DAQ chain




16x SiPM-FE boards

CAT6 cable

Data

Clock, trigger, cmd

 

2x LVDS I/O cards



2x FECs

2x GbE



# Review: NEXT-DEMO FE-SiPM read out (3/3)


These amplifiers will not be used in NEXT-100 because:

- ❑ Power dissipation would be too high ( $10V * 20mA * 3 = 600 \text{ mW/ch}$ ). This requires active cooling
- ❑ Offset adjustment by hand for  $\sim 7000$  ch may be a nightmare, so we need automatic adjustment
- ❑ Also: gated integrator requires a switch, 6.800 switches may create a large noise



As a result we defined a new scheme (D.Nygren) that has been tested in NEXT-DBDM (next slide)...
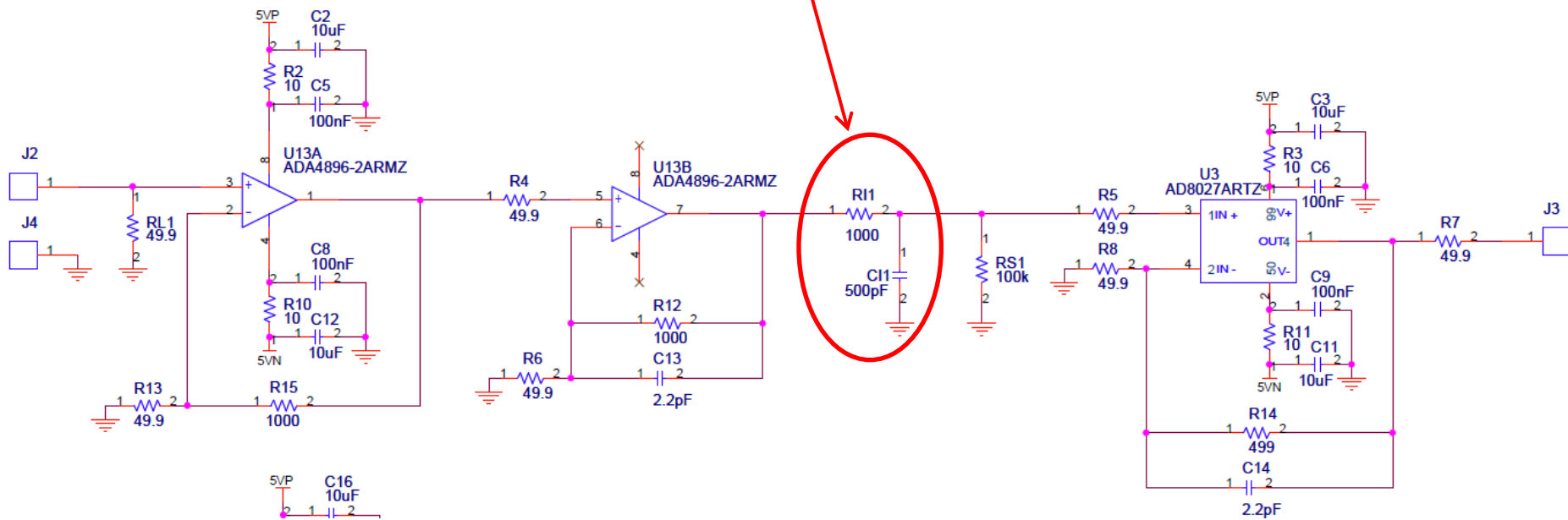
# Review: NEXT-DBDM FE-SiPM read out (1/4)

Dave: "Replace the gated integrator with a simple RC and use low power amplifiers"



  John Joseph: "Circuitry can be further simplified by using multiplexers before the ADC"





# Review: NEXT-DBDM FE-SiPM read out (2/4)



Source: [http://www.analog.com/static/imported-files/product\\_selection\\_guide/High\\_speed\\_amps\\_sel\\_table.pdf](http://www.analog.com/static/imported-files/product_selection_guide/High_speed_amps_sel_table.pdf)

Amplifier	Type	BW 3dB G=1 (MHz)	Noise (nV/√Hz)	V <sub>offset</sub> (mV)	I <sub>bias</sub> (μA)	I <sub>quiescent</sub> (mA)	Cost (\$)	Supply (V)
AD8005	CFA, single	270	4	30	10	0,4	1,63	5, ±5
AD8038/9	Single/dual	350	8	3	0,75	1	0,86/1,21	3, 5, ±5
AD8011	CFA, single	400	2	5	15	1	2,27	5, ±5
AD8014	single	480	3,5	5	15	1,1	1,19	5, ±5
ADA4841-1/-2	Single/dual	80	2,1	0,5	5,3	1,2	1,61/2,32	2.7, 5, ±5
ADA4940-1/-2	DIFF single/dual	240	3,9	0,4	1,55	1,25	1,79/2,95	3, 5
AD8029/30/40	Single/dual/ quad	125	16,5	5	1,3	1,3	0,86/1,21/ 1,62	2.7, 5, ±5
ADA4853	Single/dual/ triple	100	22	4	1,6	1,4	0,56/0,7/0,86	3, 5, ±5
AD8012	CFA dual	350	2,5	4	12	1,7	2,5	5, ±5
AD4896-2	Dual	230	1	0,5	17	3	3,2	3, 5, ±5
AD8027/8	Single/dual	190	4,3	0,9	6	6,5	1,2/1,91	3, 5, ±5

**Valencia&LBNL final decision:** higher noise and offset voltage but low power (30 mW/ch) and cost (\$3,48/ch)

**Initial LBLN prototype:** higher performance but also higher power (125 mW/ch) and cost (\$7,8/ch)
 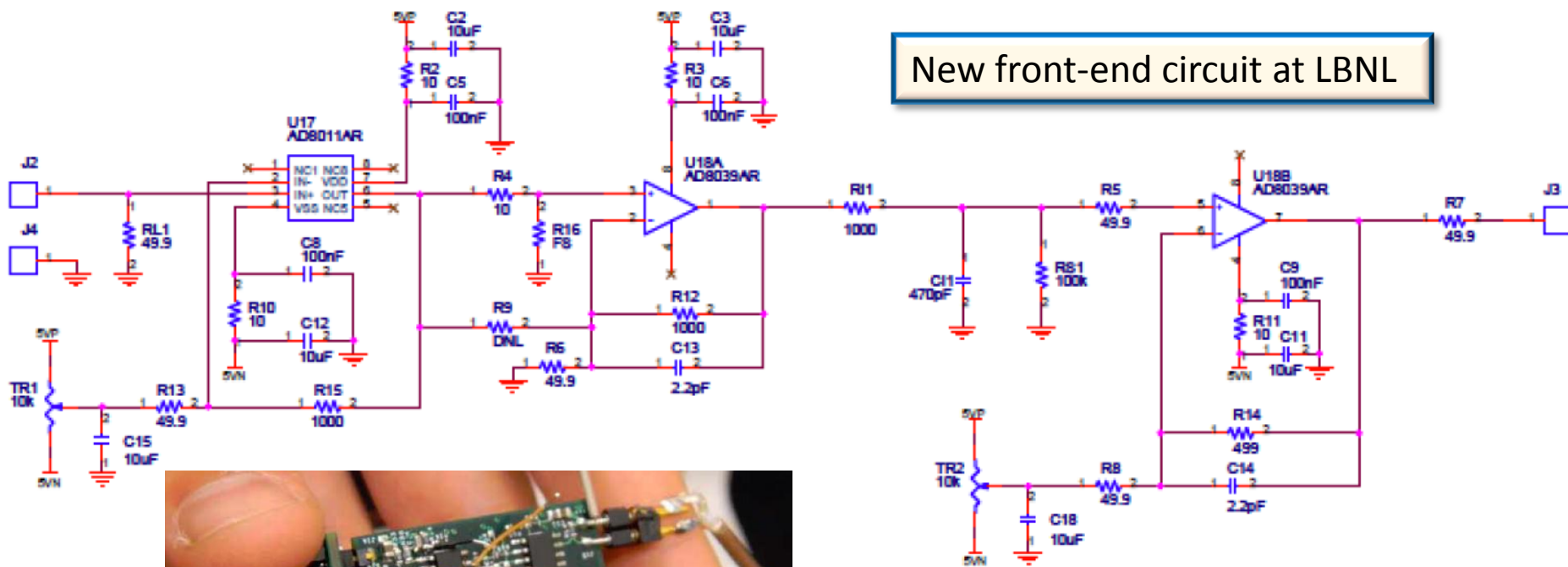
# Review: NEXT-DBDM FE-SiPM read out (3/4)



Based on AD8011 and AD8039  
Still manual offset control  
COTS external digitizer (up to 100 MHz)

16-ch mux and 4-ch front-end boards



# Review: NEXT-DBDM FE-SiPM read out (4/4)

*Digitized data have been analyzed (Lisa Gerhardt, LBNL) to find out the required sampling rate (and results show that 2-3 MHz is acceptable)*

*This prototype shows the feasibility of the new readout concept for NEXT-100*


 
 
 
 


Figure 5: Schematic of the muon tracking test setup for NEXT-DBDM.

 

**Muon tracking**

# Requirements for NEXT-100

*A requirements document is not yet finished, but let's highlight the main desing parameters*

# Requirements for NEXT-100


*A sound front-end design for NEXT-100 should:*

- Resolve the single photoelectron to ease calibration*
  - The gated integrator allows pe-based calibration*
  - The stretching&sampling approach requires a bypassable filter*
  - New LBNL analog stage dissipates 30mW/ch in the amplifiers. We could choose other opamps, trading power for noise, in order to enhance spe discrimination*
  
- Provide enough time and amplitude resolution (tbd)*
  
- Have an automatic offset voltage compensation*
  
- Be able to perform zero suppression on-the-fly and have an event buffer (see DAQ requirements)*

# Proposal for NEXT-100 (amplifier circuit)

*Use NEXT-DBDM circuit topology, add a switch to bypass the filter and an FPGA-controlled offset voltage adjustment*


Small PCB area (1,7cm<sup>2</sup>)

 

# Proposed amplifier circuit

Final opamps will be a trade off between power, noise and cost (AD8011 & AD8039 optimize power and cost)

FPGA-controlled DAC (128 DAC channels)

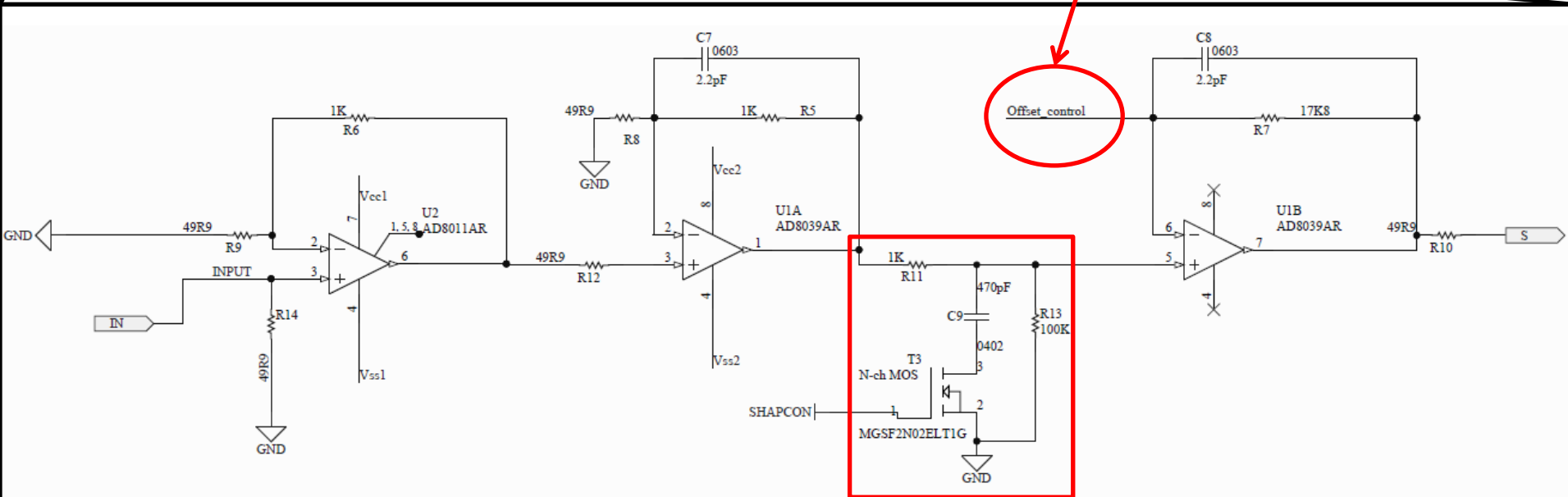

500 ns shaping filter  
Can be bypassed to enhance  
spe detection

# Sampling & offset voltage

## On the signal and its sampling:

- ❑ RC time constant is approx.  $0.5 \mu\text{s}$
- ❑ Sampling rate is 2-3 MHz

## On the offset voltage adjustment: coarse (analog) + fine (digital)

- ❑ Coarse automatic offset adjustment with a DAC (at the 3rd stage)
- ❑ ADC dynamic range is typ.  $2V_{pp}$
- ❑ Keep signal dynamic range in approx.  $1V_{pp}$
- ❑ Leave the additional ADC range for the residual offset voltage
- ❑ Correct the residual offset after digitization (fine adjustment) !!




# Proposal for NEXT-100 (front-end board -FEB)

*Packing 128 analog stages (amplifiers) and its required multiplexers, buffers, ADCs, FPGA, data transceivers and voltage regulators*


# The whole mux&sampling chain for 128 channels

128 analog channels

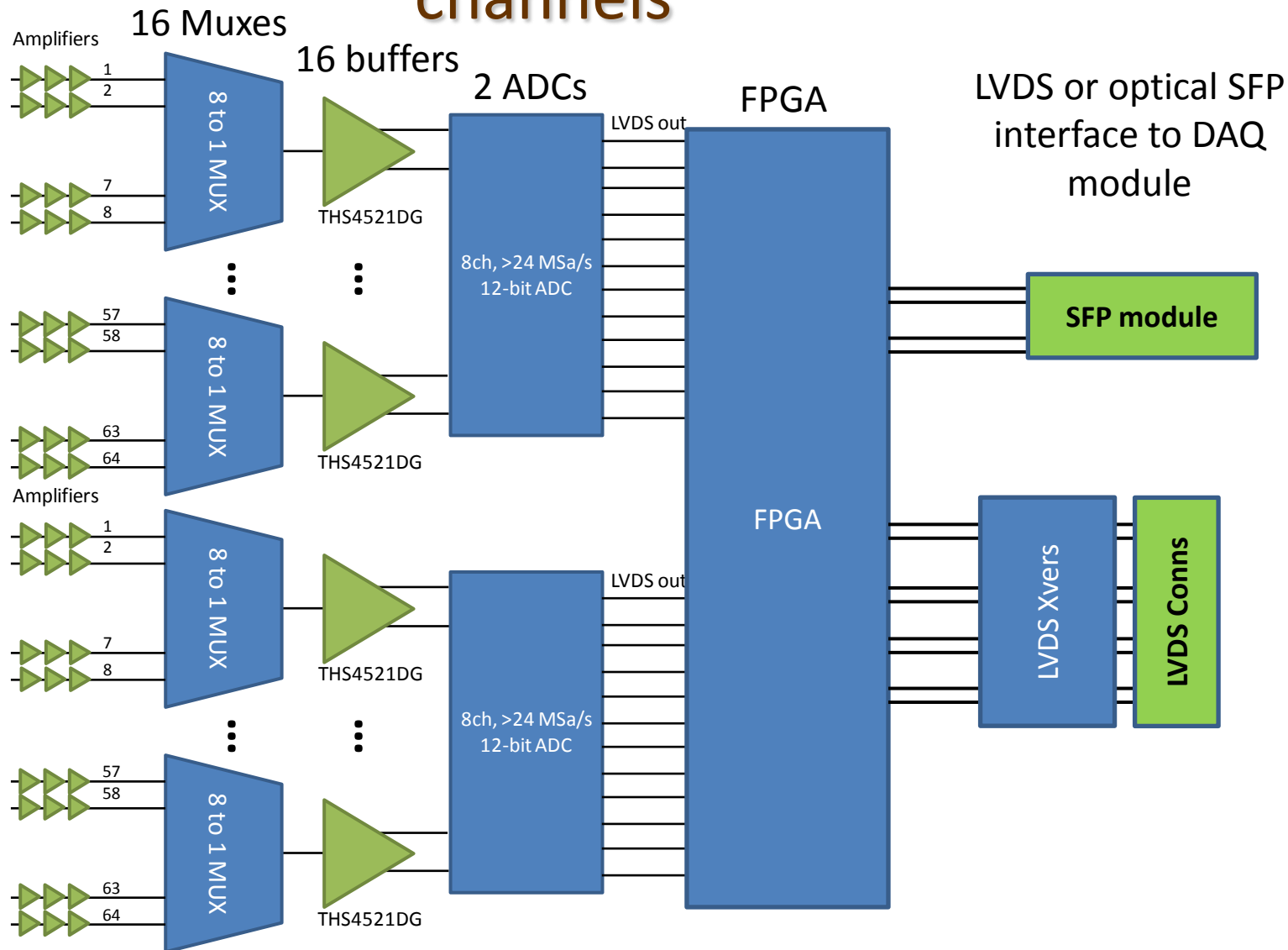

# FEB layout (missing: SFP)

6U x 280mm Eurocard

 

# Data handling and buffer in FEB

## ❑ **FPGA**

- ❑ *estimates signal baseline*
- ❑ *automatic control for per-channel coarse offset voltage compensation*
- ❑ *automatic fine correction for offset voltage*
- ❑ *controls multiplexers and ADCs*
- ❑ *zero-suppresses data (based on configurable parameters)*
- ❑ *timestamps and buffers data*
- ❑ *sends data to DAQ when a trigger is received*
- ❑ *allows monitoring&control from DAQ module*

## ❑ **Virtex-6 LX130T, 195T or 240T in BGA784 (footprint compatible)**

- ❑ *same FPGA as in ATCA FEC (DAQ module)*
- ❑ *internal dual-port buffer size: 9504/12384/14976 Kb*
  - ❑ *This allows 6336/8256/9984 samples/ch buffer depth*
  - ❑ *At 2MHz sampling, 2 chamber drift times, one full raw event needs 6400 samples/ch*

## ❑ **Uplink throughput**

- ❑ *LVDS: 400 Mb/s (as used in NEXT-DEMO)*
- ❑ *SFP with simple protocol for clock, trigger, slow controls and data: up to 1Gb/s (currently under development, CERN)*

# Proposed FE&DAQ architecture for NEXT-100 (SiPM tracking plane partition)

## NEXT-100 DAQ – ATCA Architecture (see presentation on DAQ)

