SLAC Project-X RF Development November 14th 2012


Rosa Ciprian, Heinz Schwartz







RF high power sources 325MHz & 650MHz

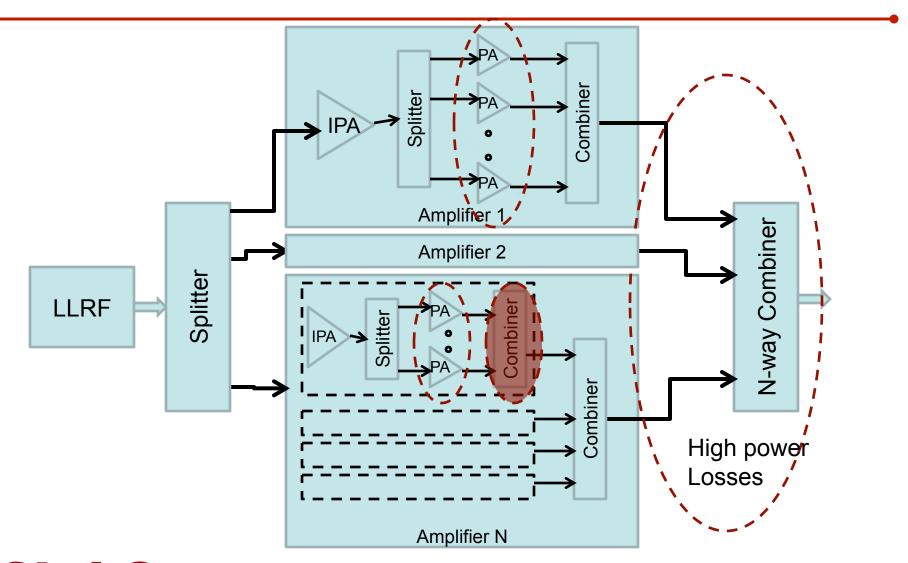



OUTLINE


- Baseline amplifier progress
- 2.5 kW vendor-built evaluation
- Options for combining networks
- Controls, LLRF



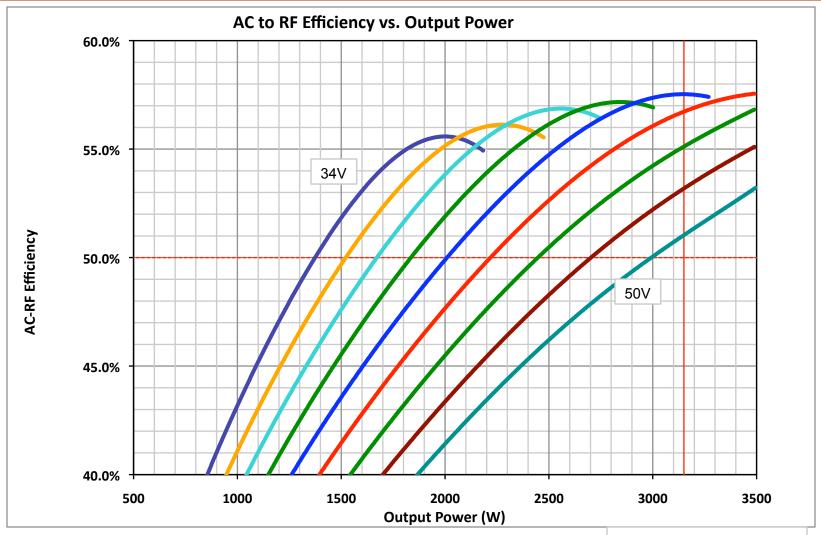2.5kW Amplifier Eval


- Nautel delivered amplifier by end of September.
- Migrated to 8 amplifiers/module (redundancy)
- Transistors evaluation of efficiency > 70%
- Efficiency varies with operating point
- Overall dimension 3U 19" rack: ~ 19" x 5.2" x 30"
- MEASURED AC-RF efficiency @ SLAC:~60% @ 2.5kW
- At 25% of max power ~800W AC-RF efficiency 48%







Nautel verification results

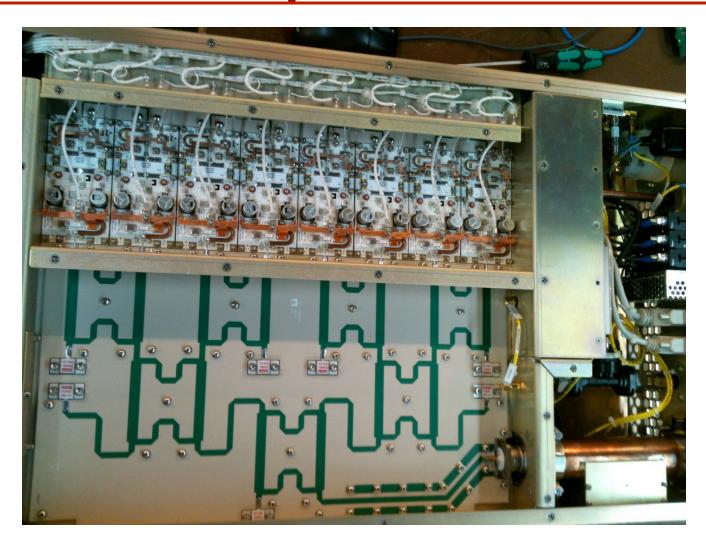







Others:

- 2.5 GPM cooling water @ ~30°C
- Best efficiency at ~800W is with Vd=21V and
 -1.5dBm input
- Best efficiency at ~2.5kW, Vd= 38V and 0dBm
- Max power ~3.5kW efficiency ~58% with Vd = 44V
- Verified some local and remote controls and protection
- ~80 lb



Combiners - losses/max pwr

| TYPE | Att (dB/ 100ft) | Average Pwr (kW) | Bend radius (in) |
|------------------------------------|--------------------|---------------------|---------------------|
| Microstrip RT6035HTC 125mils | 8.64 | 2.7 (*) | |
| Microstrip RT6035HTC 250mils | 6 | 4 (*) | |
| 7/16" HELIAX | 3 | , 2 | |
| 1 5/8" HCA158-50 air dielectric | 0.5 | 7.3 | 7 |
| 1 5/8" LCF158-50 CELLFLEX foam | 0.54 | 6.3 | 8 |
| 3" HCA-300 HELIFLEX air dielectric | 0.338 | 14.6 | 11 |
| 5" HJ9-50 HELIAX air dielectric | 0.222 | 30 | |
| 5" HCA495-50 HELIFLEX air dielec | 0.23, | 31.8, | 20 |
| 6 1/8" HCA618-50 HELIFLEX air | 0.157 | 65.6 | 39 |
| WR1150 11.5"X5.75" | 0.09 | 200 (**) | |
| WR1500 15"x7.5" | 0.0553 | 500 (**) | |



(*) For a 55°C rise

(**) For a 23°C rise, copper

30kW Combiners Failure Mode

| | 8-way | 10-way | 12-way | ,16-way |
|---------------------------|-------|--------|---------------|---------|
| Output power 1 fail (%) | 77% | 81% | 84% | 88% |
| Power/mod for 30kW (kW) | 3.75 | 3 | 2.5 | 1.875 |
| Power/mod for 1 fail (kW) | 4.9 | 3.7 | 2.975 | 2.14 |
| Output pwr 2 fail (%) | 56% | 64% | 69% | 77% |



30kW Combiners

- 2kW modules using AB amps just need two levels of hybrid combiners within.
- Gysel combiner 16x1 (2kW => 30kW) with coax inputs offers low loss. Projected design from Nautel would not fit in a 19" rack, but very close
- PS and controls separately from amp modules.
- Independent modular power lines to each subgroup (4x4 or 2x8) for redundancy and ease of implementation



30kW Efficiency assessment

Choice of 100W, 250W and 500W affects overall efficiency and dimensions:

- 100W class F amplifiers with drain efficiency in the 80% and assuming 500W modules in the 70% can get 58% overall efficiency. Modules can be arranged in 2 x 19" racks.
- 250W amplifiers with drain efficiency in the 60% range and assuming 50% at the 1.9kW module, can get to 47% overall efficiency. Modules could possibly fit in a single 19" rack.
- 500W amplifiers (derated to 320W) with drain efficiency in the 70% range and assuming 57% at the 2.5kW module ~3U each, can get to 53% overall efficiency. Modules will fit in a single 19" rack.
- The same 500W amplifiers arranged into a 2kW module can get up to 58% overall efficiency with a 16x1 Gysel combiner. Modules will be less than 2U each.



Controls

- No-beam load is about 25% of the nominal load.
- Process for maximum efficiency (class AB amplifiers):
 - Reduced drain voltage during no-beam mode
 - Ramp up drain voltage to prepare for nominal load.
 Efficiency is not optimized during this time
 - LLRF to bring up output power
 - This process can be implemented on the LLRF side (lookup table?), with digital control for PS and analog signal for phase and amplitude.
- For a class F amplifier, output power is directly controlled from the LLRF side, no major difference in efficiency throughout. Response time (BW) depends on power supply.

Additional Slides



Amplifiers - commercial

- MRFE6VP5600H: 600W CW 60% efficiency
- BLF888B: (NXP/Nautel)
 - Up to 600W
 - 500W @ 48V with 71% drain efficiency and 22dB gain.
 - Phase change
 - less than 0.1deg over 1 hour
 - ~0.45deg with 3°C change at baseplate
 - ~5deg with a 7V drain voltage change
 - ~2.5deg with a 10% load change.
 - Harmonics: More than 50dBc up to 3.9GHz.

